

New Concepts for Reaching 99% Efficiency in Compact Power Converters for Regenerative Variable Speed Drives


Christos Leontaris, Gean Jacques Maia de Sousa, Lou Scholtissek, Marcelo Lobo Heldwein (presenter)

13 November 2025

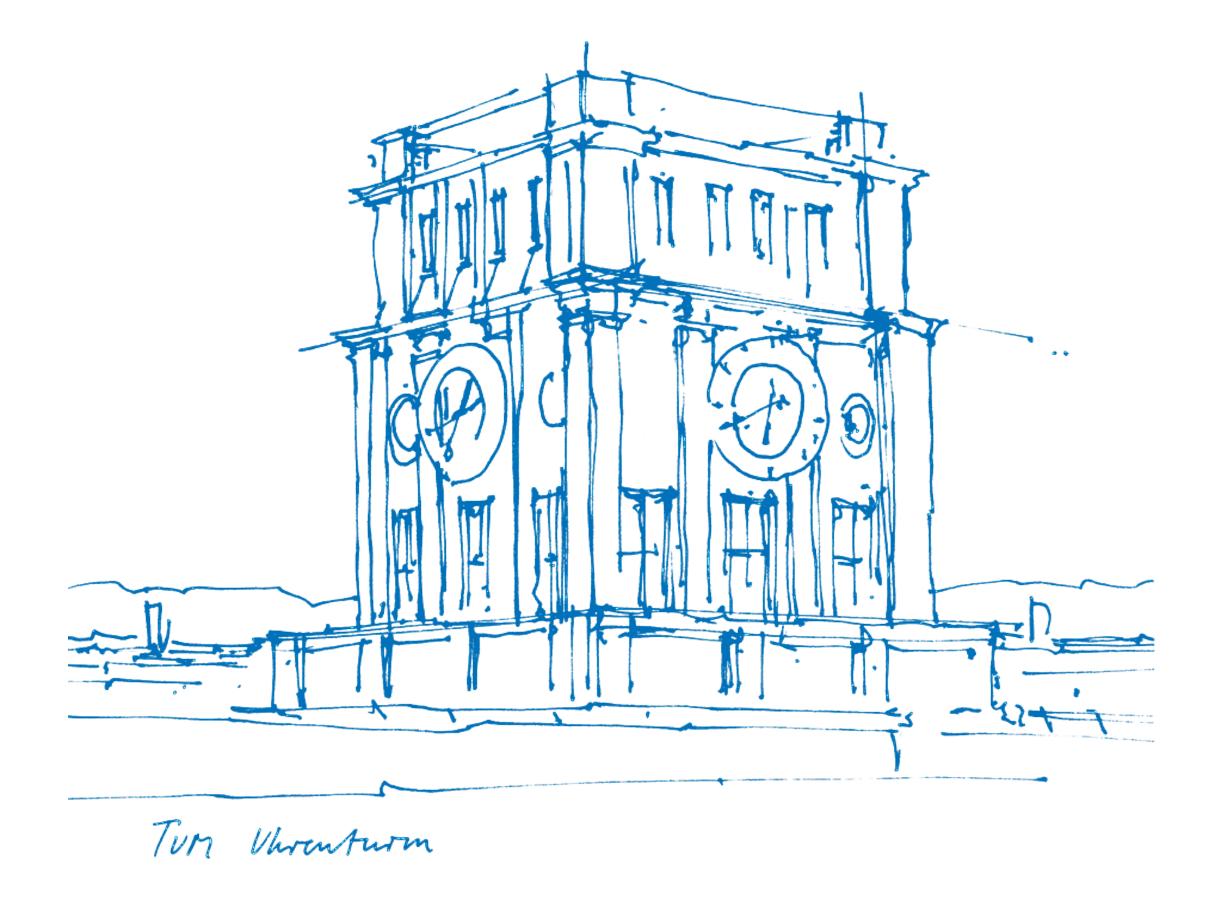Presentation at the Webinar 2025 - SOBRAEP / PELS









# Brief history of the Technical University of Munich (TUM)

Ever since it was founded in **1868**, the Technical University of Munich has seen itself as the servant of an increasingly technical society. Then as now, TUM researchers are looking for solutions to the great challenges of the future. The newly founded university was intended to place technical education in Bavaria on the foundation of natural sciences. In doing so, it made a decisive contribution to technological progress worldwide - and produced several Nobel Prize winners and important

inventions.



Hörsaal im ehemaligen Chemischen Institut (1909) Bild: TUM.Archiv



### TUM (a few numbers)

#### 50.484 Students

are enrolled at our university in the winter semester 2022/23. Of them, 36% are female students, 41% have come from abroad for their eduction at TUM.

#### 9,676 Publications

by TUM academics appeared in 2022 in international journals (peer-reviewed articles, conference papers, reviews; source: Scopus 2023).

#### **18 Nobel Prizes**

have been awarded to TUM professors and alumni since 1927, e.g. to Rudolf Mößbauer (Physics) and Ernst Otto Fischer (Chemistry).

#### 78 Start-up companies

were founded at TUM in 2022.

#### 643 Professors

research and teach at TUM. We have appointed 209 professors from universities abroad (as of 2006–2020).

#### 1,109 Doctorates

were awarded by TUM in the academic year 2020/21. Modernized doctoral degree regulations were published in 2012.

#### 24 Leibniz Prizes

have been awarded to TUM scientists since 1987 (as of: 2023). Our long-serving President Wolfgang A. Herrmann received it in 1987.

#### 73 Patents

for inventions from TUM researchers were submitted to Patent Offices 2020.

#### 8 Schools and departments

form the academic foundation of our university, connected by 6 integrative research institutes at the interfaces between disciplines.

#### 430.4 mio. Euros third-party funding

for research and teaching was secured in accounting year 2021 making TUM one of German's top-ranked universities.

#### **8 Humboldt Professors**

have joined the TUM ranks (as of: 2022) – a major success in this competition for top international talent.


#### > 6,000 Cooperation agreements

were concluded with companies or other partners for research projects since 2013.



### TUM structure

# Bridges to Innovation

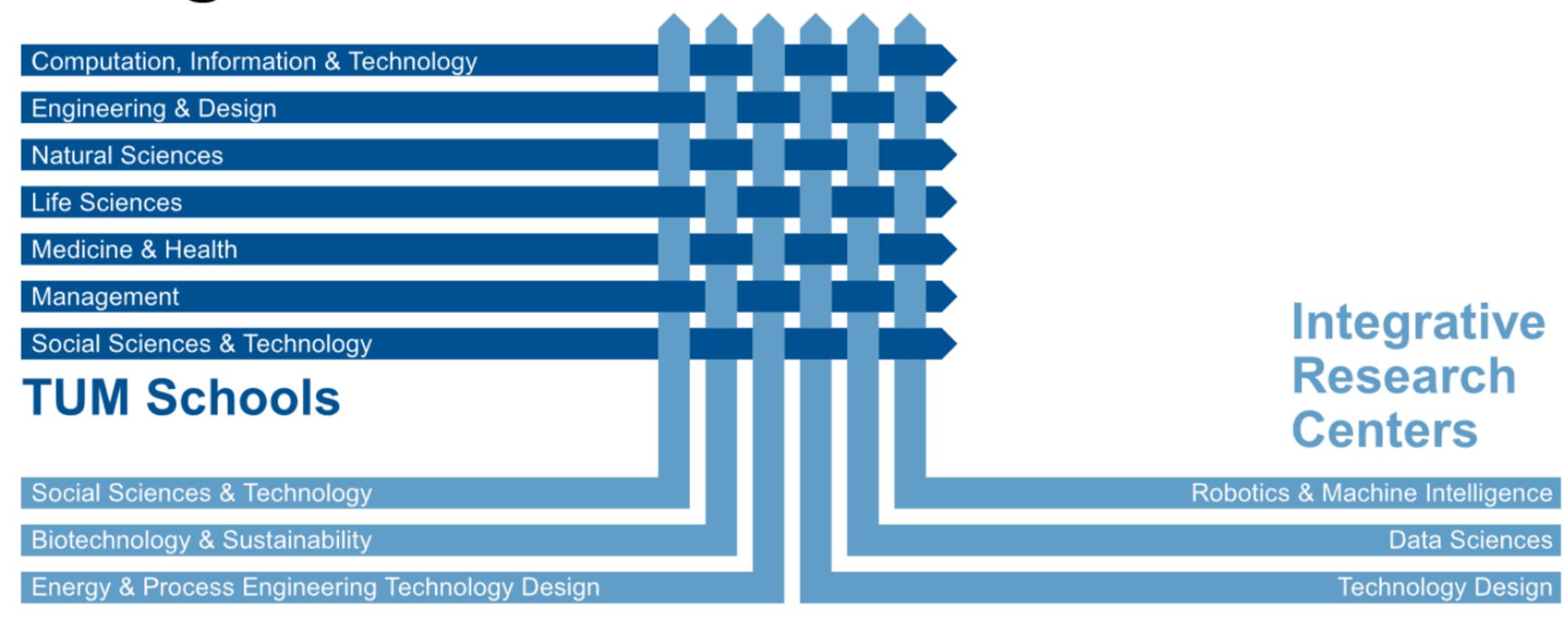

TUM School of Engineering and Design | Technical University of Munich






# A part of our labs



Photo: Wei Tian (TUM)




# Path to net zero emissions by 2050

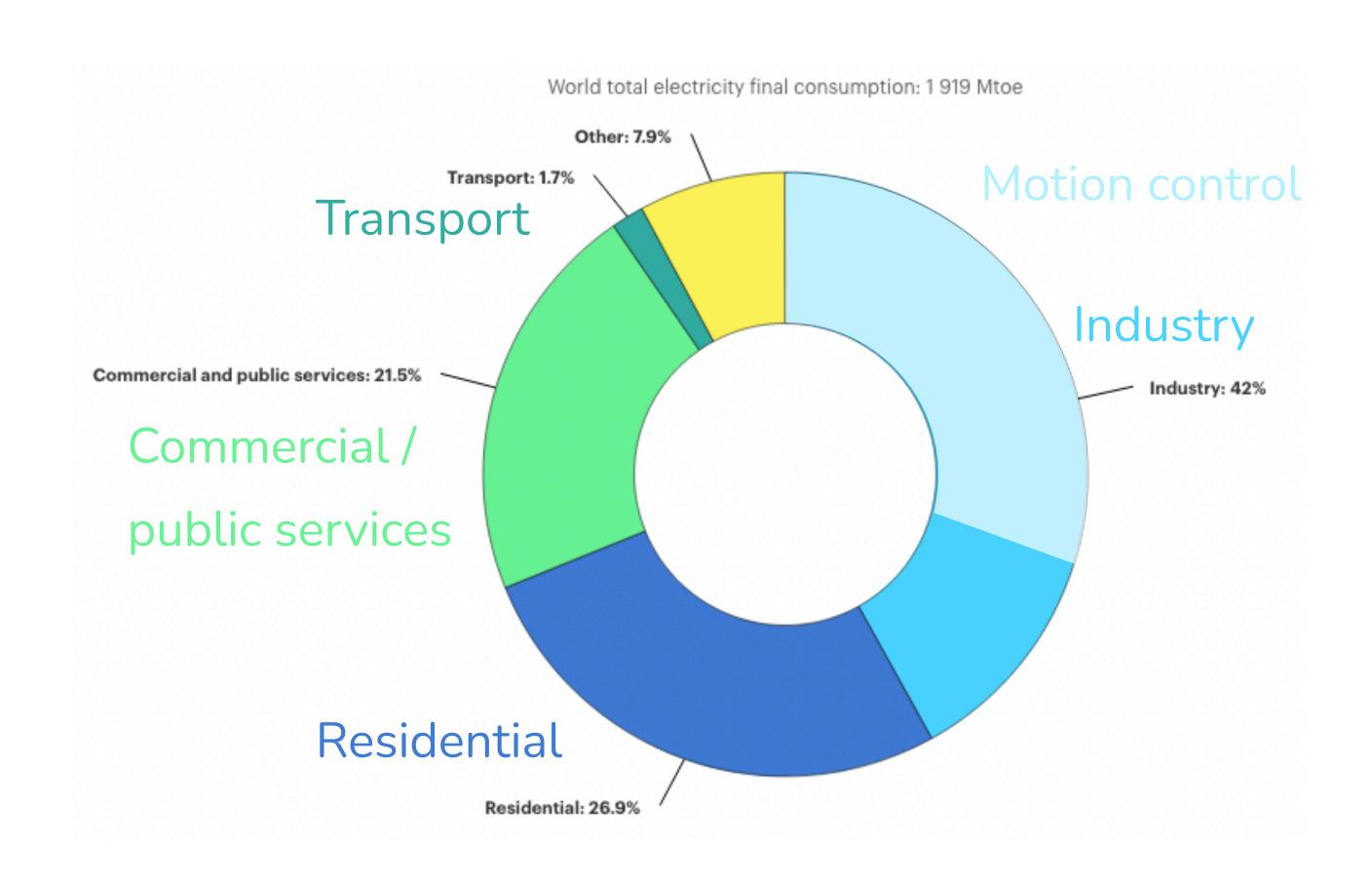




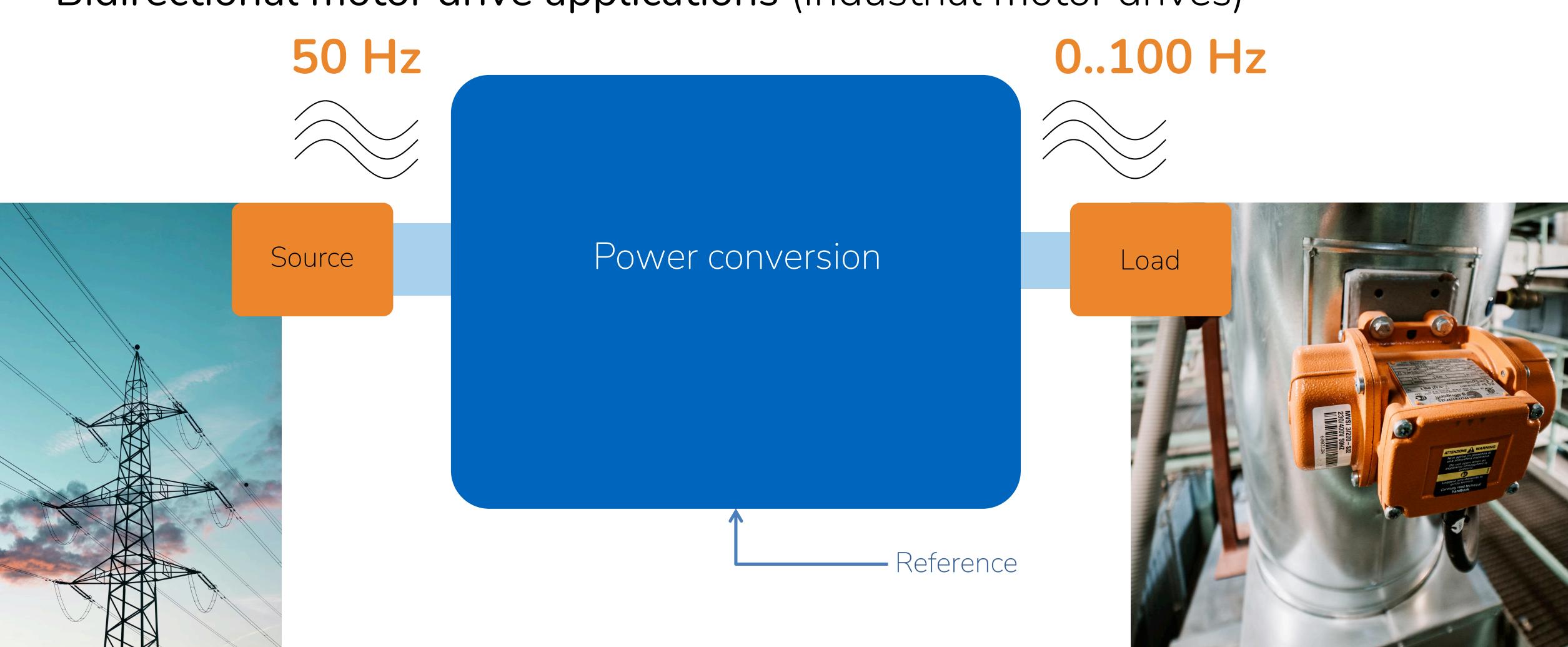Bidirectional motor drive applications (Industrial motor drives)






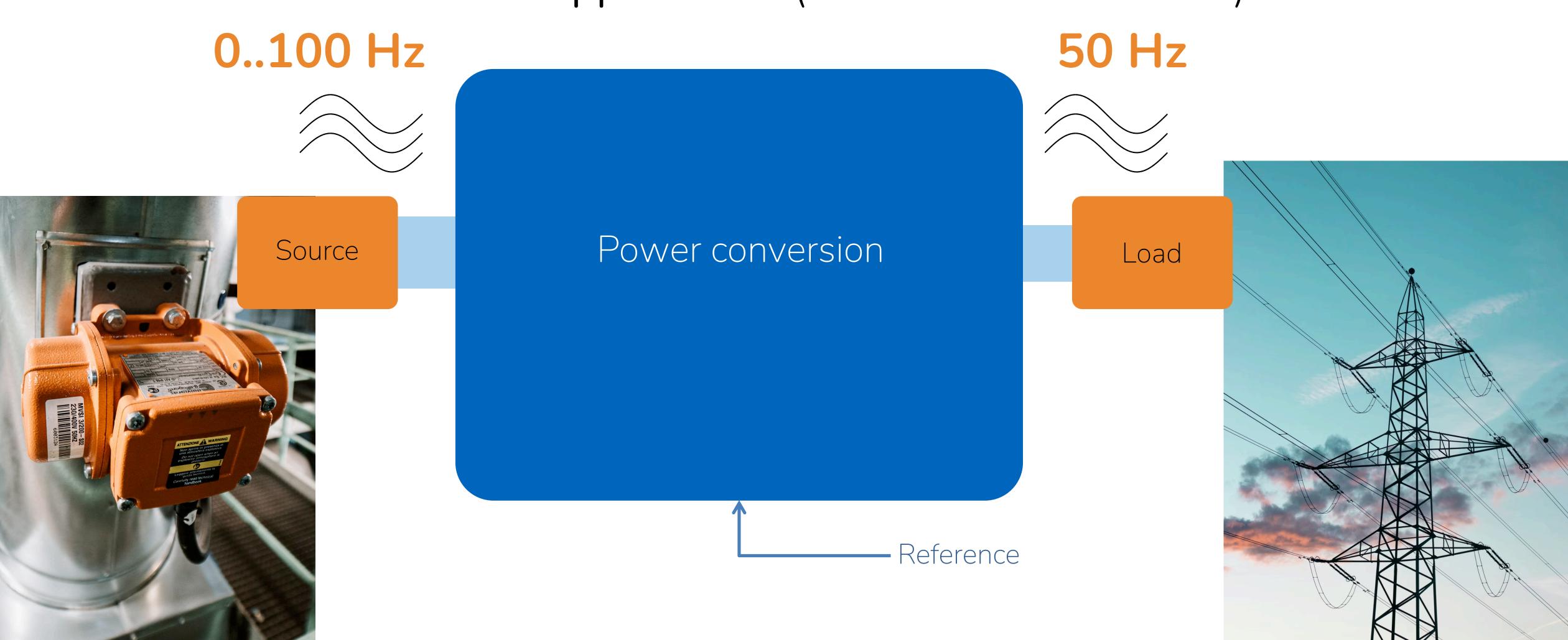Bidirectional motor drive applications (Industrial motor drives)




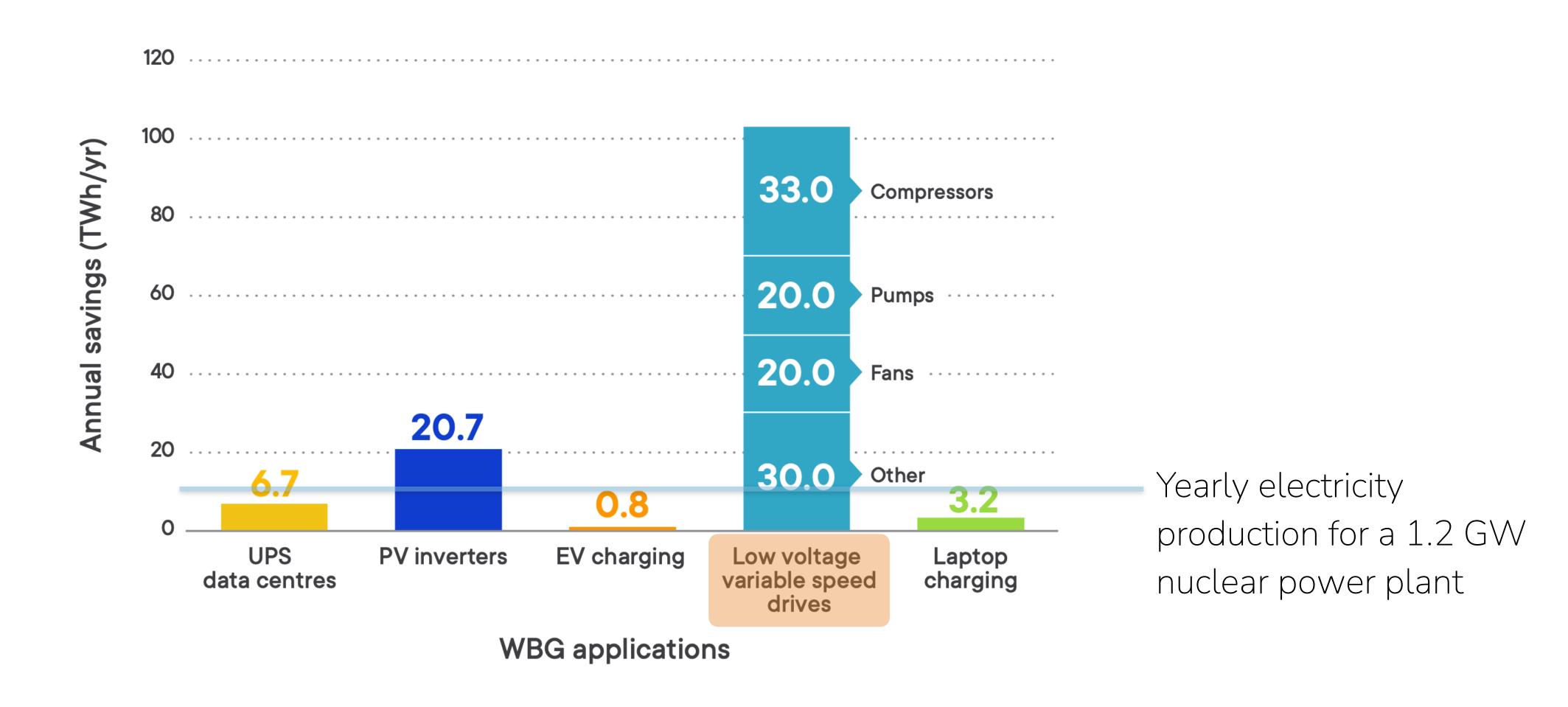
# Potential energy savings for different applications in 2021





Source: https://superefficient.org/

10



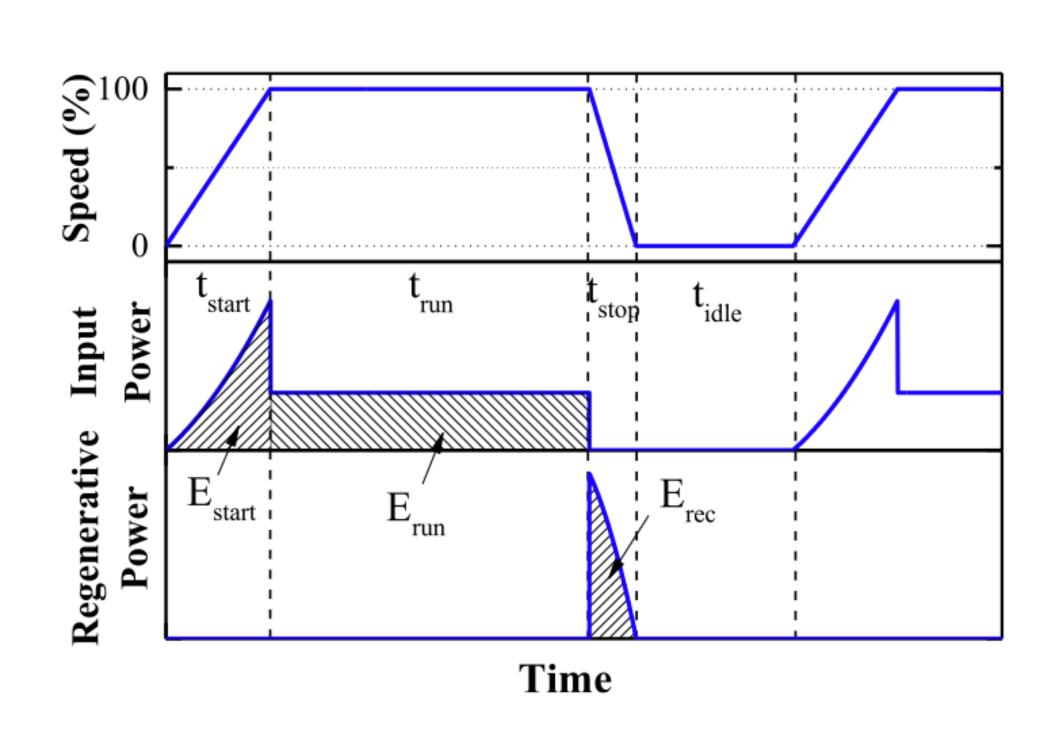
# Energy lost (or recovered) during motor deceleration




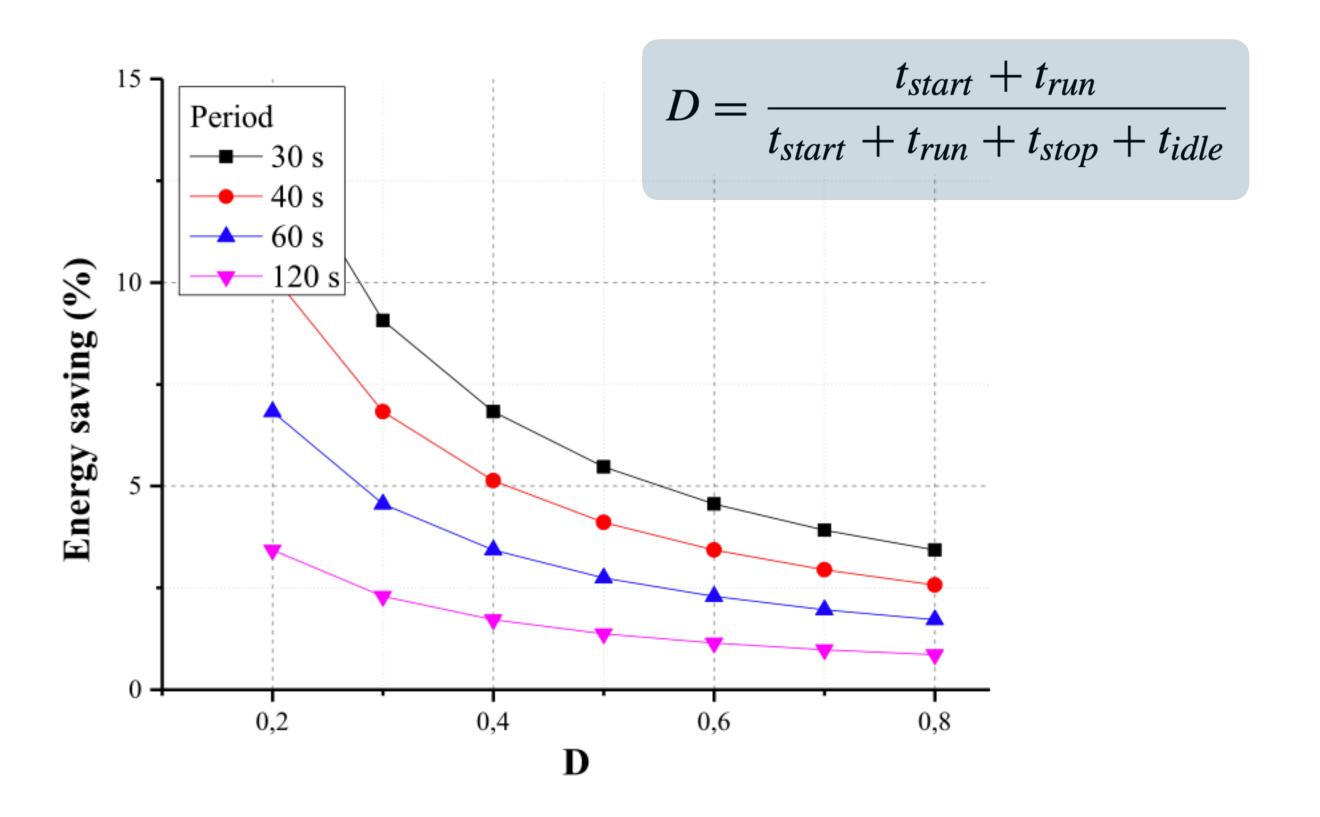


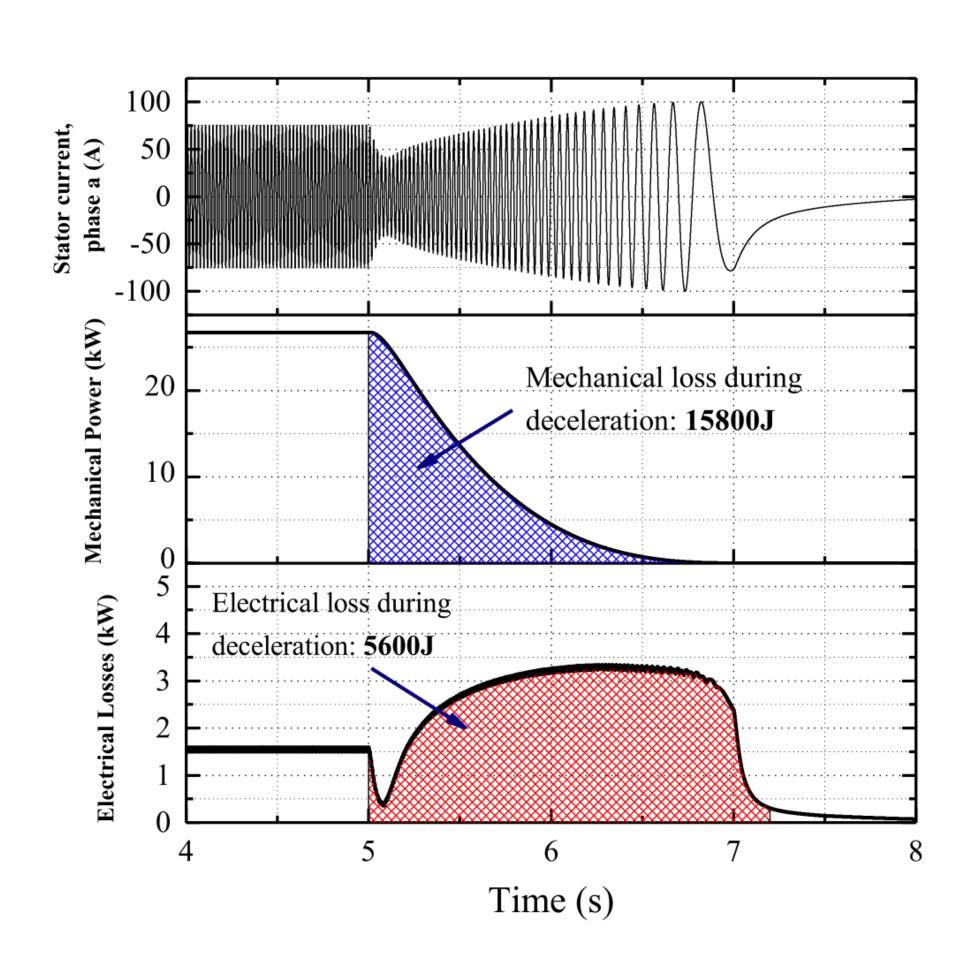
# Energy losses during motor deceleration




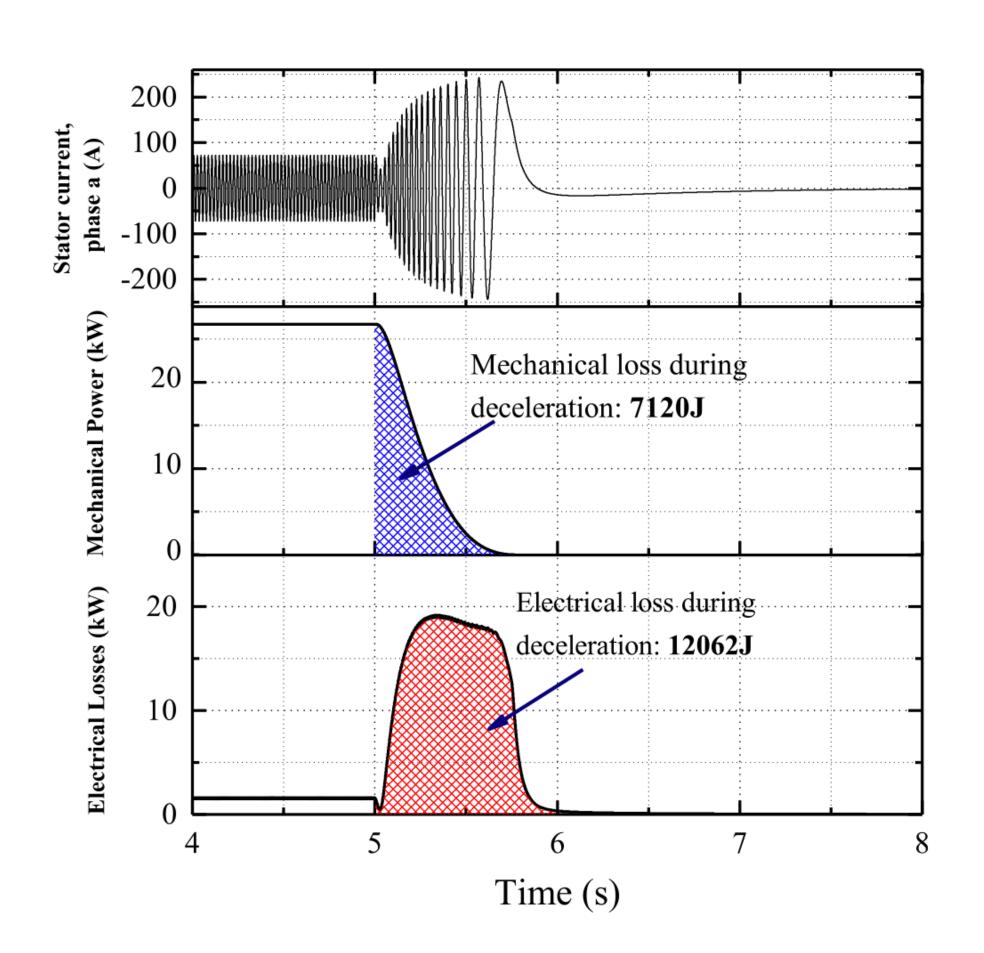

Source: I. Karatzaferis, E. C. Tatakis and N. Papanikolaou, "Investigation of Energy Savings on Industrial Motor Drives Using Bidirectional Converters," in IEEE Access, vol. 5, pp. 17952-17961, 2017, doi: 10.1109/ACCESS.2017.2748621.



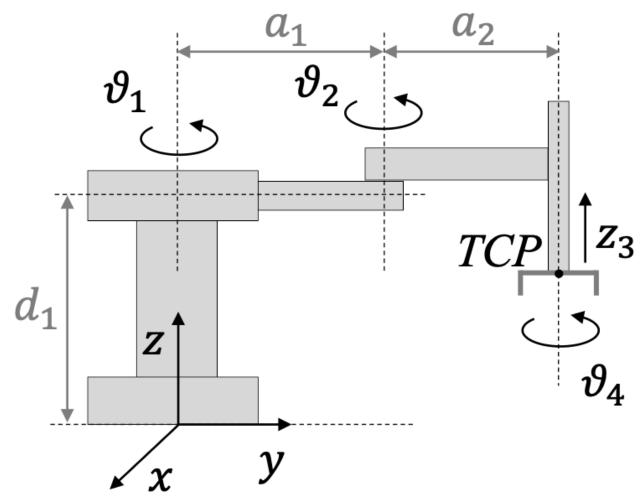
# Energy recovery potential in industrial robots




Denavit-Hartenberg parameters

i	$\alpha_i$ [rad]	<i>a<sub>i</sub></i> [mm]	$d_i$ [mm]	$\vartheta_i$ [rad]
1	0	425	398	$artheta_1$
2	0	375	0	$artheta_2$
3	0	0	$z_3$	0
4	0	0	0	$artheta_3$

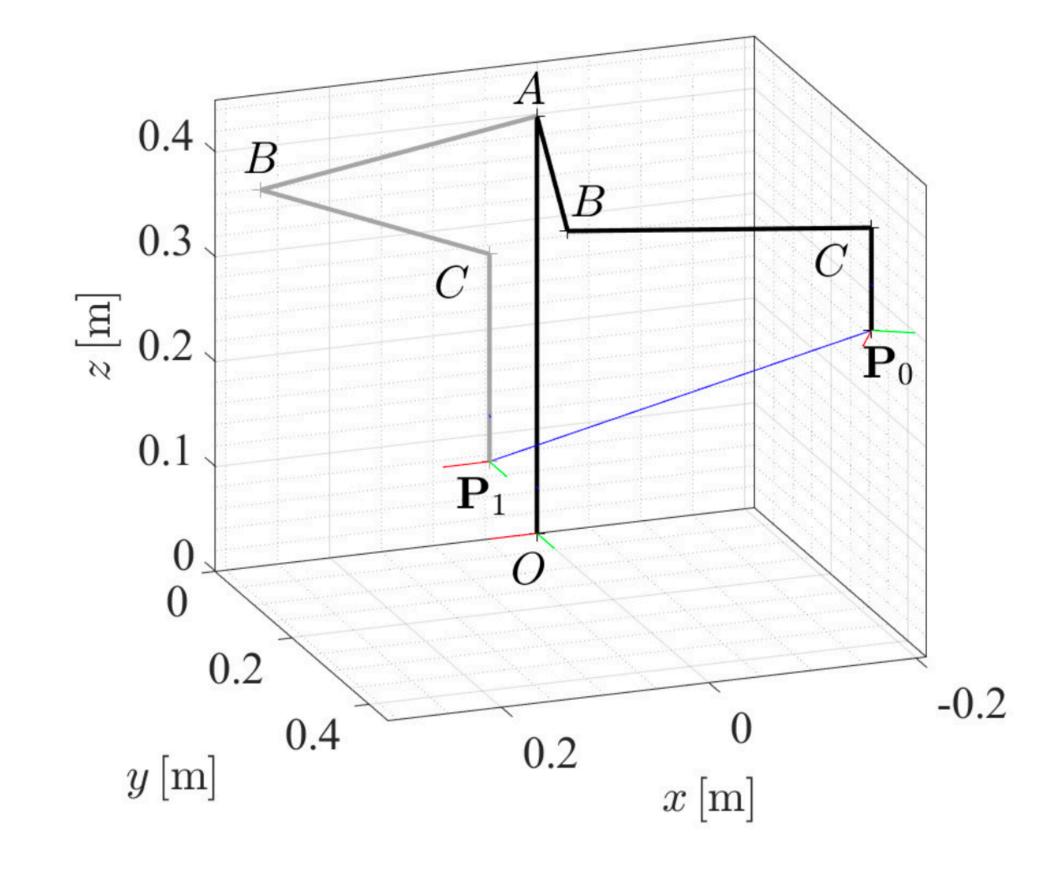


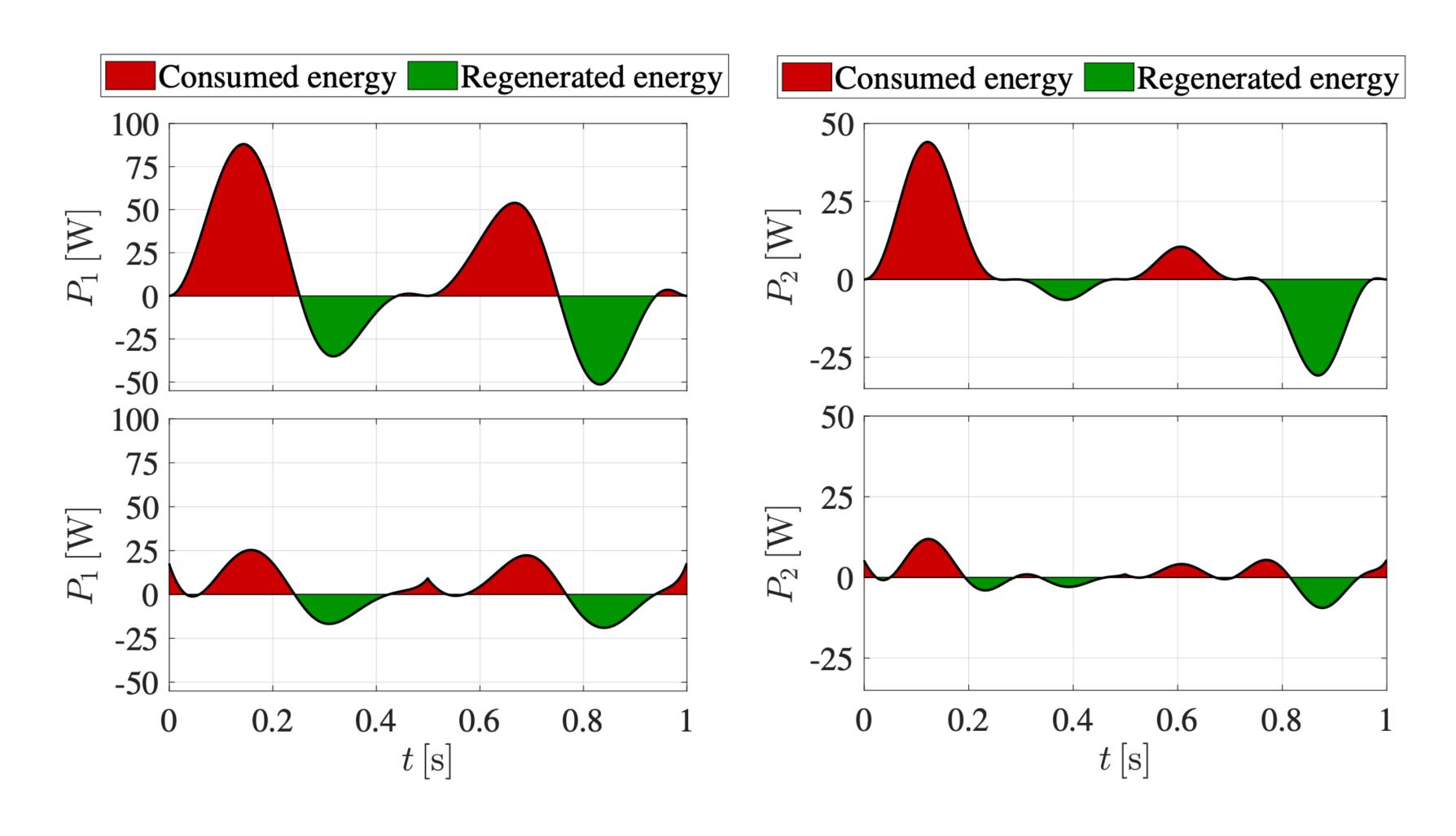
### Energy recovery potential in industrial robots





# Integrated motor drives

Industrial examples





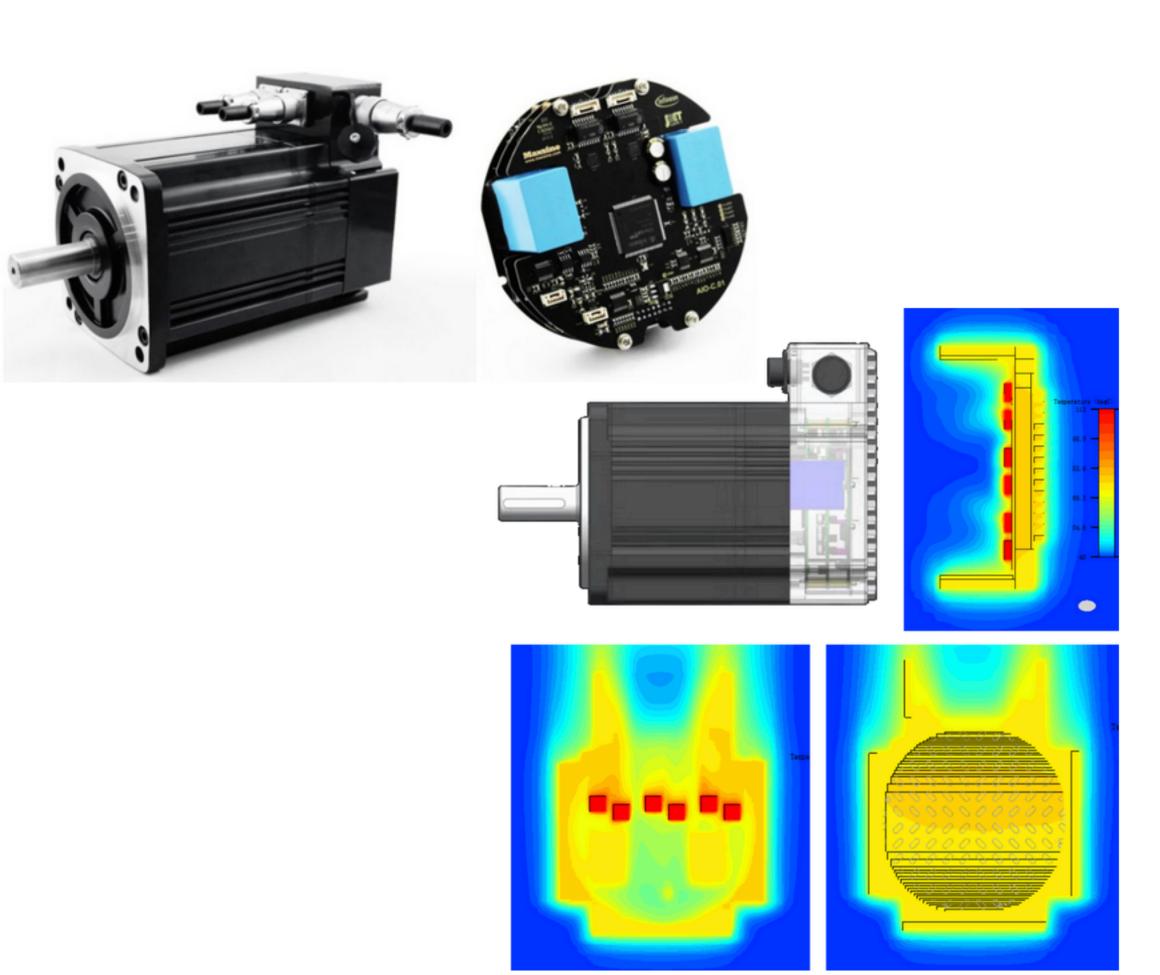


Fig. 2: Finite-element thermal analysis of a compact, fully integrated SiC-

https://semiengineering.com/sic-and-industrial-servos-a-perfect-match/





### Integrated motor drives

Great potential for improving industrial systems!
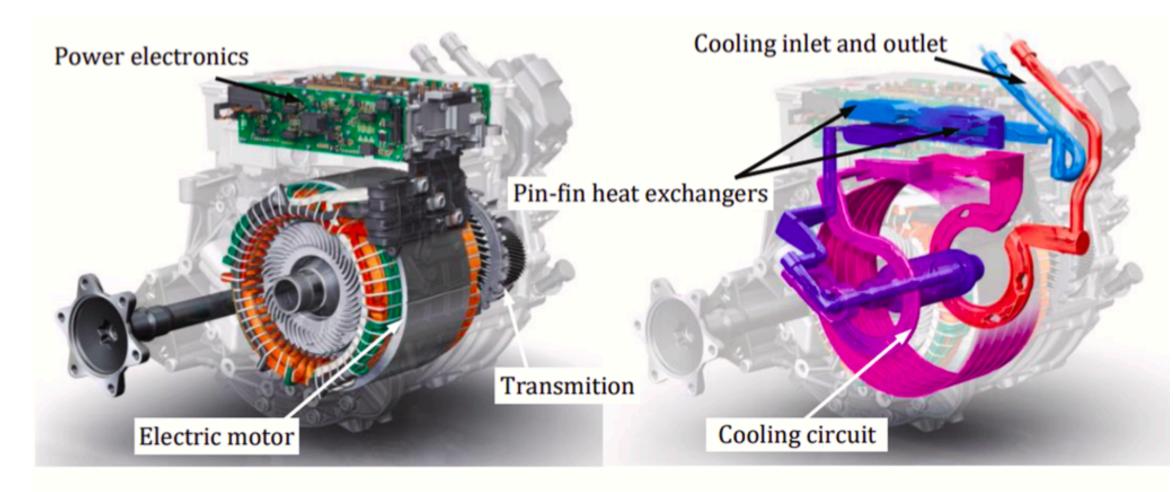
#### Challenges:

- Cooling (two subsystems with different requirements)
- High dv/dt right at the motor terminals (overvoltages at the winding, HF bearing currents, core losses, etc)



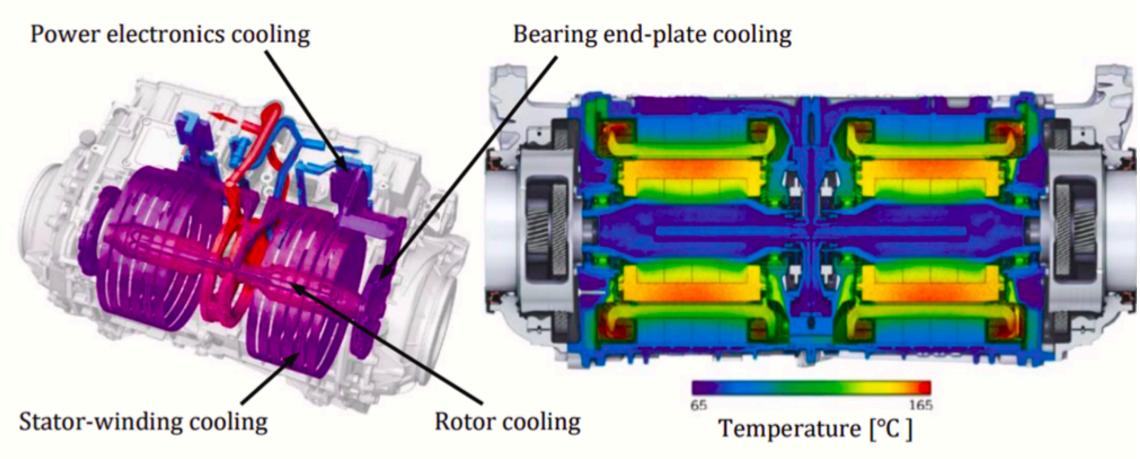



### Integrated motor drives


Great potential for improving industrial systems!


#### Challenges:

- Cooling (two subsystems with different requirements)
- High dv/dt right at the motor terminals (overvoltages at the winding, HF bearing currents, core losses, etc)

Solutions from the power converter perspective:

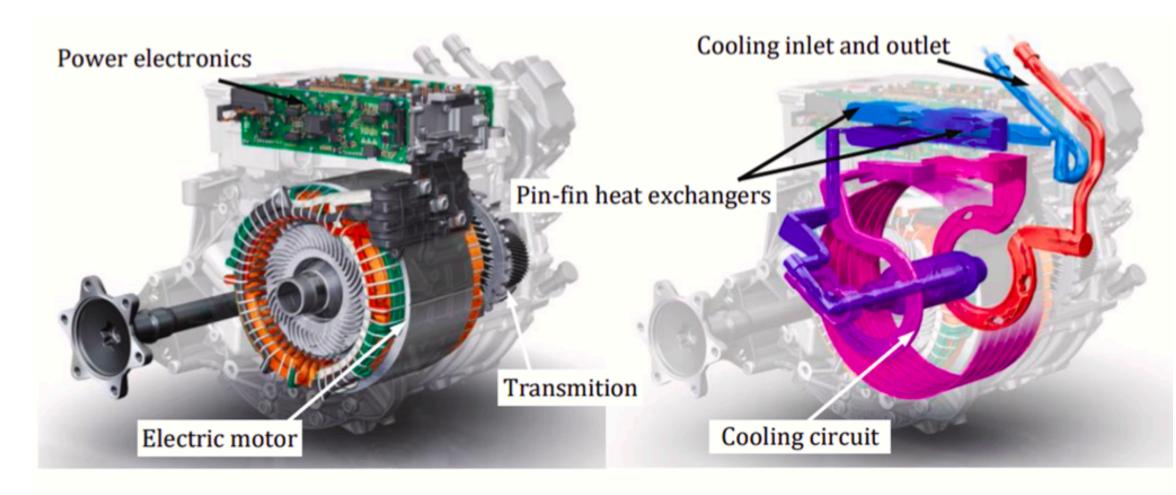- Ultra high efficiency
- Filtered voltage waveforms




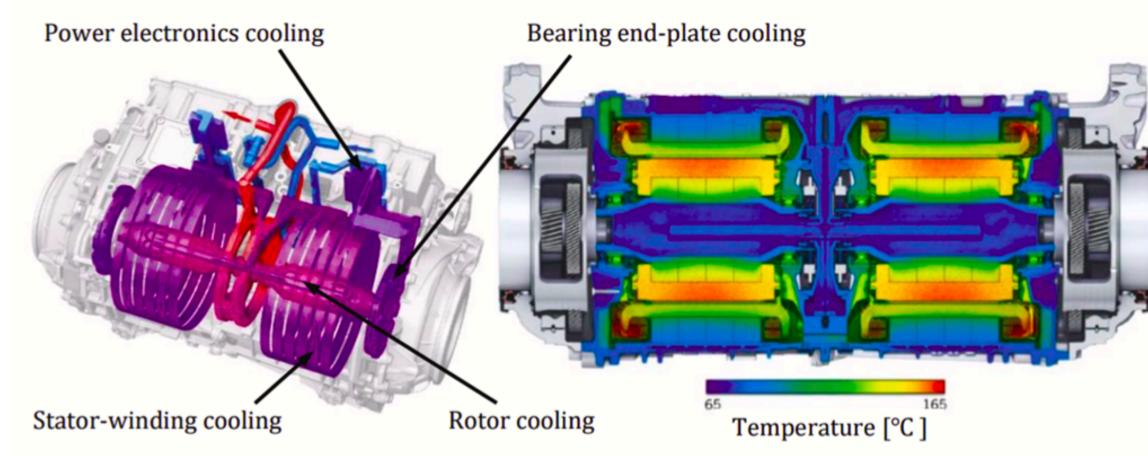



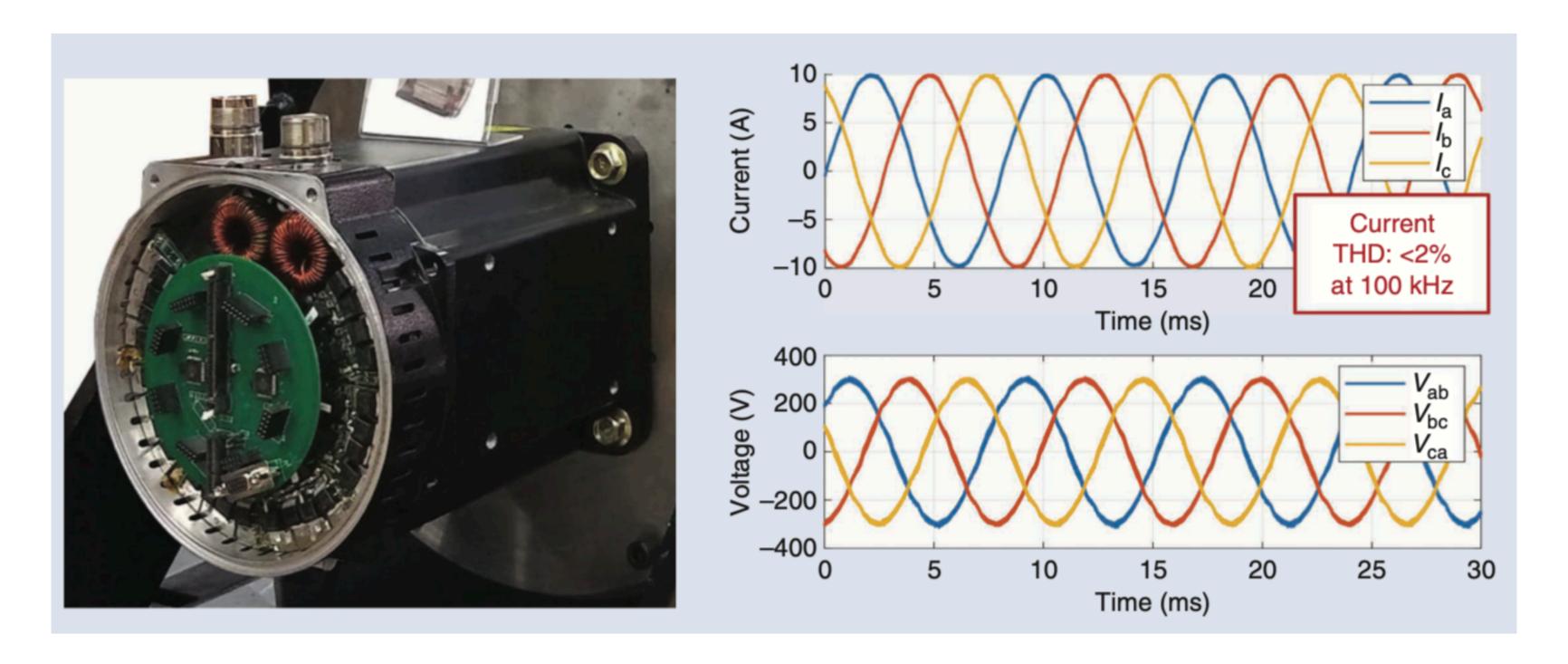
# Integrated motor drives - example based on Current Source Converters

Current DC-link Back-to-Back converters seem like an interesting solution





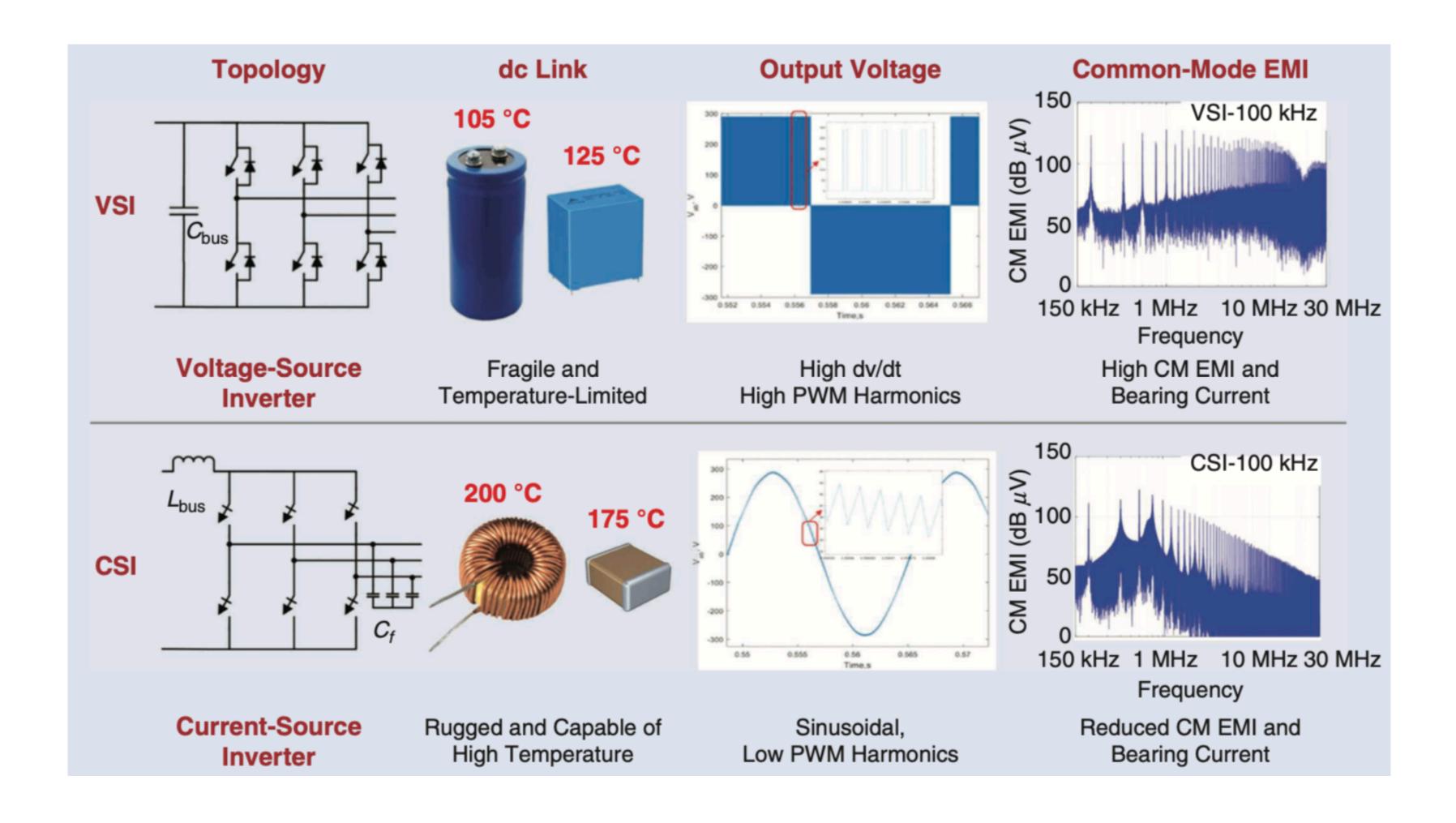
### Integrated motor drives - example based on a Current Source Converters





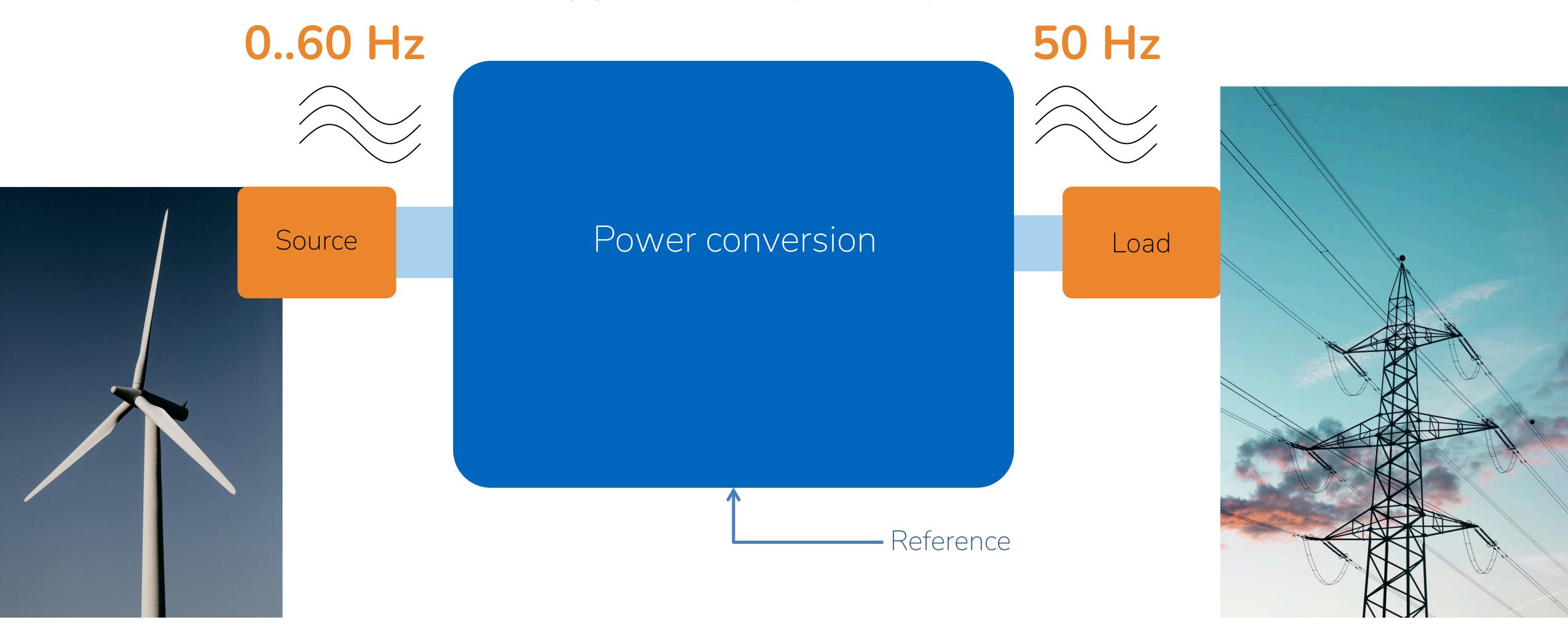
# Bidirectional motor drive applications (WECS)




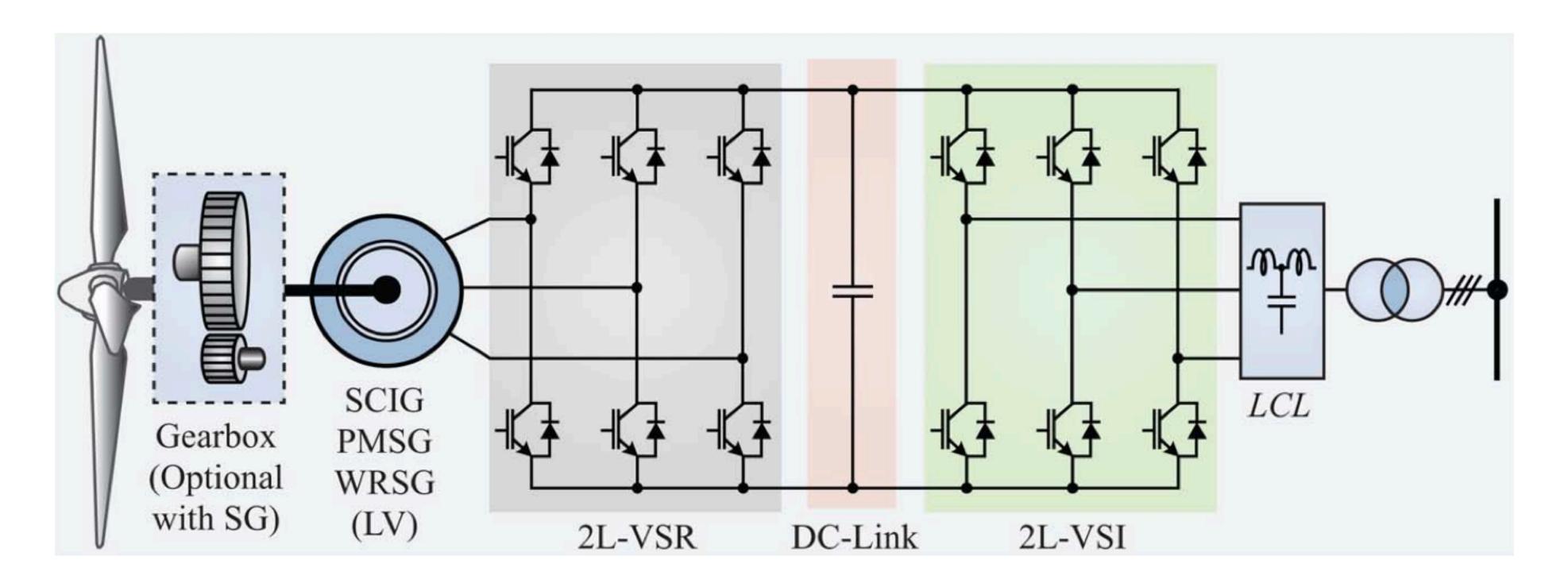
# Powertrains of Wind Energy Conversion Systems

Type 4 WECS with two-level back-to-back (B2B) voltage source converters




Mainstream commercial powertrain configuration for WECSs



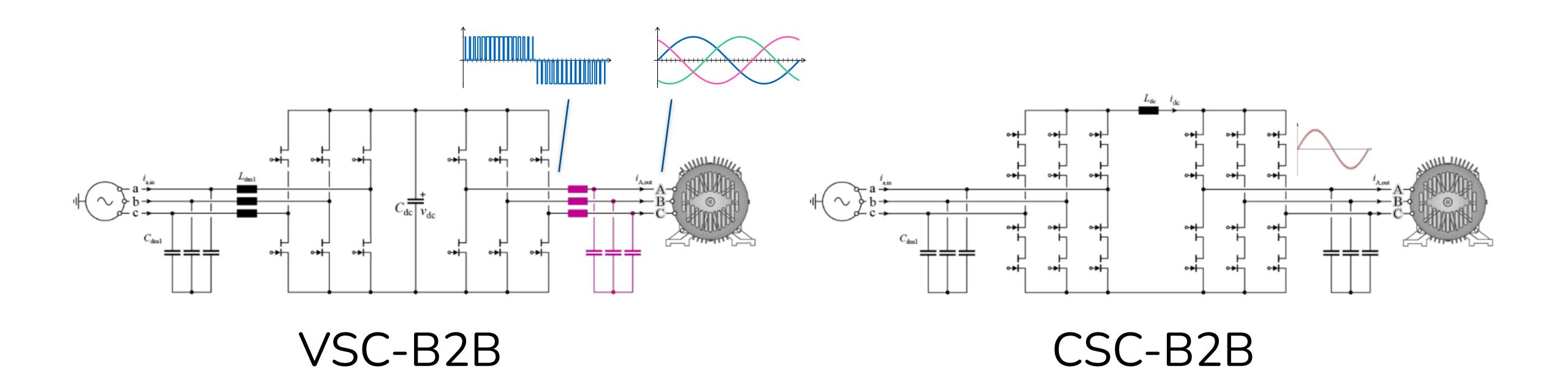Conventional power converter architectures for AC-AC conversion










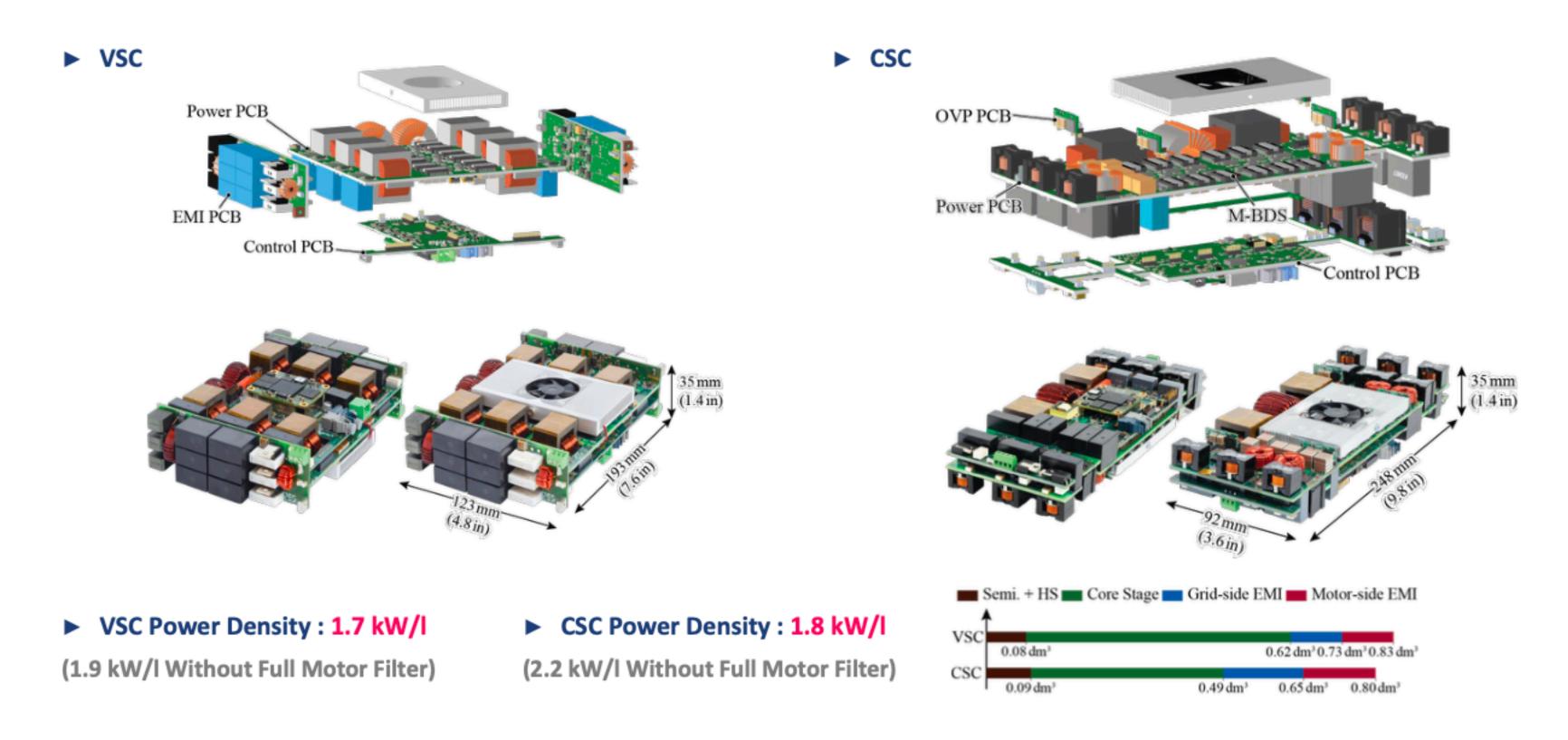
### Hardware Demonstrators (1.4kW AC-AC VSD Incl. Grid & Motor EMI)








#### Conducted EMI Measurements

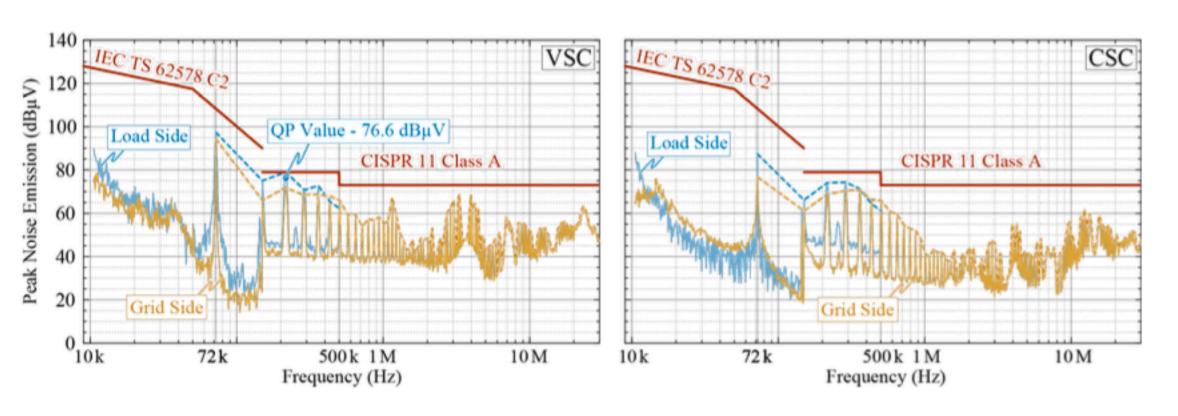

#### CSC Radiated EMI Measurement

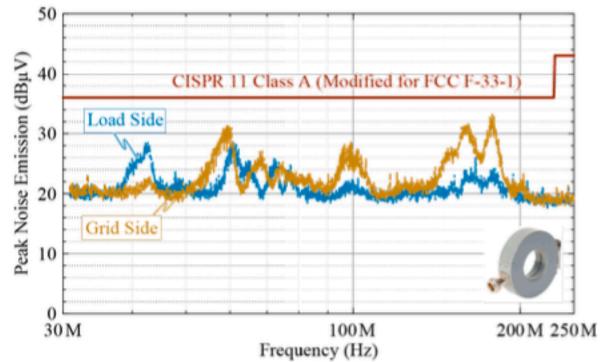


- ▶ Both VSC and CSC Prototype Satisfy Pre-Compliance Conducted EMI Limits.
- ► CSC Satisfies Pre-Compliance Radiated EMI Limits Use of Unshielded Cables Validated!
  - Measured with FCC F-33-1 Current Clamp Across All Four Wires On Grid and Motor Side






► Controllers for Both VSC and CSC Designed to Maximize v<sub>o</sub> Control Bandwidth Under Identical System Constraints

Output Voltage Loop Gain

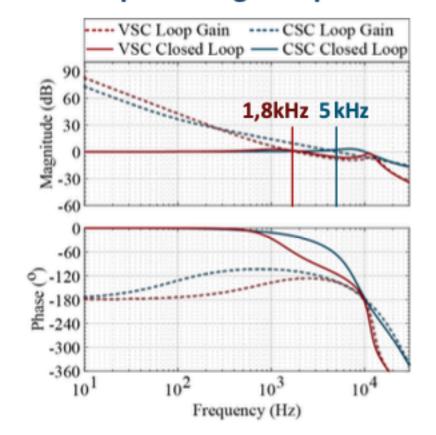


- Step Response Two Considered Cases for CSC :
  - Equal Worst Case Output Voltage Ripple as VSC (Same  $\Delta v_o \rightarrow C_{o,CSC} > C_{o,VSC}$ )
  - Equal Fundamental Frequency Capacitive Reactive Power (Same  $Q_r \rightarrow C_{o,CSC} = C_{o,VSC}$ )

#### Small-Signal

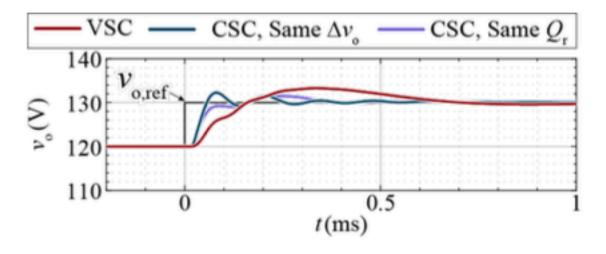

#### Large-Signal

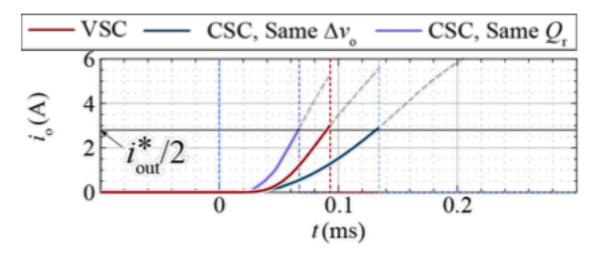

- CSC Achieves Higher Bandwidth!
- ► Small Signal: Both Cases of CSC are Faster!
- Large Signal: CSC, Same Q<sub>r</sub> is Faster / CSC, Same Δν<sub>o</sub> is Slower!





- ► CSC Offers Higher Weighted Eff. (for Characteristic Mission Profile of a Var. Centrifugal Load According to NEMA PI)
- 95.7 % for VSC vs. 96.6% for CSC → Avg. Mission Profiles Losses of CSC < VSC By Around 20 %






What options exist to reduce switching losses?




# Switching losses reduction 1 - soft-switching

#### Example 1 - ARCP inverters

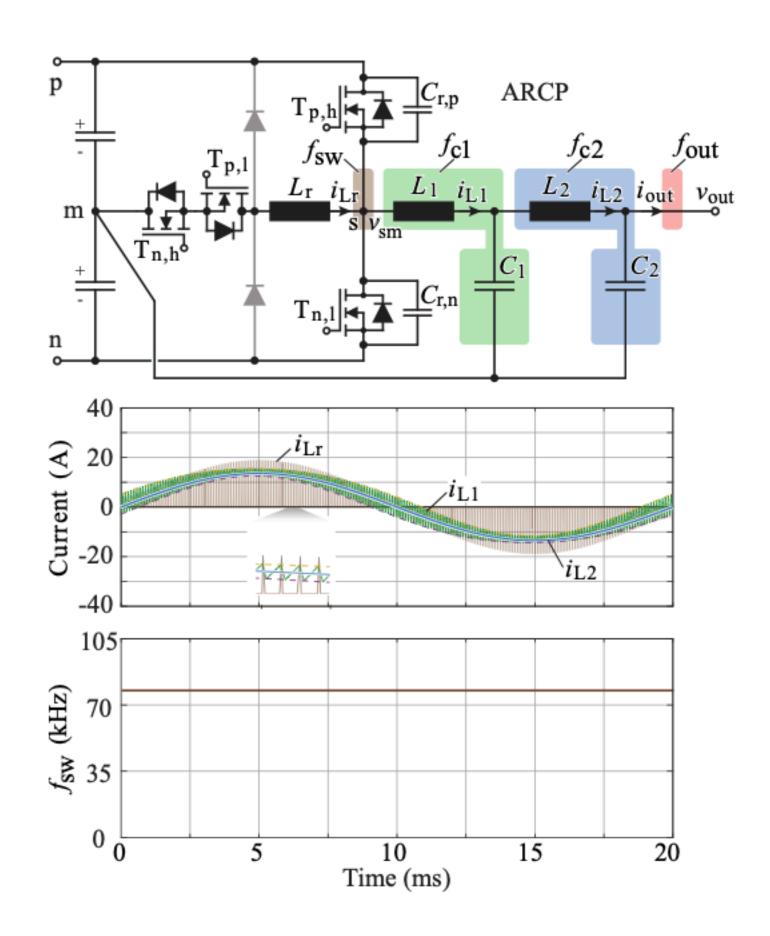

#### Example 2 - TCM modulated inverters

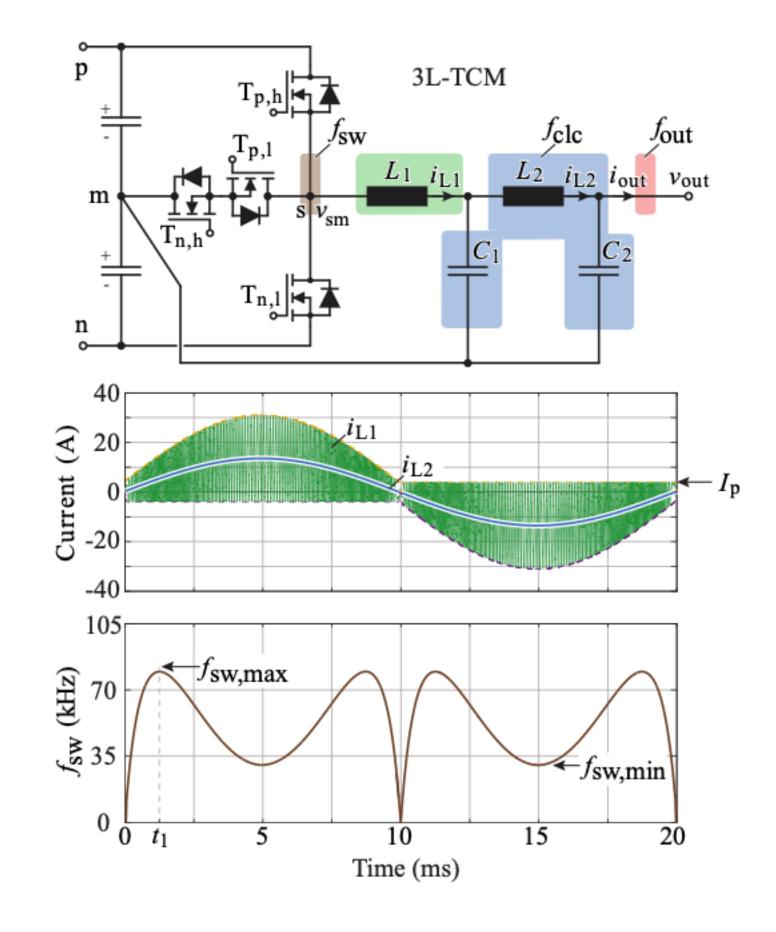


Source: C. T. Langbauer, S. Miric, M. Haider, J. Huber and J. W. Kolar, "Comparative Evaluation of ARCP and Three-Level TCM Soft-Switching Bridge-Legs for High-Frequency SiC Converter Systems," 2022 International Power Electronics Conference (IPEC-Himeji 2022- ECCE Asia), Himeji, Japan, 2022, pp. 1734-1741, doi: 10.23919/IPEC-Himeji2022-ECCE53331.2022.9806882.




# Switching losses reduction 1 - soft-switching

Example 1 - ARCP inverters

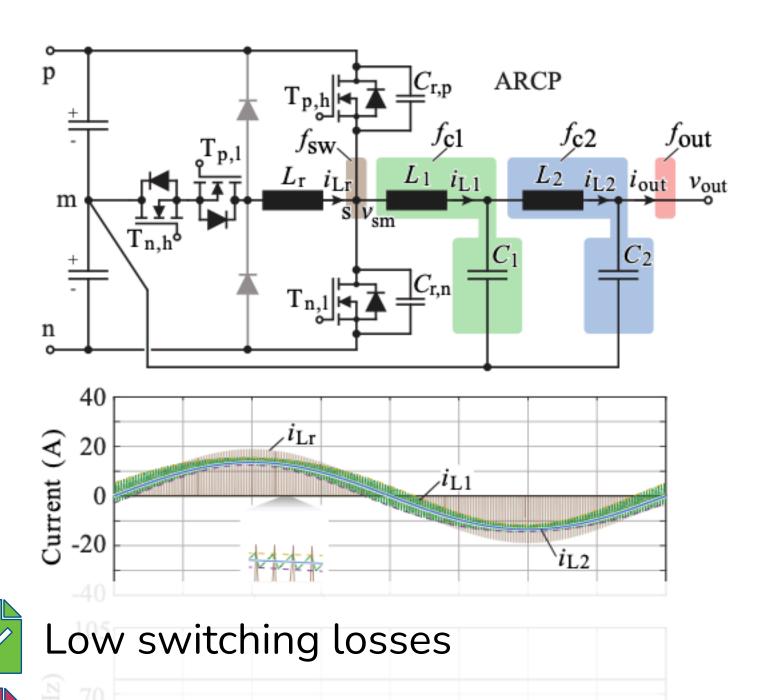

Example 2 - TCM modulated inverters

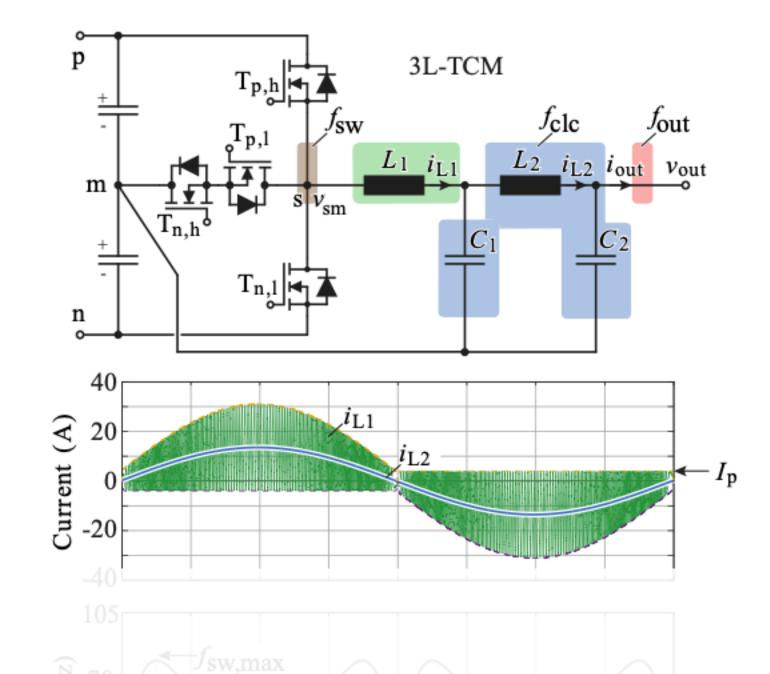


Increased conduction losses, extra components, high flux swing inductors, challenging timing or highly

variable frequency




# Switching losses reduction 2 - Diode(-like) rectififiers


#### Typical variable speed drive

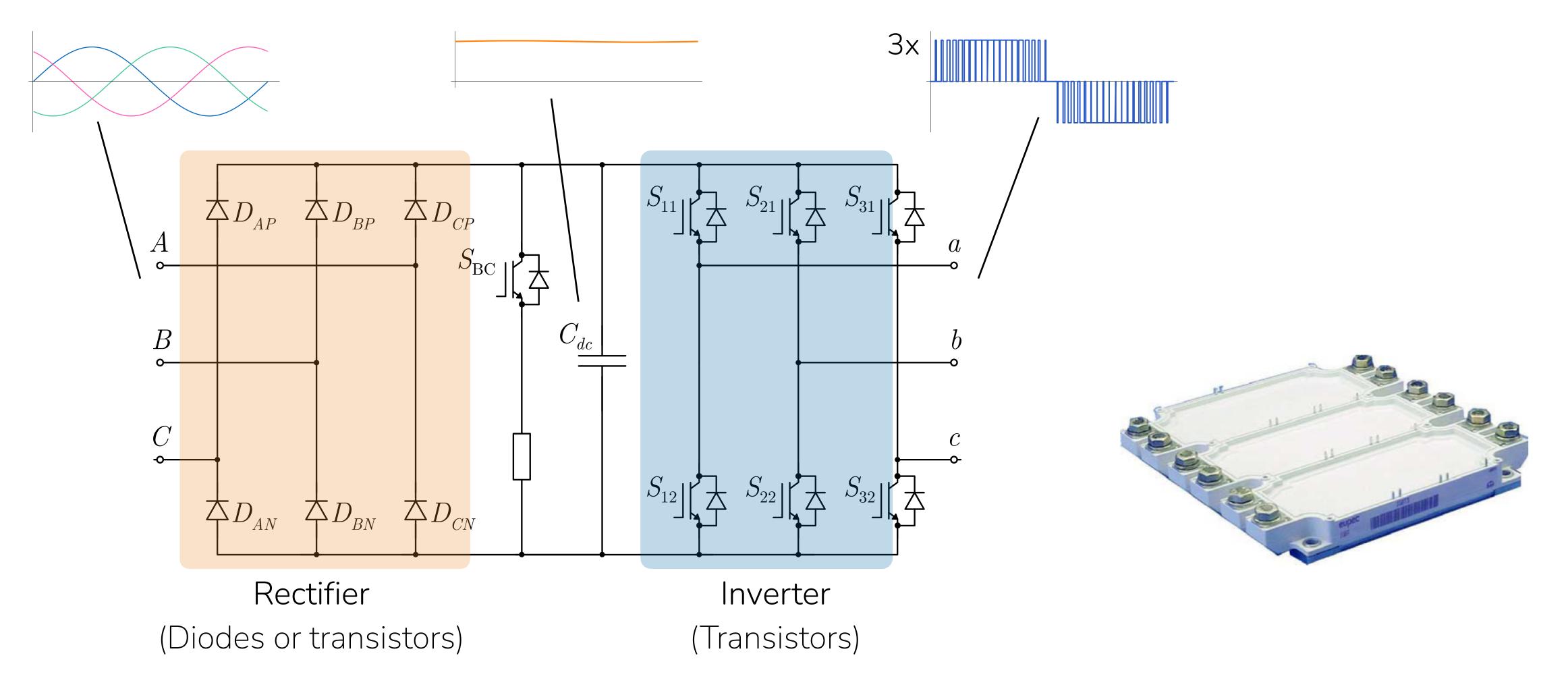


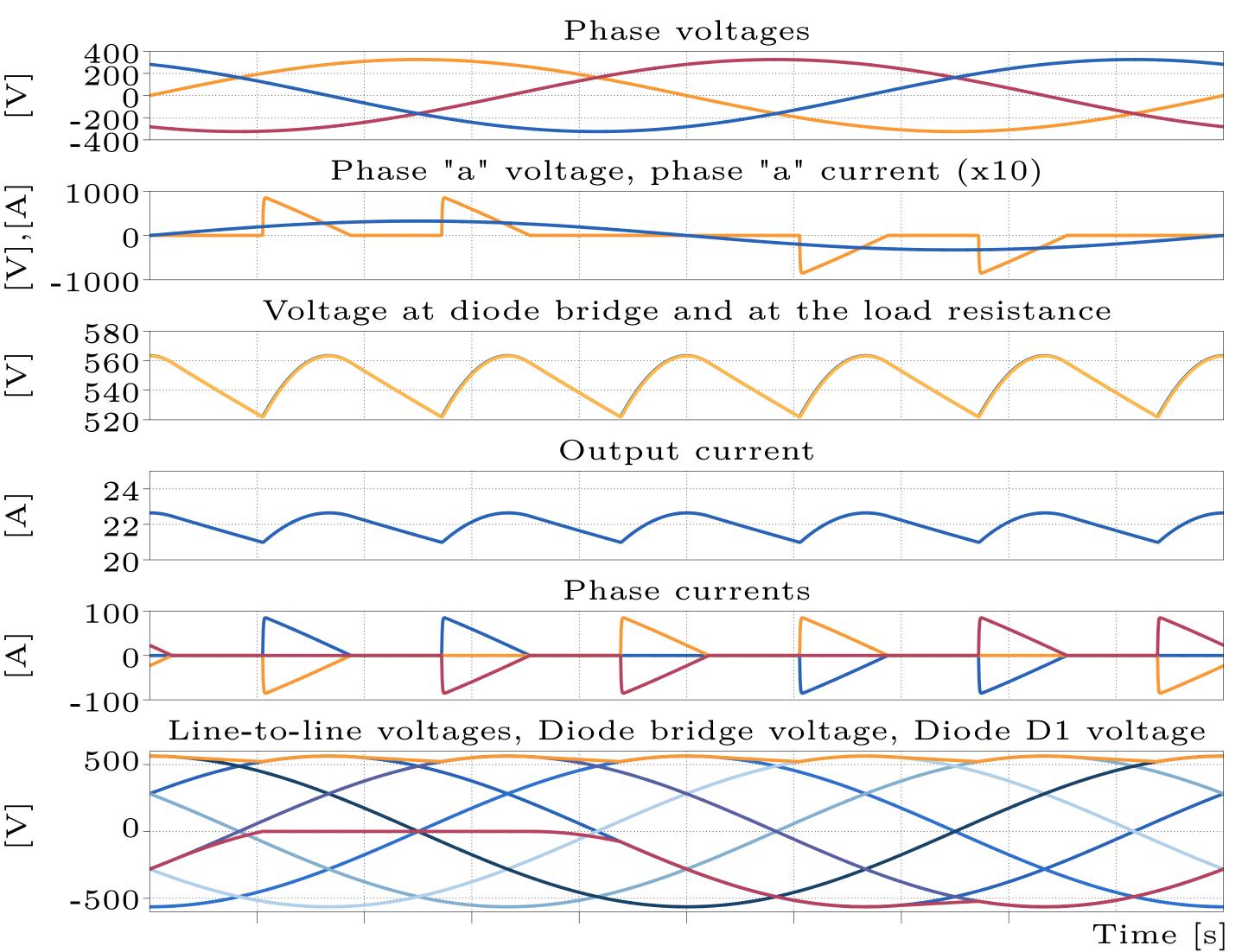
### Switching losses reduction 2 - Diode(-like) rectififiers



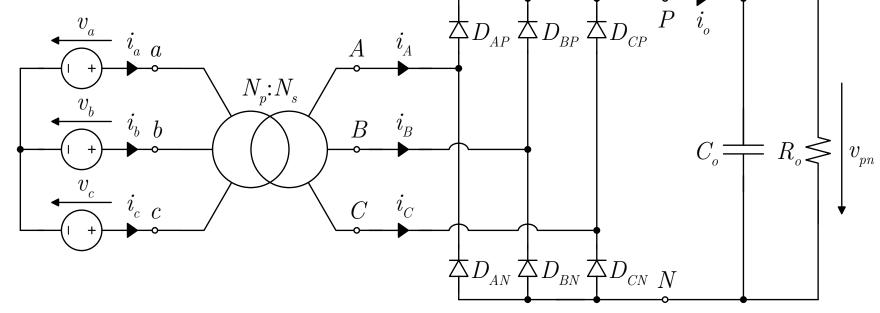



$$C_o = 1 \text{ mF}$$

$$W_{stored} = \frac{1}{2}C_o V_o^2 \approx 317 J$$


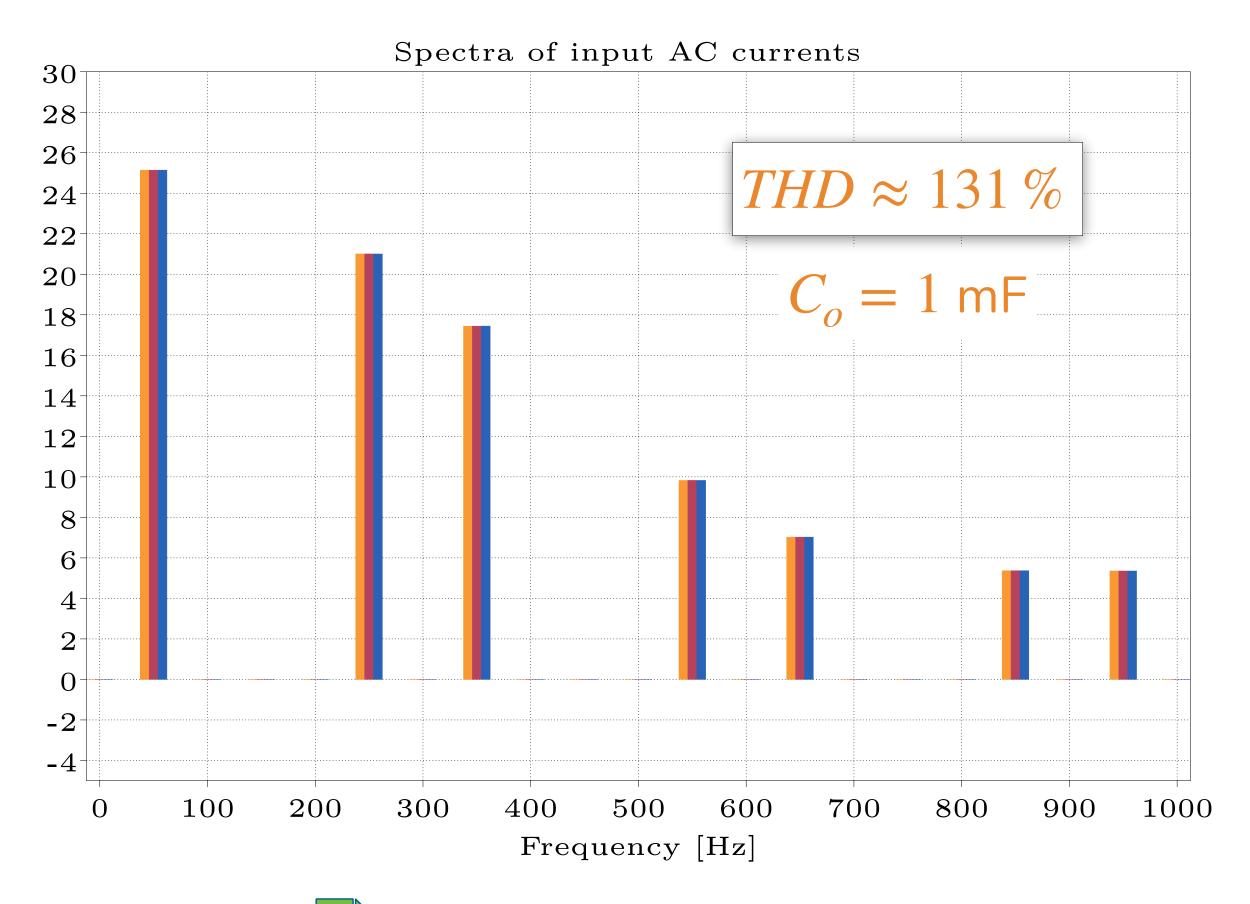
### Switching losses reduction 2 - Diode(-like) rectififiers



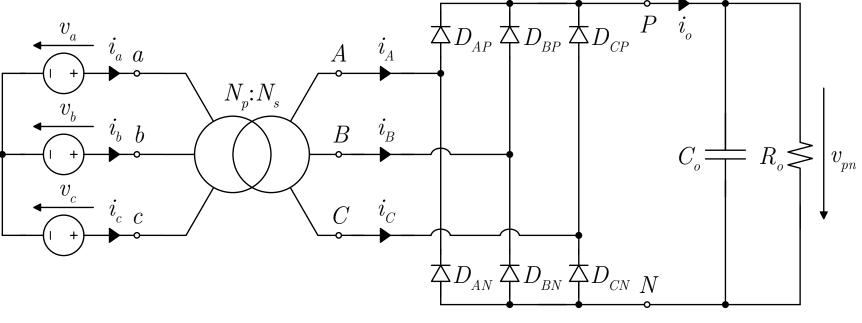



- A bidirectional solution can be achieved by replacing the diodes with transistors.
- Current distortion will not be eliminated, and large energy storage -> large dimensions




# Switching losses reduction 3 - Discontinuous modulation

#### Exemplary switching losses:

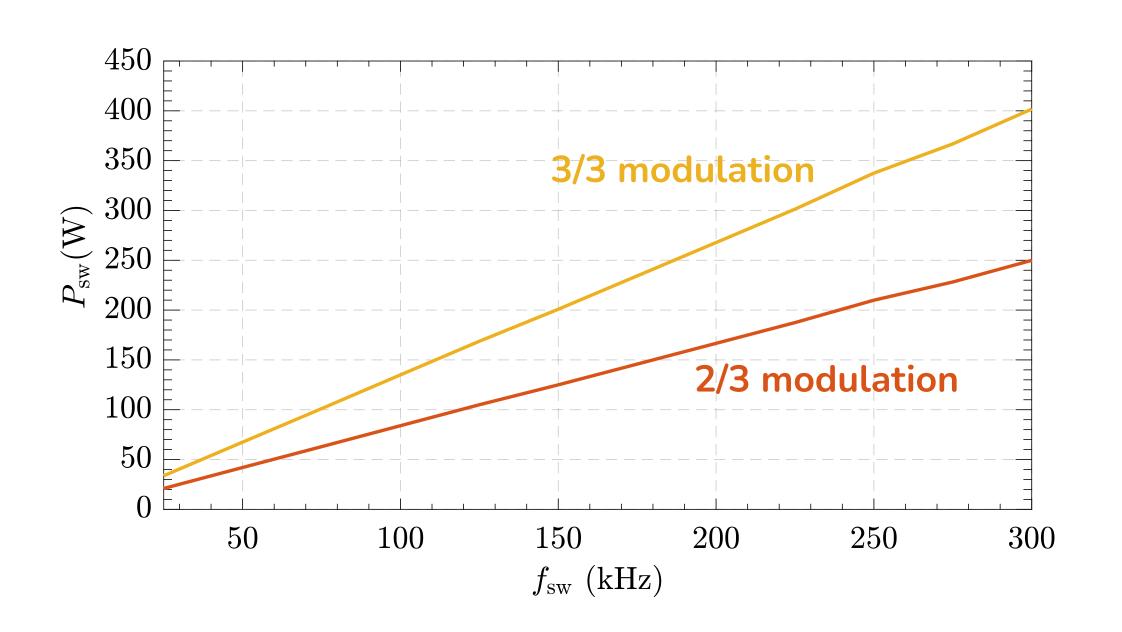

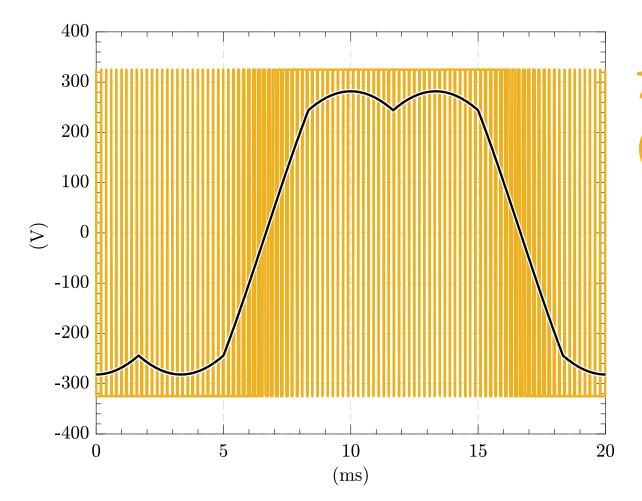

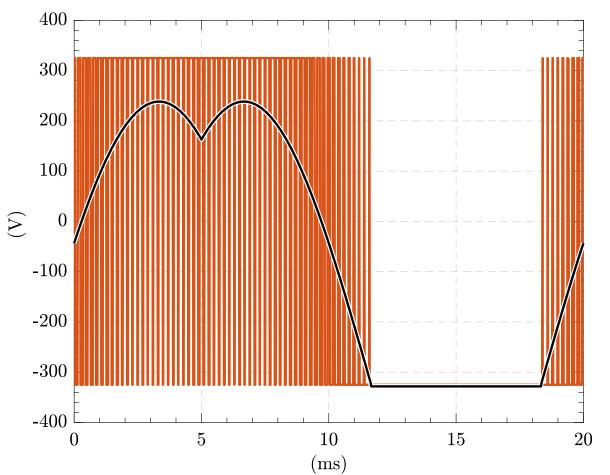7-segment space vector modulation (3/3 modulation)




Discontinuous modulation (2/3 modulation)



# Switching losses reduction 4 - synergetic control/modulation

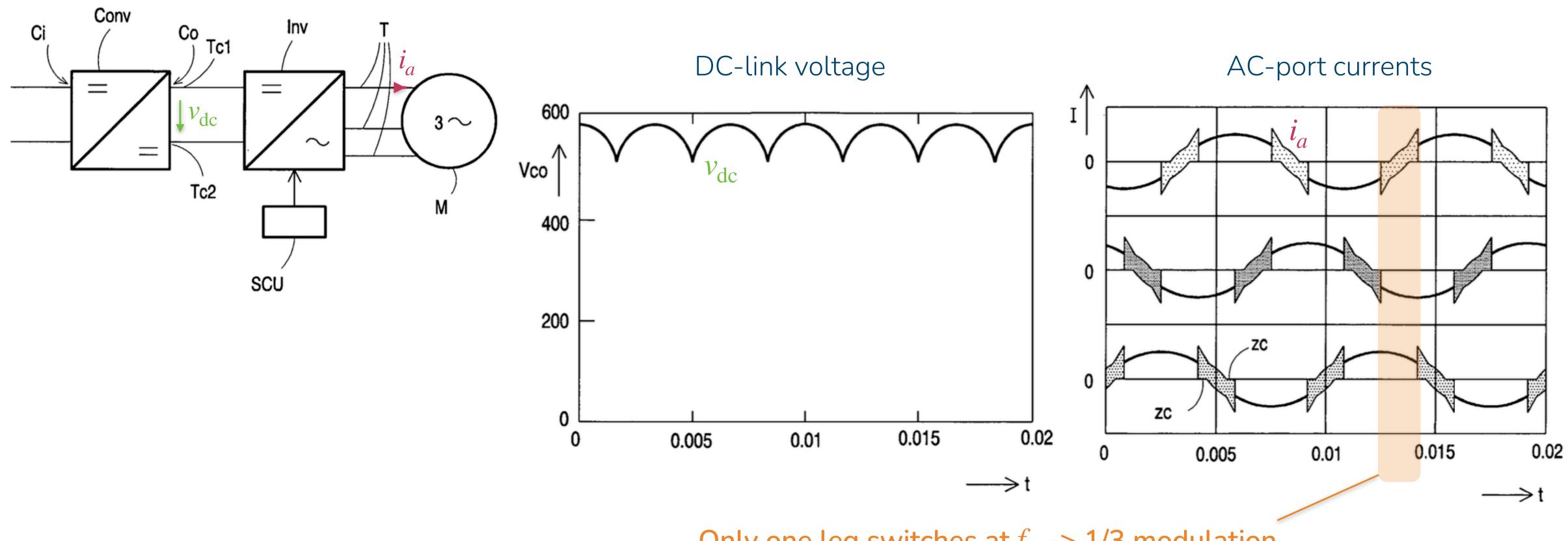Example - Two-stage DC-DC-AC converter with 1/3 modulation at the VSI stage




Only one leg switches at  $f_s \rightarrow 1/3$  modulation



# Switching losses reduction 4 - synergetic control

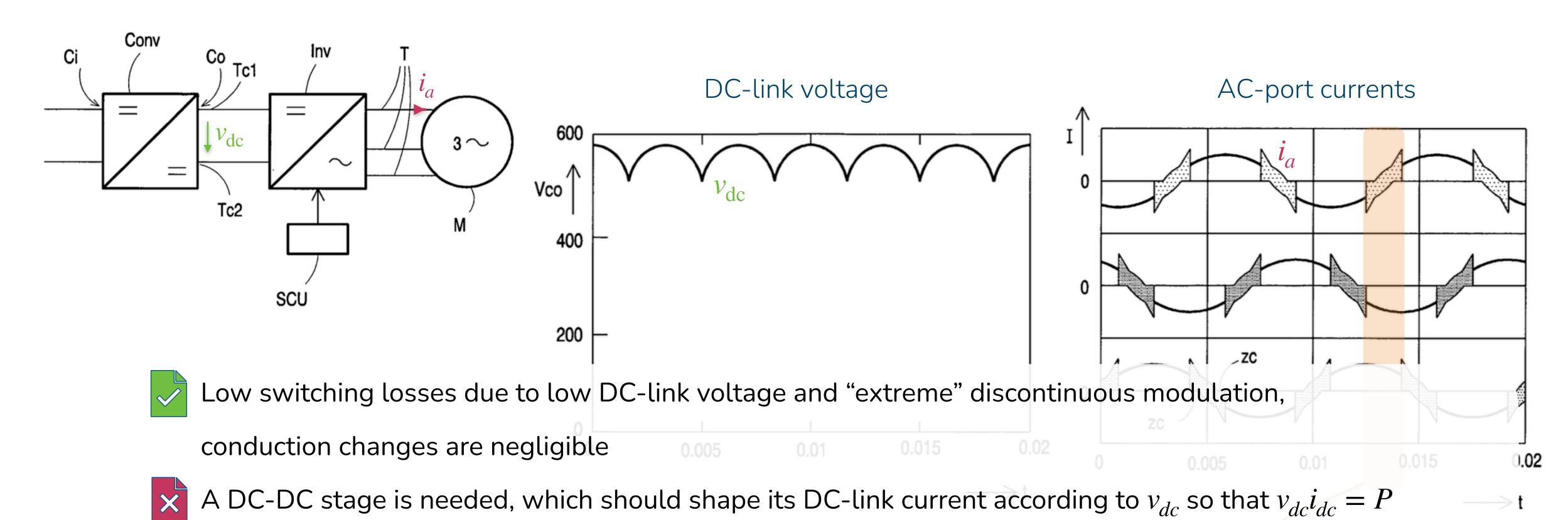Example - Two-stage DC-DC-AC converter with 1/3 modulation at the VSI stage



Source: Philips Intellectual Property & Standards GMBH, "3-phase solar converter circuit and method", Patent number WO2006011071A2, Feb. 2006.

-> not optimal DC-DC operation




New concept 1 - VSC+BC+CSC



#### VSC + Bidirectional buck converter + CSC


Topology

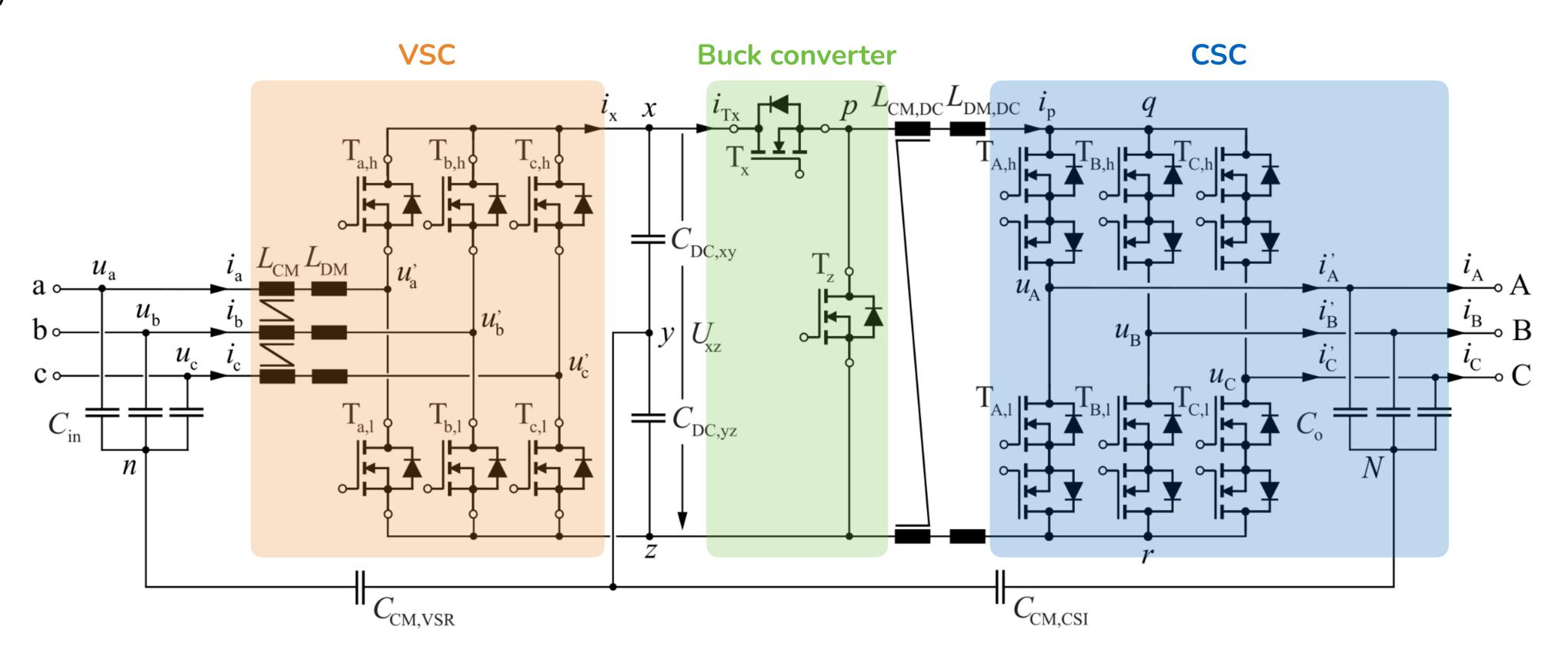



#### VSC + Bidirectional buck converter + CSC

Topology

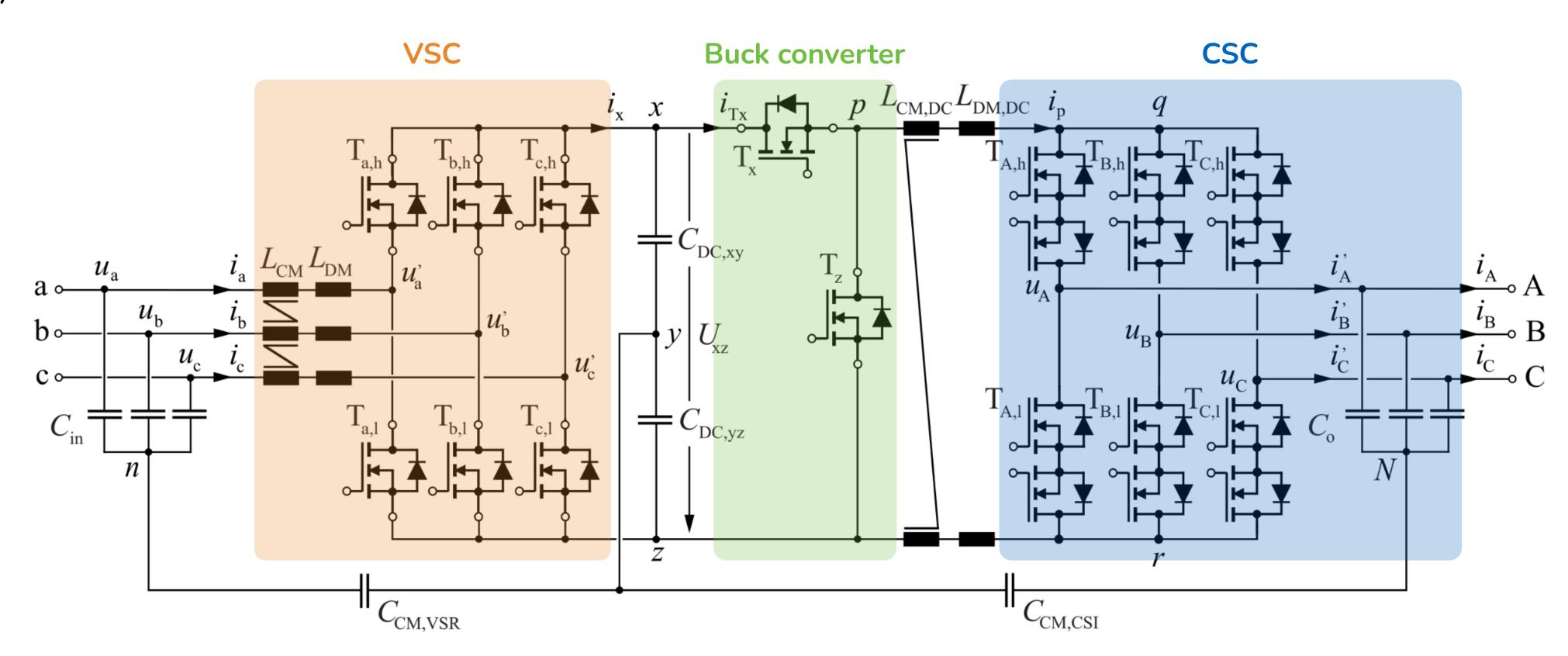

The intermediate DC-DC converter enables synergies among all converter stages!



Grid side voltages,

$$u_j = \hat{U}_{\rm m} \sin(\omega_{\rm m} t - \theta_j)$$
, with  $j = a, b, c$   
 $\theta_{\rm a} = 0$ ,  $\theta_{\rm b} = \frac{2\pi}{3}$ ,  $\theta_{\rm c} = -\frac{2\pi}{3}$ ,



Motor side currents,

$$i_{\rm j} = \hat{I}_{\rm o,pk} \sin(\omega_{\rm o}t - \phi - \theta_{\rm j}), \text{ with j} = A, B, C$$
  
 $\theta_{\rm A} = 0, \, \theta_{\rm B} = \frac{2\pi}{3}, \, \theta_{\rm C} = -\frac{2\pi}{3},$ 

Organizing the voltages according to their amplitudes:

$$u_{\text{max}} = \max(u_{\text{a}}, u_{\text{b}}, u_{\text{c}})$$
 $u_{\text{min}} = \min(u_{\text{a}}, u_{\text{b}}, u_{\text{c}})$ 
 $u_{\text{mid}} = -(u_{\text{VSR,max}} + u_{\text{VSR,min}})$ 

For 1/3 modulation, the rectifier DC-link voltage has to follow,  $U_{
m xz}=U_{13}=u_{
m max}-u_{
m min}$ 

$$U_{xz} = U_{13} = u_{\text{max}} - u_{\text{min}}$$

For the CSS, we want to operate it with just two phase legs switching at any given switching period. Thus, the CSC DC-link current has to follow

$$i_{\rm p} = i_{23} = \max(|i_{\rm A}|, |i_{\rm B}|, |i_{\rm C}|)$$



Rewriting, 
$$U_{xz}=U_{13}=u_{\max}-u_{\min}$$
 and  $i_{\mathrm{p}}=i_{23}=\max(|i_{\mathrm{A}}|,|i_{\mathrm{B}}|,|i_{\mathrm{C}}|)$ 

Now, we need modulation/reference signals that would generate proper voltages and currents in both AC ports. Thus, the modulation signals should be,

**VSC** 

$$d_{\text{max}} = 2U_{\text{xz}}^{-1}(u_{\text{max}} + u_{\text{yn}})$$
 $d_{\text{mid}} = 2U_{\text{xz}}^{-1}(u_{\text{mid}} + u_{\text{yn}})$ 
 $d_{\text{min}} = 2U_{\text{xz}}^{-1}(u_{\text{min}} + u_{\text{yn}})$ 

with,

$$u_{\rm yn} = -(u_{\rm max} + u_{\rm min})/2.$$

**CSC** (for 
$$-\pi/6 \le \theta \le \pi/6$$
)

$$\begin{split} d_{\rm [AC]} &= 0.5 \, m_{\rm CSI} \cos \theta + 0.5 \sqrt{3} \, m_{\rm CSI} \sin \theta \\ d_{\rm [AB]} &= 0.5 \, m_{\rm CSI} \cos \theta - 0.5 \sqrt{3} \, m_{\rm CSI} \sin \theta \\ d_{\rm [zero]} &= 1 - d_{\rm [AC]} - d_{\rm [AB]} = 0 \end{split}$$



Rewriting, 
$$U_{xz}=U_{13}=u_{\max}-u_{\min}$$
 and  $i_{\mathrm{p}}=i_{23}=\max(|i_{\mathrm{A}}|,|i_{\mathrm{B}}|,|i_{\mathrm{C}}|)$ 

Now, we need modulation/reference signals that would generate proper voltages and currents in both AC ports. Thus, the modulation signals should be,

$$d_{\text{max}} = 2U_{\text{xz}}^{-1}(u_{\text{max}} + u_{\text{yn}})$$
  
 $d_{\text{mid}} = 2U_{\text{xz}}^{-1}(u_{\text{mid}} + u_{\text{yn}})$   
 $d_{\text{min}} = 2U_{\text{xz}}^{-1}(u_{\text{min}} + u_{\text{yn}})$ 

$$u_{\rm yn} = -(u_{\rm max} + u_{\rm min})/2.$$

**CSC** (for 
$$-\pi/6 \le \theta \le \pi/6$$
)

$$d_{
m [AC]} = 0.5 \, m_{
m CSI} \cos \theta + 0.5 \sqrt{3} \, m_{
m CSI} \sin \theta$$
  $d_{
m [AB]} = 0.5 \, m_{
m CSI} \cos \theta - 0.5 \sqrt{3} \, m_{
m CSI} \sin \theta$   $d_{
m [zero]} = 1 - d_{
m [AC]} - d_{
m [AB]} = 0$ 


The DC-DC converter must adapt its voltage-port current and current-port voltage so that power is constant.

Thus,

$$d_{
m DC/DC} = rac{u_{
m qr,LF}}{U_{
m xz}} = rac{i_{
m x,LF}}{i_{
m p}}$$
 Buck converter




# VSC+BC+CSC operation principle

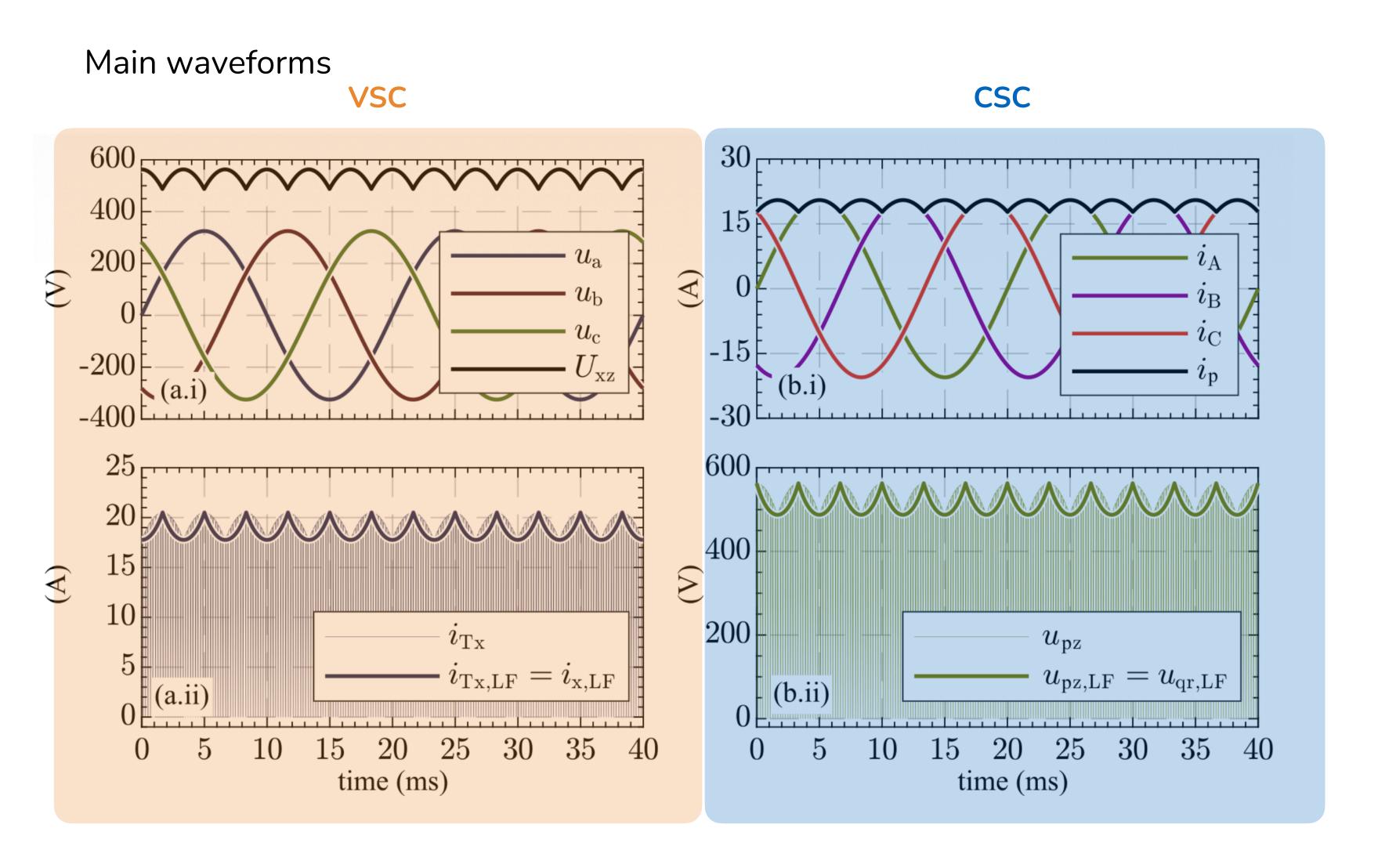



# VSC+BC+CSC operation principle

#### Main waveforms

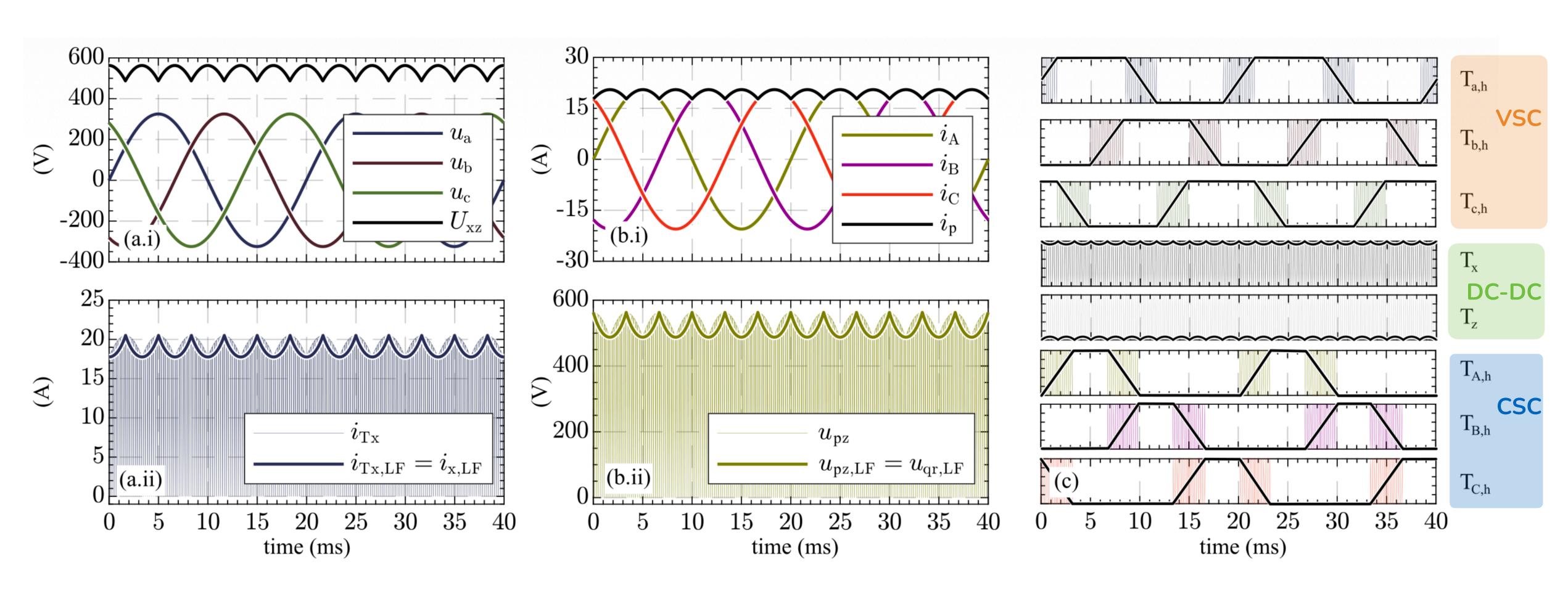



### Operation limits

Power conservation should be observed:  $P=U_{
m xz}\,i_{
m x,LF}=u_{
m qr,LF}\,i_{
m p}$ 

The other physical restrictions are:  $U_{
m xz} \geq u_{
m qr,LF}$  ,  $i_{
m x,LF} \leq i_{
m p}$  ,  $d_{
m DC/DC} \leq 1$ 

Thus, the following relation must hold 
$$\frac{P}{U_{\rm xz}\,i_{\rm p}} = \frac{P}{U_{13}\,i_{23}} = \frac{(3/2)\,\hat{U}_{\rm o,pk}\,\hat{I}_{\rm o,pk}\,{\rm PF}}{U_{13}\,i_{23}} \leq 1 \qquad \hat{U}_{\rm o,pk,max} = \frac{\sqrt{3}\,\hat{U}_{\rm m,pk}}{2\,{\rm PF}} = \frac{1}{2\,{\rm PF}} = \frac{1$$

$$\hat{U}_{
m o,pk,max} = rac{\sqrt{3}\,\hat{U}_{
m m,pk}}{2\,{
m PF}}$$

Maximum output voltage



# Operation limits

Power conservation should be observed:  $P = U_{xz} i_{x,LF} = u_{qr,LF} i_{p}$ 

$$P = U_{\rm xz} i_{\rm x.LF} = u_{\rm cr.LF} i_{\rm r}$$

The other physical restrictions are:  $U_{
m xz} \geq u_{
m qr,LF}$  ,  $i_{
m x,LF} \leq i_{
m p}$  ,  $d_{
m DC/DC} \leq 1$ 


$$U_{\mathrm{xz}} \geq u_{\mathrm{qr,LF}}$$
 ,

$$i_{
m x, LF} \, \leq \, i_{
m p}$$
 ,


$$d_{\mathrm{DC/DC}} \leq 1$$


Thus, the following relation must hold
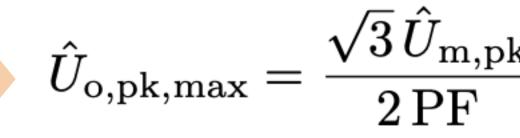
$$\frac{P}{U_{\rm xz} i_{\rm p}} = \frac{P}{U_{13} i_{23}} = \frac{(3/2) \, \hat{U}_{\rm o,pk} \, \hat{I}_{\rm o,pk} \, PF}{U_{13} i_{23}} \le 1 \qquad \hat{U}_{\rm o,pk,max} = \frac{\sqrt{3} \, \hat{U}_{\rm m,pk}}{2 \, PF}$$




Maximum output voltage

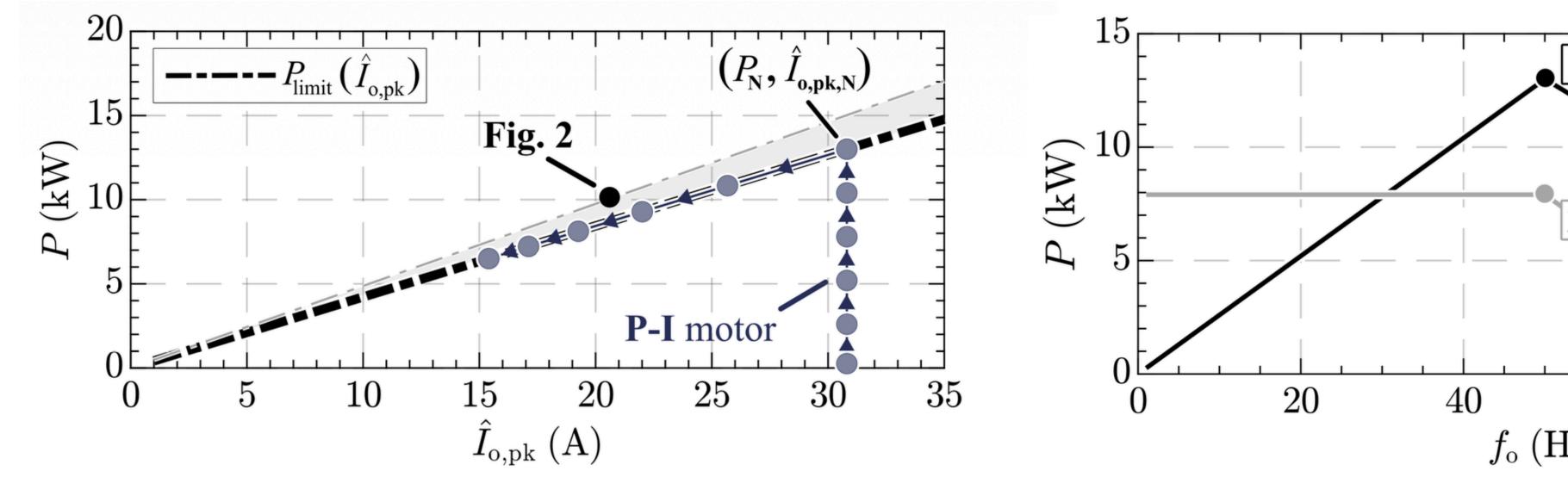

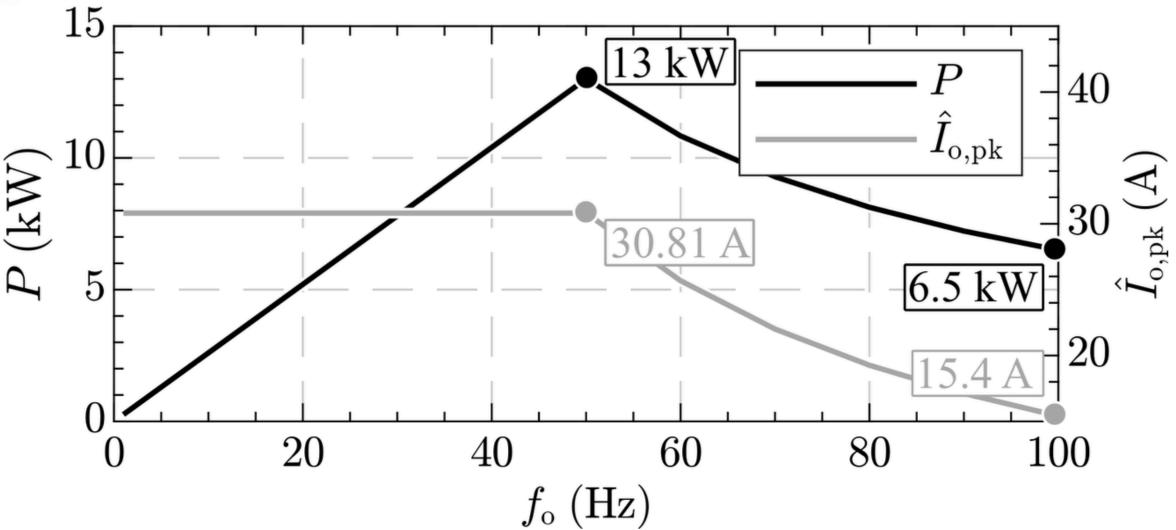




# Control principle

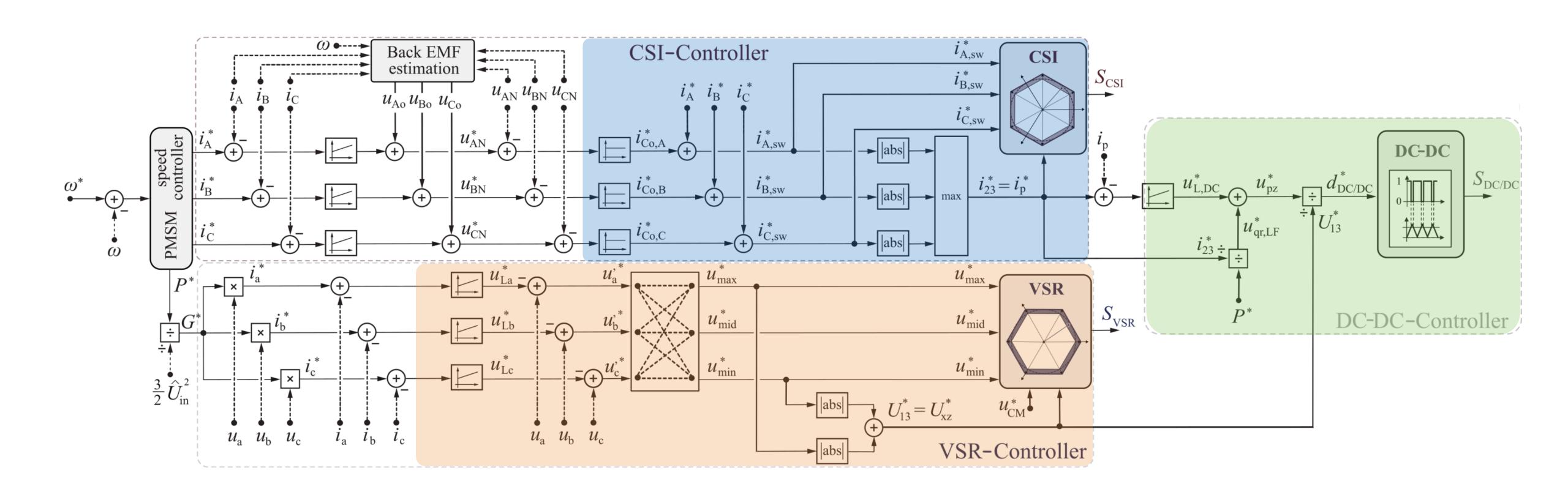

# Accelerating a motor

Description	Value
Nominal power	13 kW
Nominal peak current	30.81 A
Nominal electrical frequency	50 Hz
Electrical frequency range	[0, 100] Hz
Nominal RMS phase voltage	200 V
Nominal Power Factor	1.0

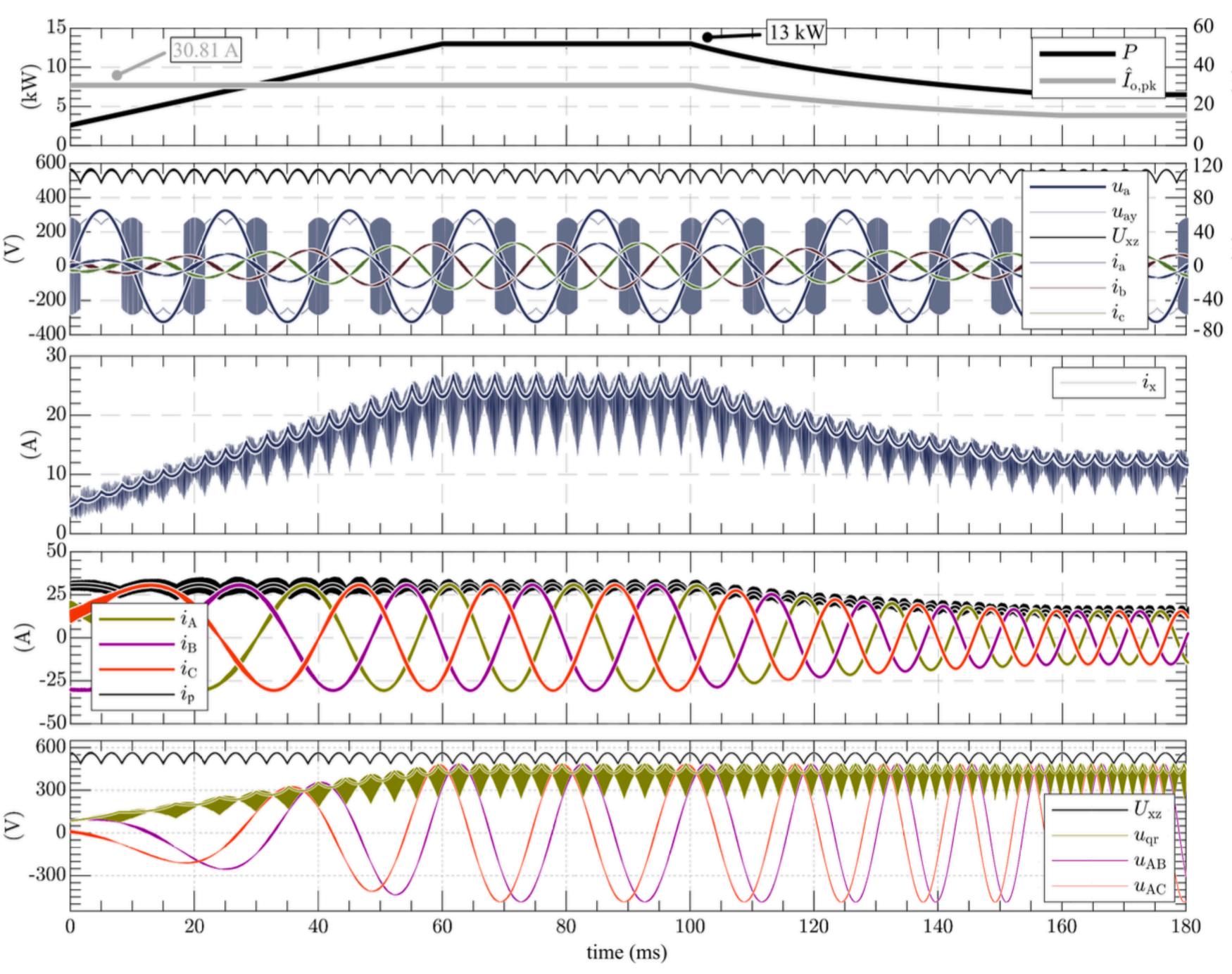



# Comparison with VSC-B2B


#### Load specifications:

Description	Value
Nominal power	13 kW
Nominal peak current	30.81 A
Nominal electrical frequency	50 Hz
Electrical frequency range	[0, 100] Hz
Nominal RMS phase voltage	200 V
Nominal Power Factor	1.0

#### Chosen design parameters:


	Description	Value
$f_{ m sw}$	Switching freq.	100 kHz
$T_{ m VSR} \ T_{ m DC/DC} \ T_{ m CSI}$	VSR semiconductor DC/DC semiconductor CSI semiconductor	SCT012W90G3AG (900 V, 12 mΩ) C3M0030090K (900 V, 30 mΩ) C3M0010090K (900 V, 10 mΩ)
$L_{ m DM} \ L_{ m CM} \ L_{ m DM,DC} \ L_{ m CM,DC}$	VSR DM inductor VSR CM inductor DC DM inductor DC CM inductor	176 μH (2×N87 E65/32/27, 14 turns) 1.2 mH (VAC 40/25/15, 3×8 turns) 75.7 μH (2×N87 E30/25/16, 12 turns) 1.5 mH (VAC 40/25/15, 2×9 turns)
$C_{ m in}$ $C_{ m DC,xy-yz}$ $C_{ m o}$ $C_{ m CM,VSR}$ $C_{ m CM,CSI}$	VSR DM capacitor DC-link capacitor CSI DM capacitor VSR CM capacitor CSI CM capacitor	2.0 μF 9.0 μF 5.3 μF 63 nF 76 nF
$ ho \eta$	Volumetric Power Density Efficiency	$7.68 \text{ kW/dm}^3$ $98.80 \%$

Efficiency vs. power density comparison:

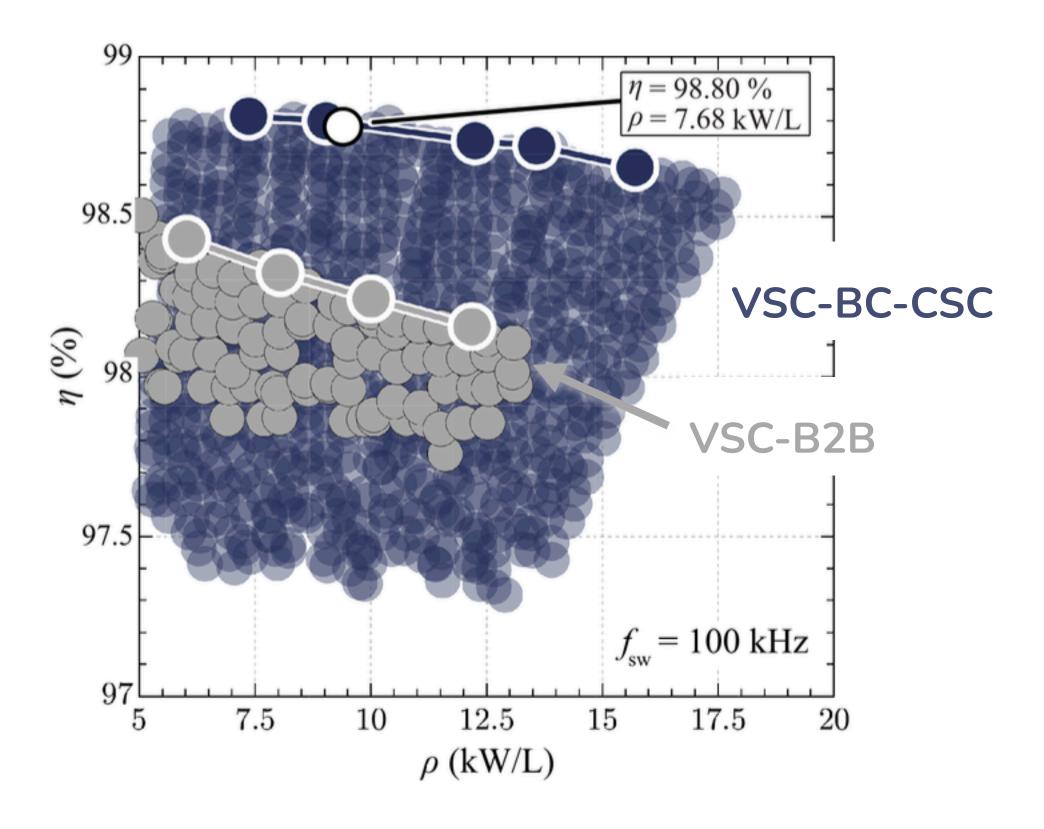


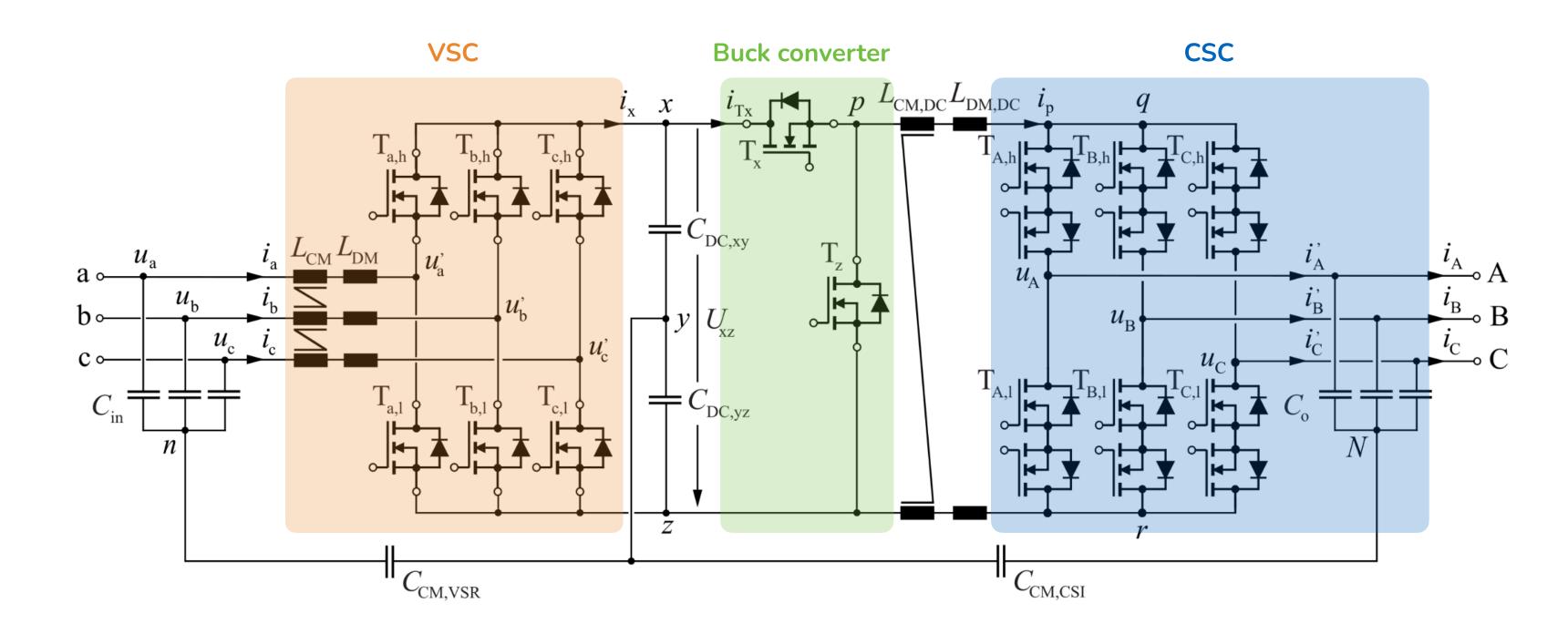
# Critical evaluation of the VSC-BC-CSC concept




- Motor is fed with near sinusoidal voltages, switching losses are low, and conduction losses are not much altered
- Extra components when compared with VSC-B2B, CSC requires many gate drivers, did not achieve 99%



New concept 2 - Three-leg operation of VSC-B2B



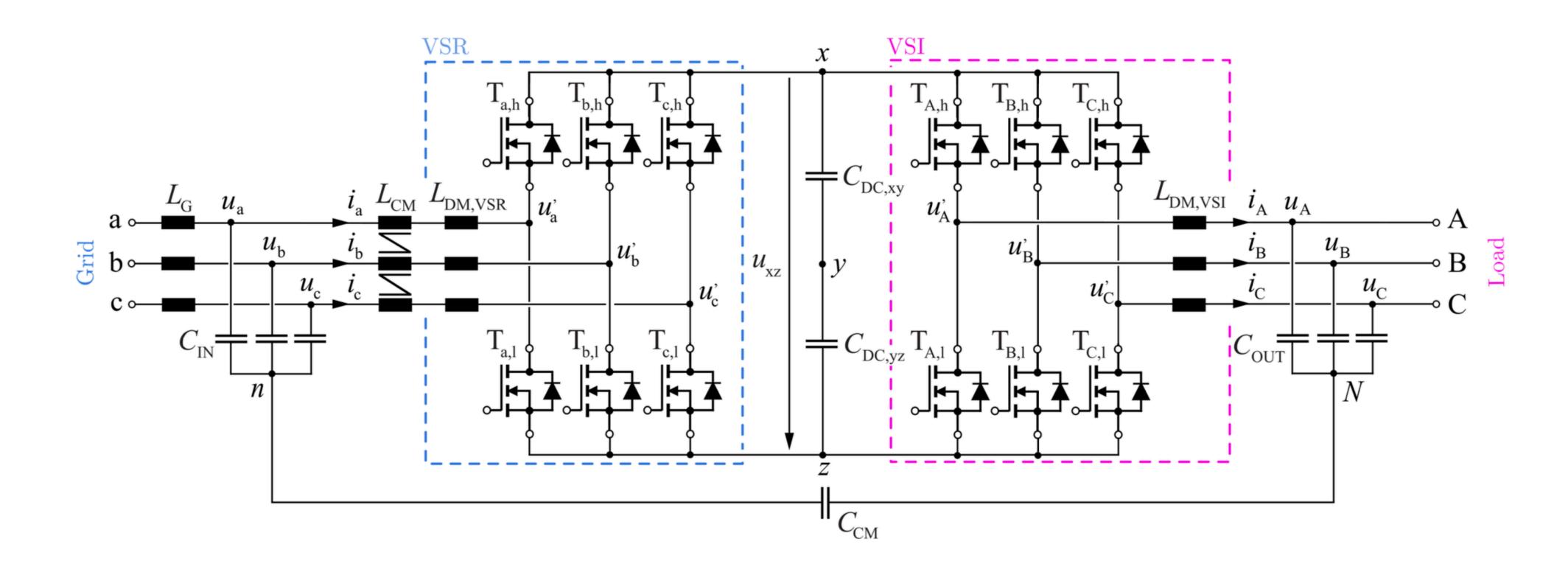
#### The voltage source back-to-back AC-(DC)-AC converter



- Industry standard for bidirectional AC-AC power conversion.
- Switching losses limit the achievable maximum efficiency and, therefore, the compactness of the filters.


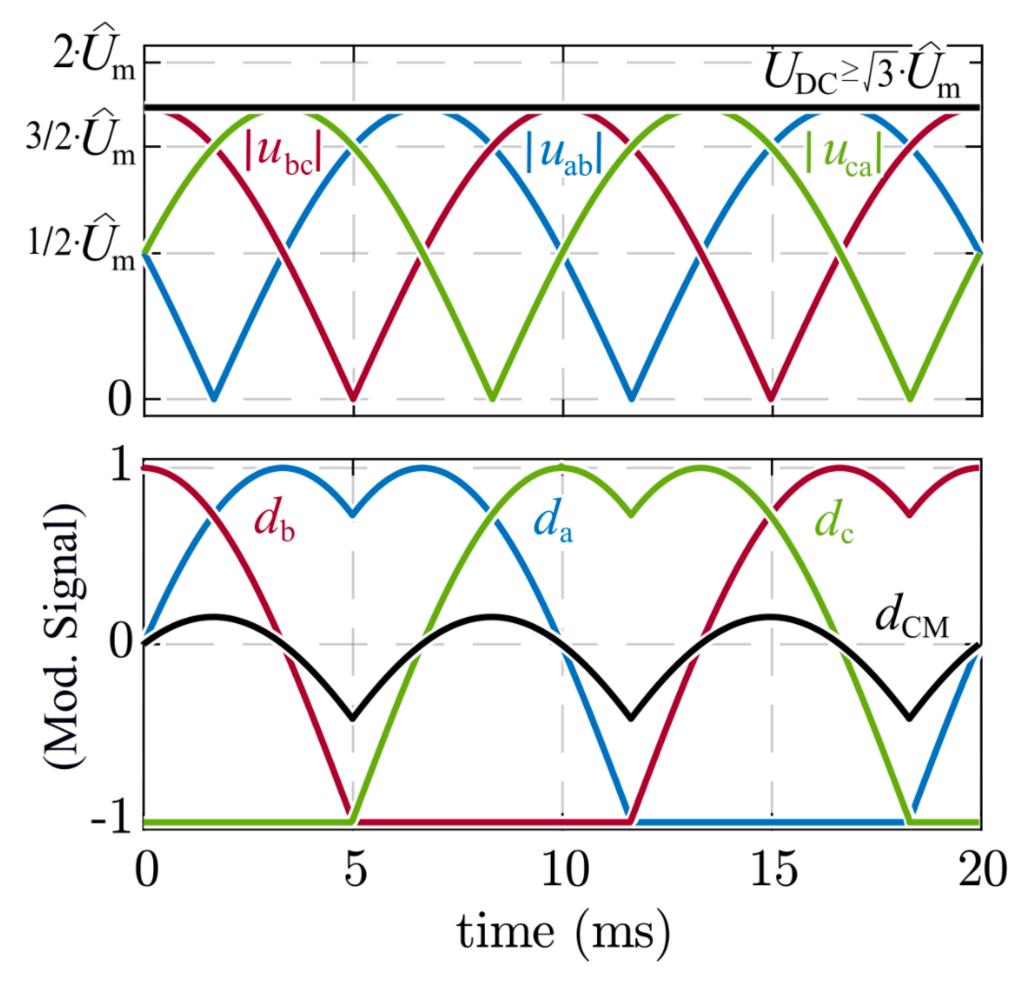
#### Principles of discontinuous modulation for a VSC




Line voltages define the minimum DC-link voltage

Modulation signals must guarantee that the output voltages are as expected, i.e.,  $v_{\text{out},j} = (d_j - d_{\text{CM}}) \ U_{\text{DC}}$  with  $d_j \in [0,1]$ 



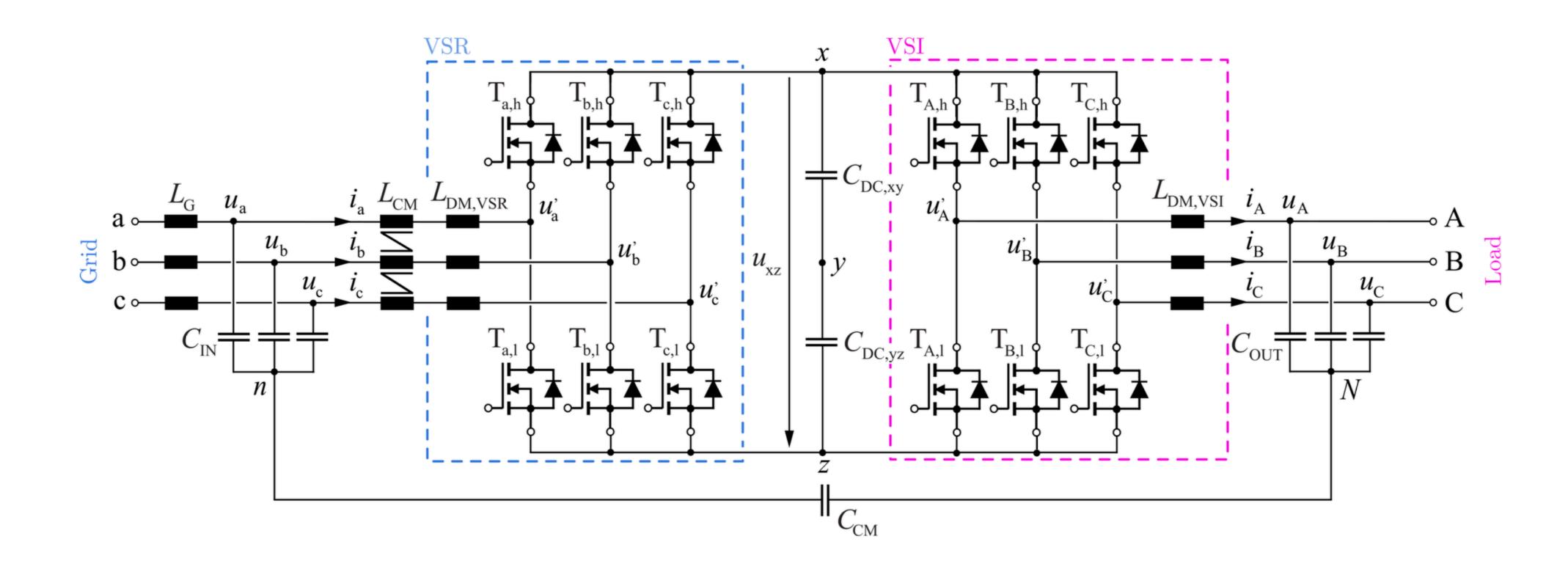
### The back-to-back AC-(DC)-AC converter



- Industry standard for bidirectional AC-AC power conversion.
- We, power electronics engineers, treat it like two VSC converters, i.e., use the DC-link as a decoupling network.


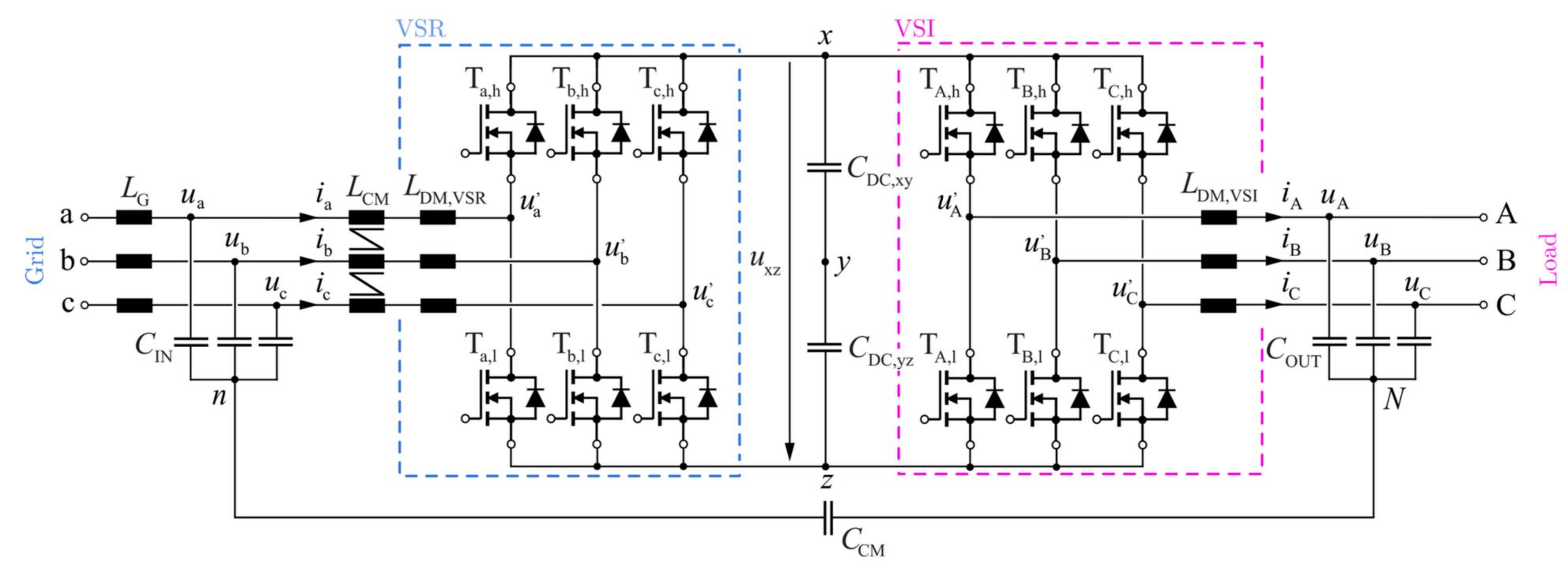
#### The back-to-back AC-(DC)-AC converter



Let's try to see it from a different angle!


- Industry standard for bidirectional AC-AC power conversion.
- We, power electronics engineers, treat it like two VSC converters, i.e., use the DC-link as a decoupling network.


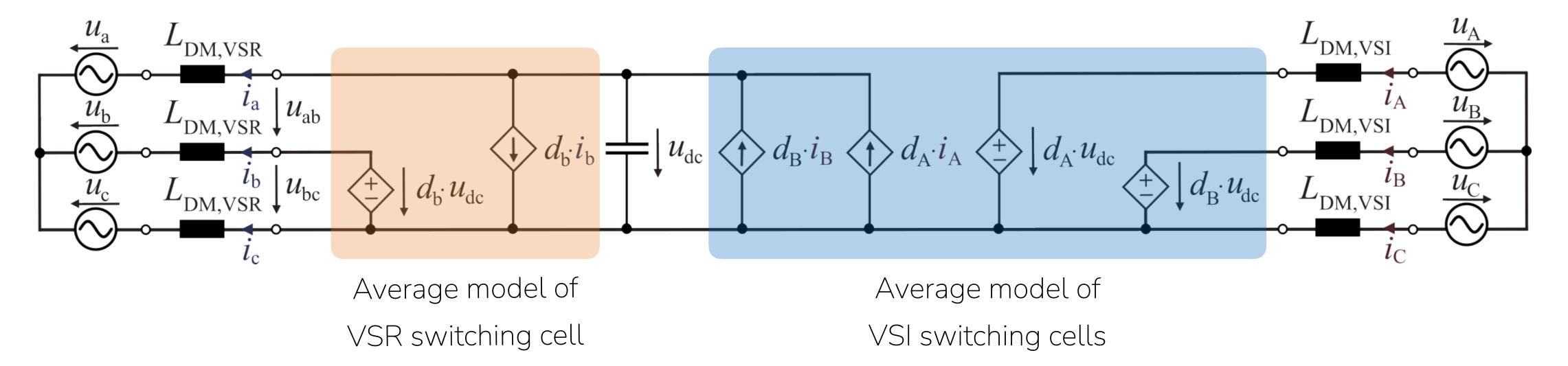
# Basic principle of operating the B2B with just three legs at a time


We start with the idea of using only three legs...

To simplify things, let's consider the average model of using only three legs,





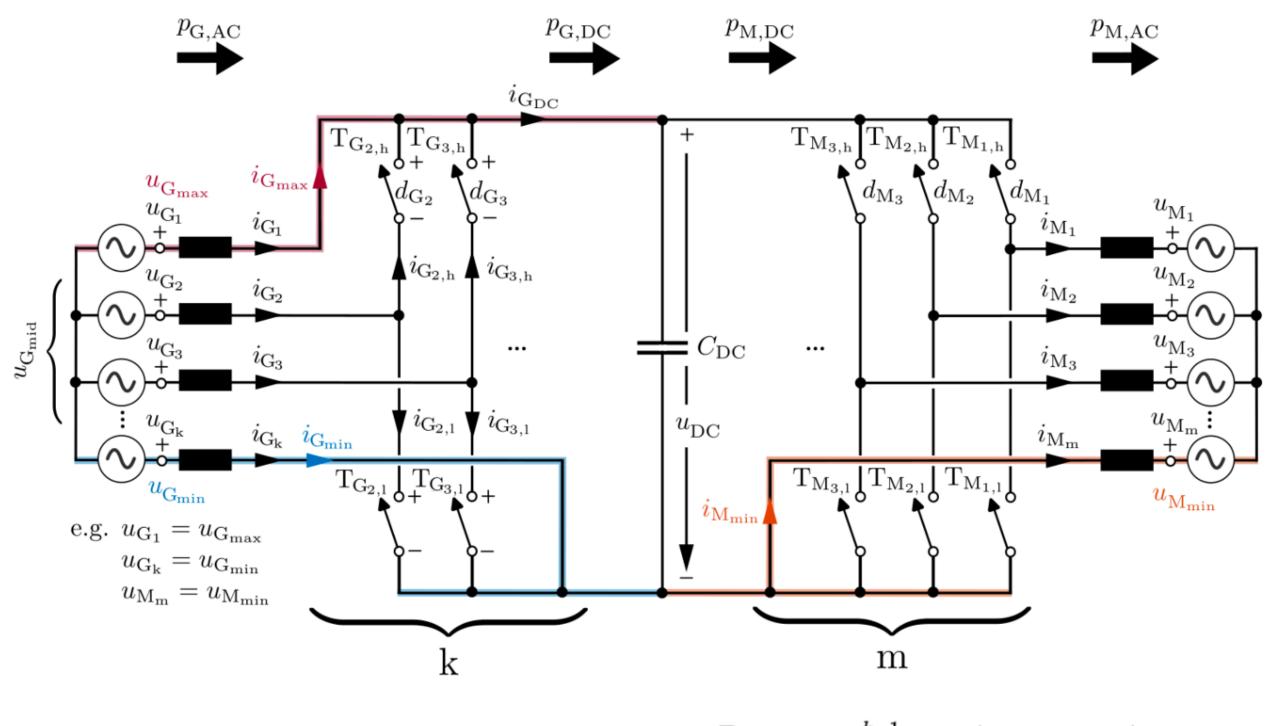
#### Generalization to any number of phases



$$\frac{\text{controlled}}{d_{G_{2...k-1}}} \Longrightarrow \begin{cases} i_{G_1} = i_{G_{\text{max}}} = \frac{P}{u_{G_{\text{max}}} - u_{G_{\text{min}}}} - \sum_{l=2}^{k-1} \frac{i_{G_l} \cdot (u_{G_l} - u_{G_{\text{min}}})}{u_{G_{\text{max}}} - u_{G_{\text{min}}}} \end{cases} \Longrightarrow \begin{cases} i_{G_1} = i_{G_{\text{max}}} = \frac{P}{u_{G_{\text{max}}} - u_{G_{\text{min}}}} - \sum_{l=2}^{k-1} \frac{i_{G_l} \cdot (u_{G_{\text{max}}} - u_{G_{\text{min}}})}{u_{G_{\text{max}}} - u_{G_{\text{min}}}} \end{cases}$$

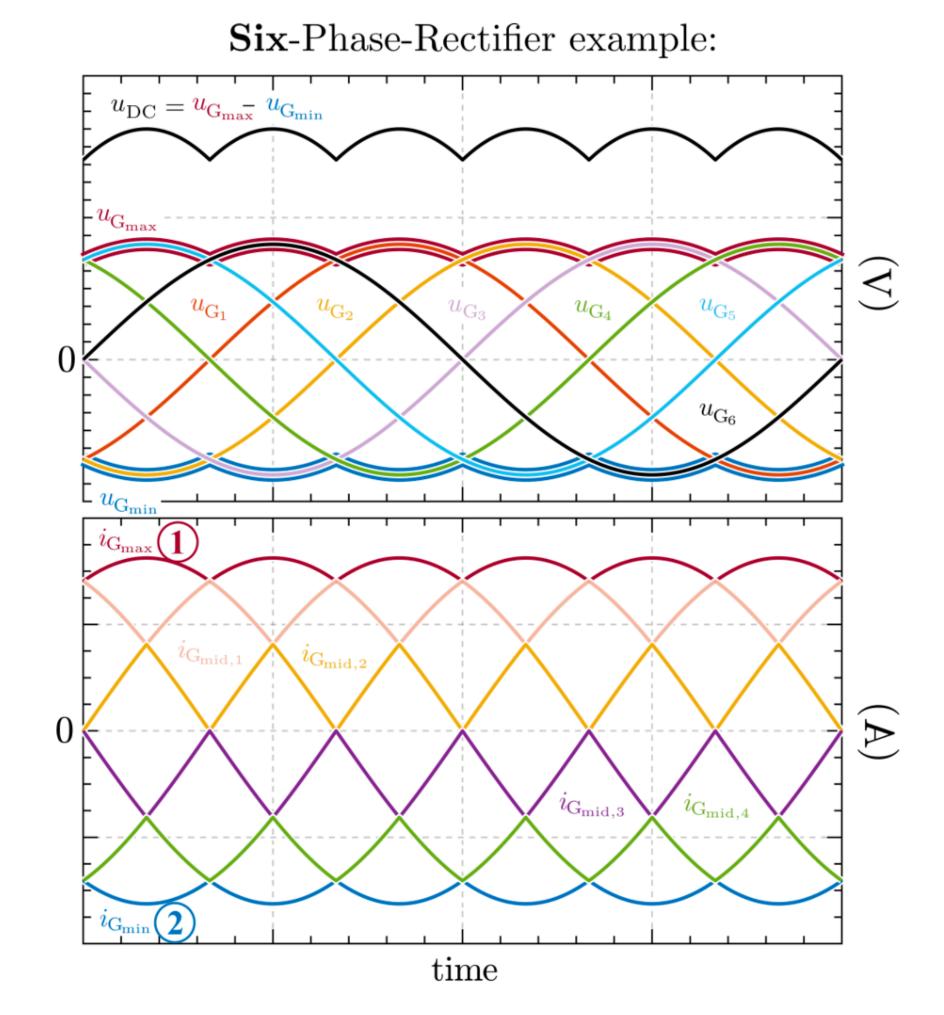



Grid side voltages,

$$u_j = \hat{U}_{\rm m} \sin(\omega_{\rm m} t - \theta_j)$$
, with  $j = a, b, c$   
 $\theta_{\rm a} = 0$ ,  $\theta_{\rm b} = \frac{2\pi}{3}$ ,  $\theta_{\rm c} = -\frac{2\pi}{3}$ ,



Motor side voltages,

$$u_k = \hat{U}_0 \sin(\omega_0 t - \phi - \theta_k), \text{ with } k = A, B, C$$
  
 $\theta_A = 0, \, \theta_B = \frac{2\pi}{3}, \, \theta_C = -\frac{2\pi}{3},$ 



$$u_{
m VSR,max} = \max(u_{
m a}, u_{
m b}, u_{
m c})$$
 $u_{
m VSR,min} = \min(u_{
m a}, u_{
m b}, u_{
m c})$ 
 $u_{
m VSR,mid} = -(u_{
m VSR,max} + u_{
m VSR,min})$ 
 $u_{
m VSI,max} = \max(u_{
m A}, u_{
m B}, u_{
m C})$ 
 $u_{
m VSI,min} = \min(u_{
m A}, u_{
m B}, u_{
m C})$ 
 $u_{
m VSI,min} = -(u_{
m VSI,max} + u_{
m VSI,min})$ 



Grid side voltages,

$$u_j = \hat{U}_{\rm m} \sin(\omega_{\rm m} t - \theta_j)$$
, with  $j = a, b, c$   
 $\theta_{\rm a} = 0$ ,  $\theta_{\rm b} = \frac{2\pi}{3}$ ,  $\theta_{\rm c} = -\frac{2\pi}{3}$ ,



Motor side voltages,

$$u_k = \hat{U}_0 \sin(\omega_0 t - \phi - \theta_k), \text{ with } k = A, B, C$$
  
 $\theta_A = 0, \, \theta_B = \frac{2\pi}{3}, \, \theta_C = -\frac{2\pi}{3},$ 



$$u_{
m VSR,max} = \max(u_{
m a}, u_{
m b}, u_{
m c})$$
 $u_{
m VSR,min} = \min(u_{
m a}, u_{
m b}, u_{
m c})$ 
 $u_{
m VSR,mid} = -(u_{
m VSR,max} + u_{
m VSR,min})$ 
 $u_{
m VSI,max} = \max(u_{
m A}, u_{
m B}, u_{
m C})$ 
 $u_{
m VSI,min} = \min(u_{
m A}, u_{
m B}, u_{
m C})$ 
 $u_{
m VSI,mid} = -(u_{
m VSI,max} + u_{
m VSI,min})$ 

The largest line-to-line voltages are defined as,

$$u_{\text{VSI},13} = u_{\text{VSI},\text{max}} - u_{\text{VSI},\text{min}}$$
  
 $u_{\text{VSI},13} = u_{\text{VSI},\text{max}} - u_{\text{VSI},\text{min}}$ 



Grid side voltages,

$$u_j = \hat{U}_{\rm m} \sin(\omega_{\rm m} t - \theta_j)$$
, with  $j = a, b, c$   
 $\theta_{\rm a} = 0$ ,  $\theta_{\rm b} = \frac{2\pi}{3}$ ,  $\theta_{\rm c} = -\frac{2\pi}{3}$ ,



Motor side voltages,

$$u_k = \hat{U}_0 \sin(\omega_0 t - \phi - \theta_k), \text{ with } k = A, B, C$$
  
 $\theta_A = 0, \, \theta_B = \frac{2\pi}{3}, \, \theta_C = -\frac{2\pi}{3},$ 

Organizing the voltages according to their amplitudes:

$$u_{
m VSR,max} = \max(u_{
m a}, u_{
m b}, u_{
m c})$$
 $u_{
m VSR,min} = \min(u_{
m a}, u_{
m b}, u_{
m c})$ 
 $u_{
m VSR,mid} = -(u_{
m VSR,max} + u_{
m VSR,min})$ 
 $u_{
m VSI,max} = \max(u_{
m A}, u_{
m B}, u_{
m C})$ 
 $u_{
m VSI,min} = \min(u_{
m A}, u_{
m B}, u_{
m C})$ 
 $u_{
m VSI,mid} = -(u_{
m VSI,max} + u_{
m VSI,min})$ 

The largest line-to-line voltages are defined as,

$$u_{\text{VSI},13} = u_{\text{VSI},\text{max}} - u_{\text{VSI},\text{min}}$$
  
 $u_{\text{VSI},13} = u_{\text{VSI},\text{max}} - u_{\text{VSI},\text{min}}$ 

A minimum DC-link voltage  $v_{xy}$  will lead to reduced switching losses. We know that  $v_{xy}$  needs to be larger than the maximum overall system voltage, i.e.,

$$u_{xz} = \max(u_{VSR,13}, u_{VSI,13})$$



Rewriting,  $u_{xz} = \max(u_{\text{VSR},13}, u_{\text{VSI},13})$ 

Now, we need modulation/reference voltage signals that would generate proper voltages in both sides. We can assume that the voltage drops across the inverter and rectifier inductances will be low, i.e.,

$$\Delta u_{LDM,j-k} = L_{DM,j-k} \frac{\mathrm{d}i_{LDM,j-k}}{\mathrm{d}t} \approx 0$$

Thus, the modulation signals should be,  $d_{\rm VSR-I,max} = (u_{\rm VSR-I,max})/(u_{\rm xz}/2) + d_{\rm VSR-I,CM}$   $d_{\rm VSR-I,mid} = (u_{\rm VSR-I,mid})/(u_{\rm xz}/2) + d_{\rm VSR-I,CM}$   $d_{\rm VSR-I,min} = (u_{\rm VSR-I,min})/(u_{\rm xz}/2) + d_{\rm VSR-I,CM}$ 





Rewriting,  $u_{xz} = \max(u_{\text{VSR},13}, u_{\text{VSI},13})$ 

Now, we need modulation/reference voltage signals that would generate proper voltages in both sides. We can assume that the voltage drops across the inverter and rectifier inductances will be low, i.e.,

$$\Delta u_{LDM,j-k} = L_{DM,j-k} \frac{\mathrm{d}i_{LDM,j-k}}{\mathrm{d}t} \approx 0$$


Thus, the modulation signals should be,  $d_{\rm VSR-I,max} = (u_{\rm VSR-I,max})/(u_{\rm xz}/2) + d_{\rm VSR-I,CM}$   $d_{\rm VSR-I,mid} = (u_{\rm VSR-I,mid})/(u_{\rm xz}/2) + d_{\rm VSR-I,CM}$   $d_{\rm VSR-I,min} = (u_{\rm VSR-I,min})/(u_{\rm xz}/2) + d_{\rm VSR-I,CM}$ 

A smooth transition between 1/3 and 2/3 modulation modes can be achieved by employing the 0-axis (common mode) signal,


$$d_{\text{VSR-I,CM}} = \frac{u_{\text{VSR-I,min}}}{u_{\text{xz}}/2} + 1$$


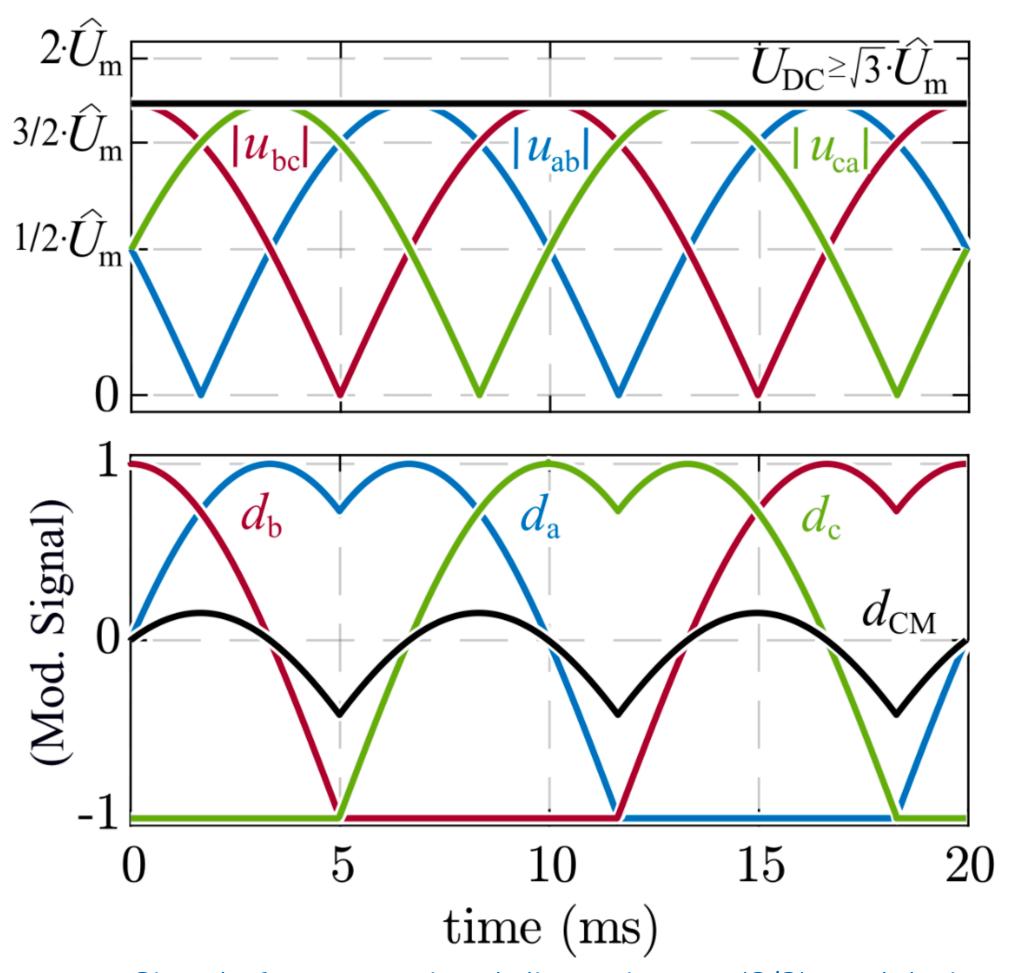
# Principles of discontinuous modulation for a VSC



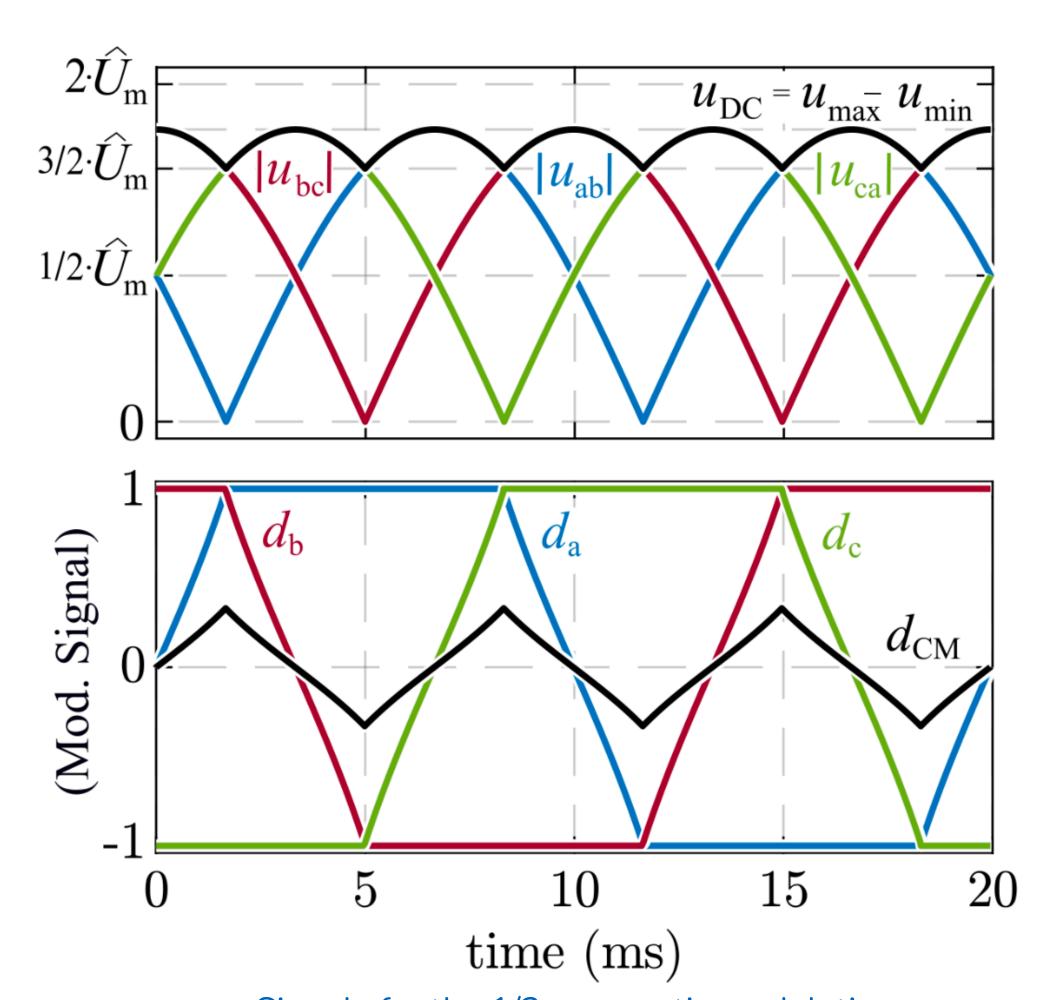Signals for conventional discontinuous (2/3) modulation Remark: Zero modulation margin.





Signals for the 1/3 synergetic modulation



# Principles of discontinuous modulation for a VSC


#### Exemplary switching losses:

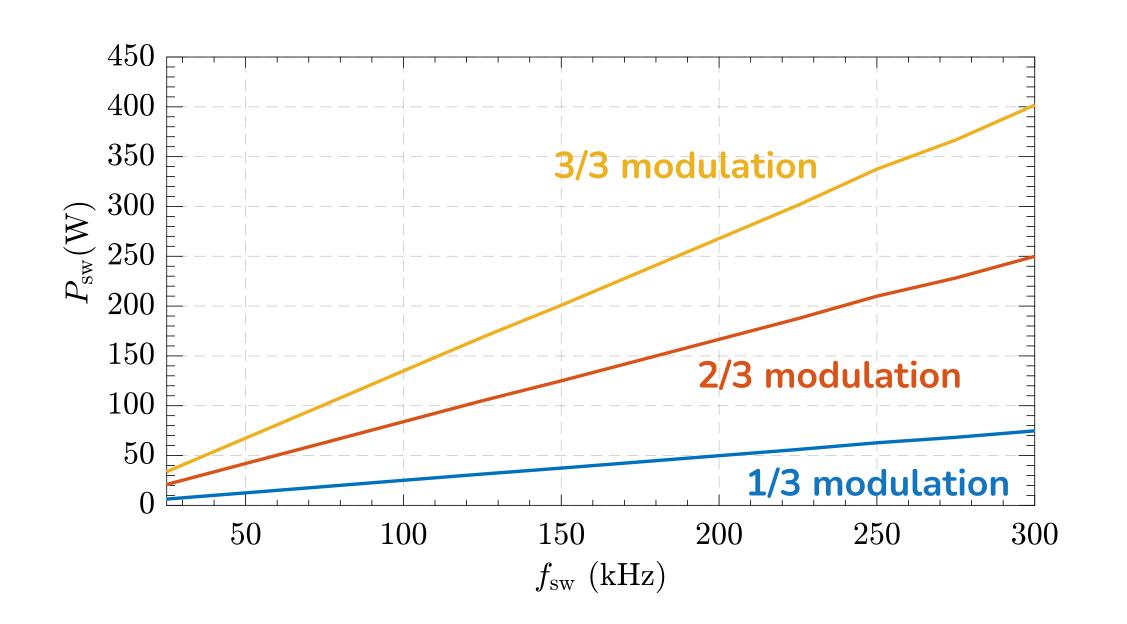


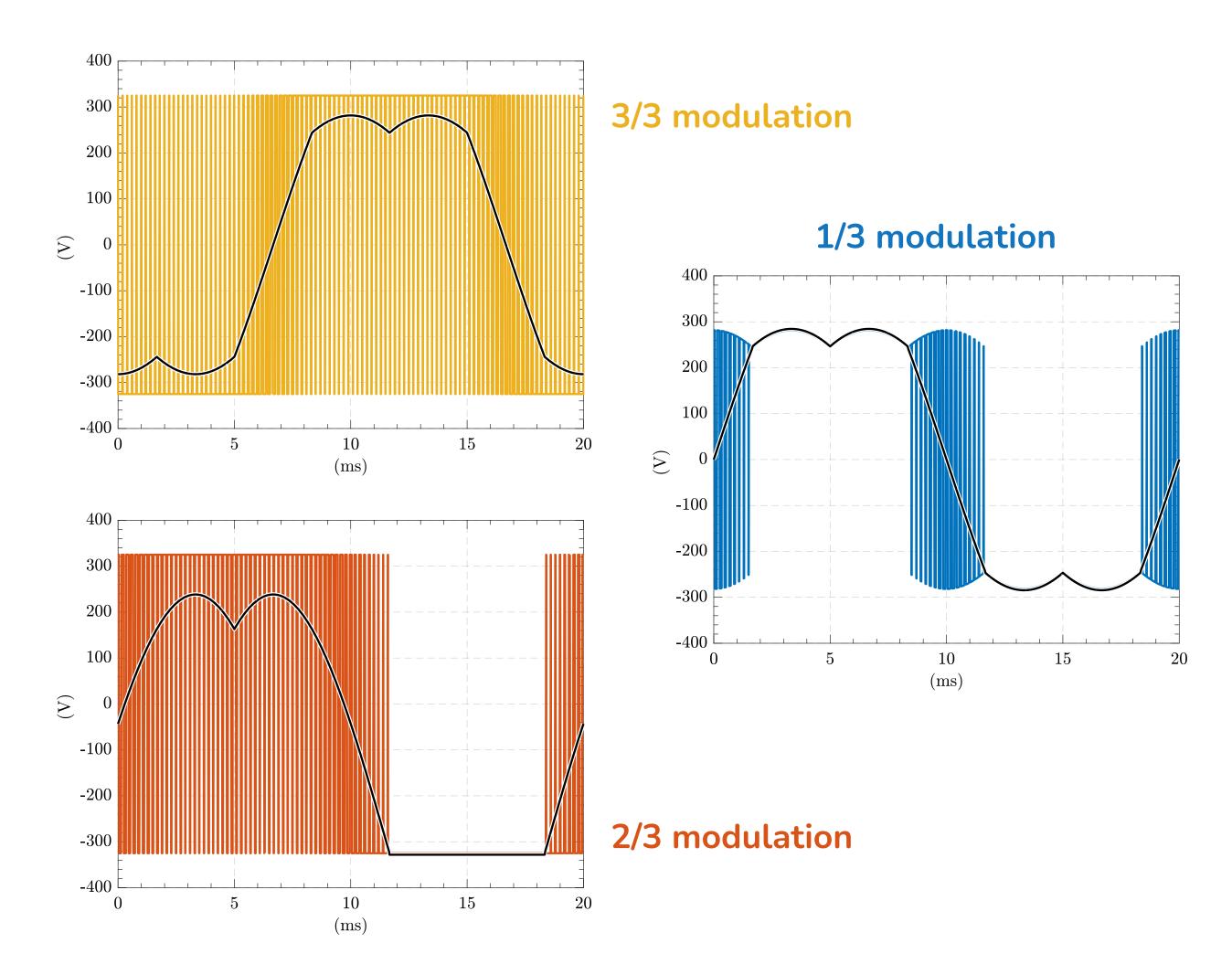




# Control principle

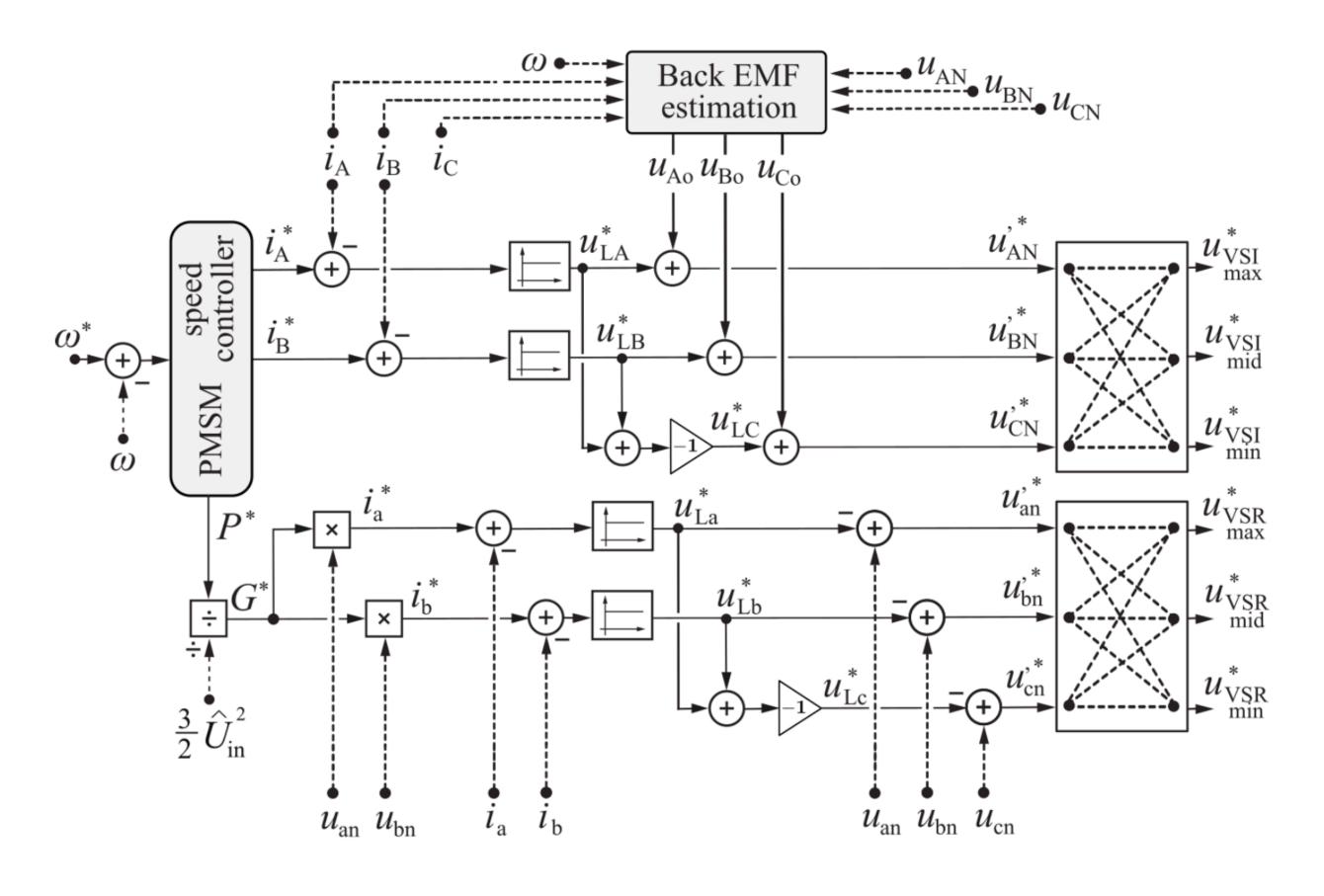

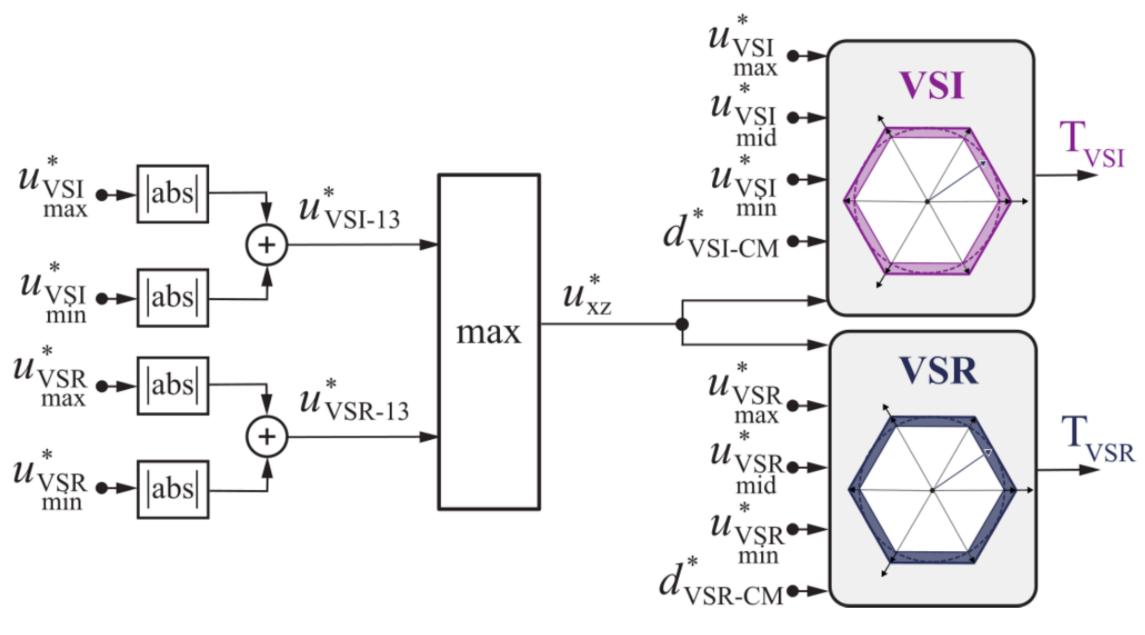



#### Waveforms

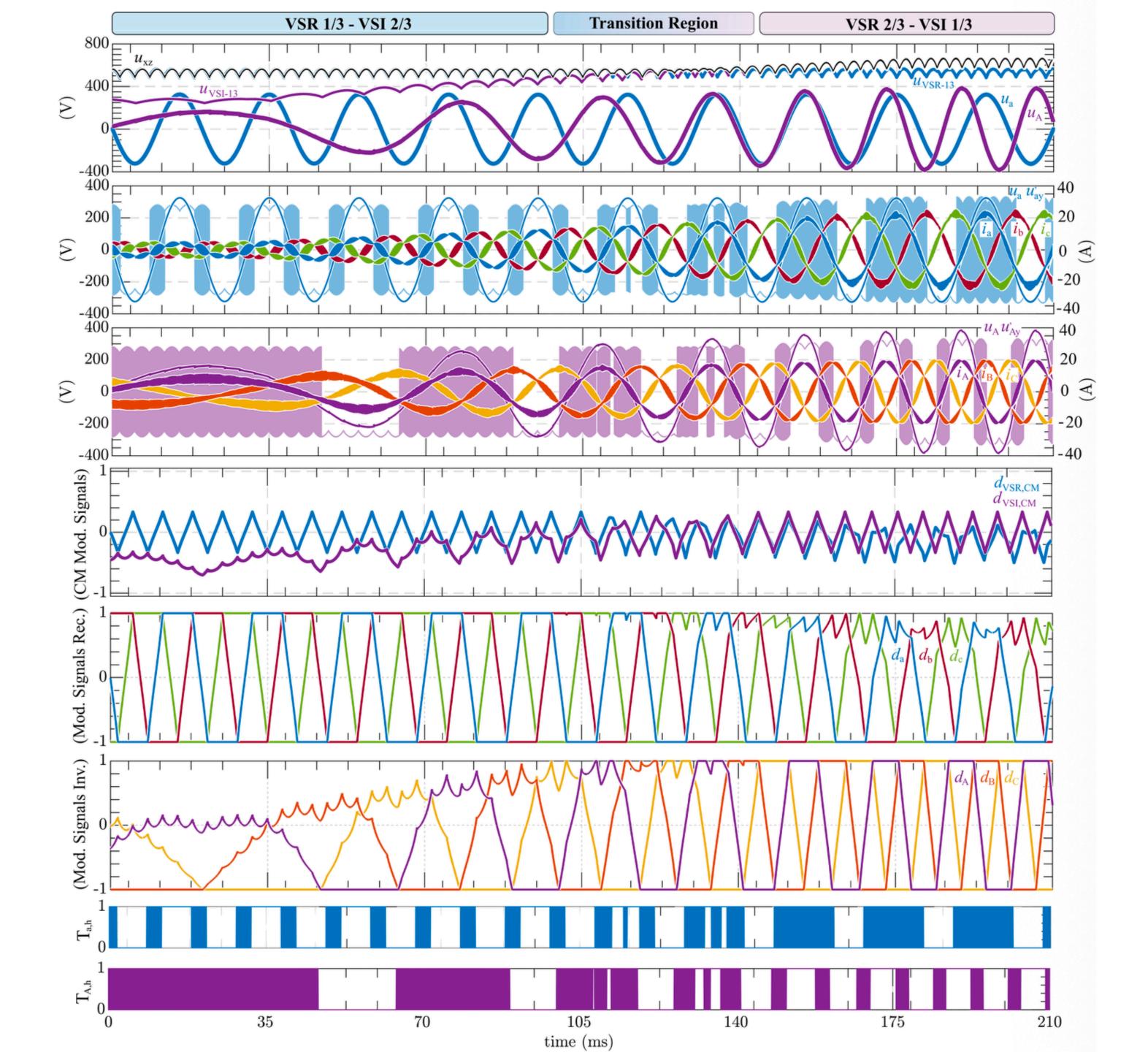



# Design with IGBTs

Specifications

$$P = 50 \,\mathrm{kW}$$


$$V_{\rm grid} = 380 \,\mathrm{V}$$

$$f_{\rm grid} = 50 \, \mathrm{Hz}$$

 $f_o \in \{0..60\} \, \text{Hz}$ 


IGBT:


FS75R12W2T7 (1200 V, 75 A)

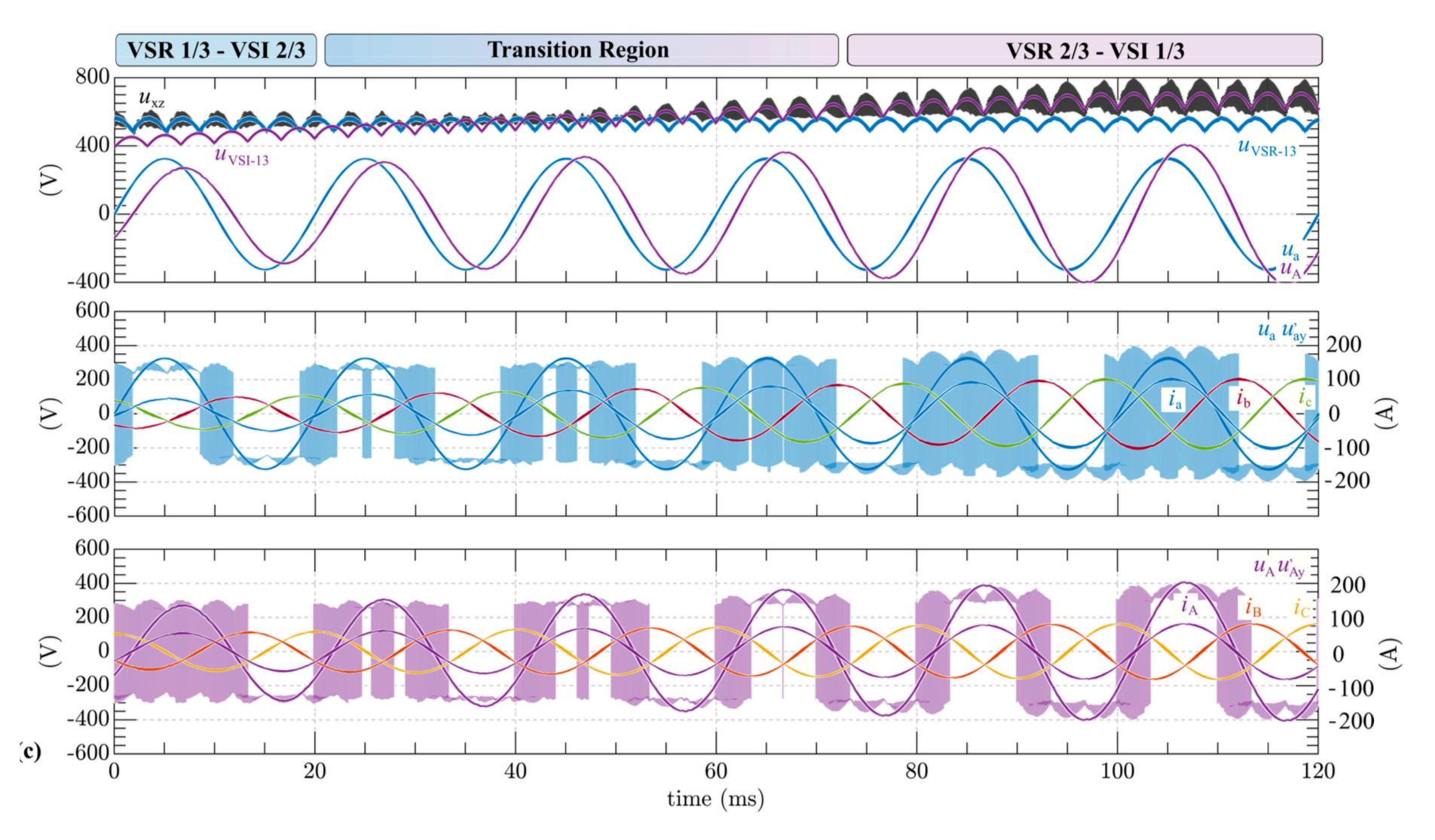




# Design with IGBTs

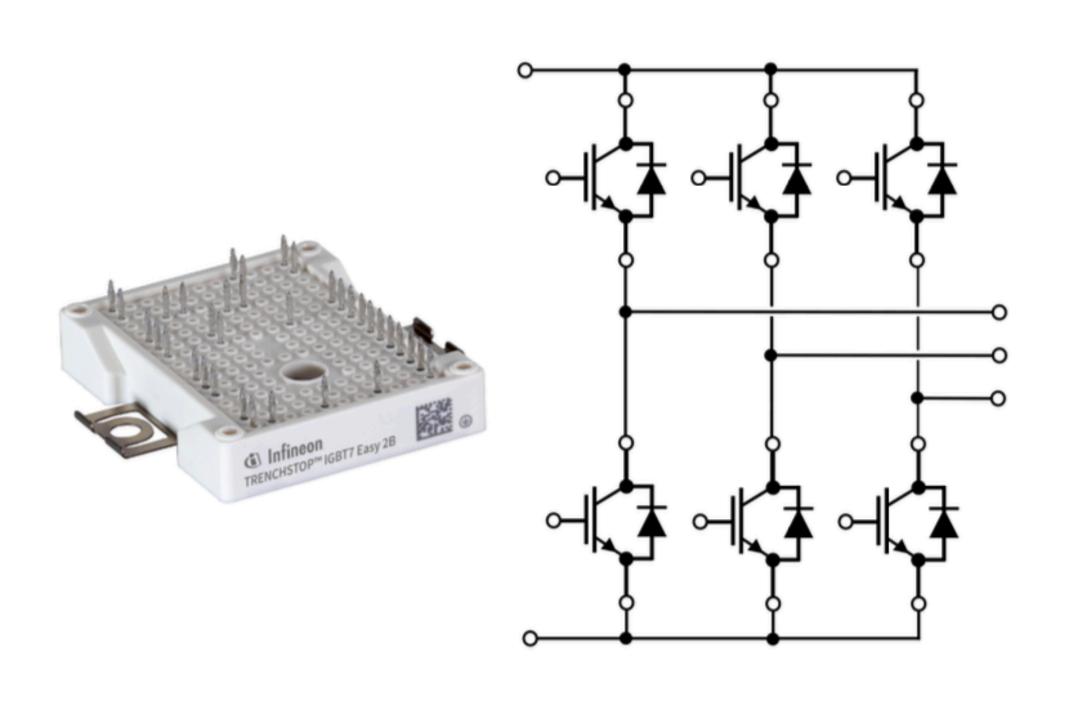


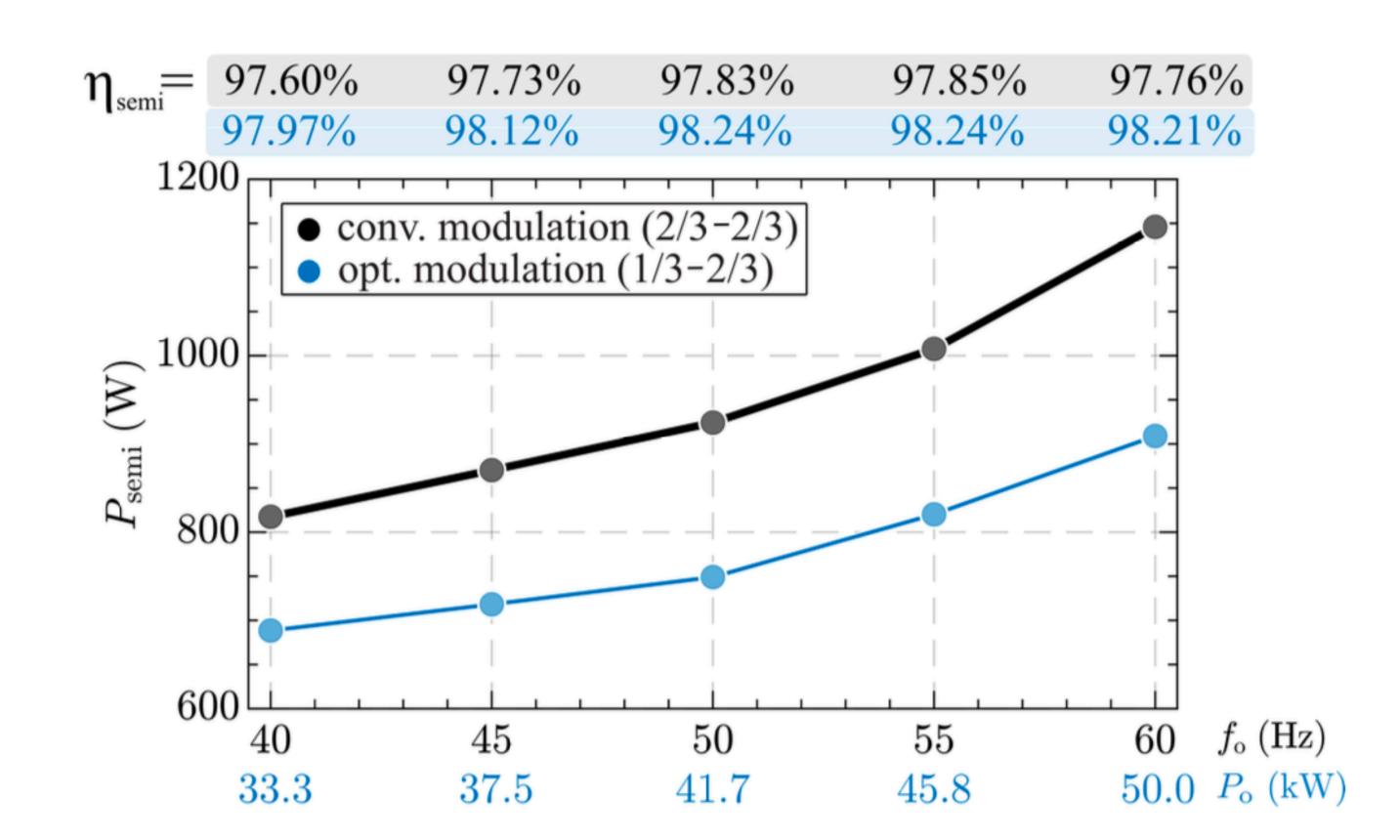



# Design with IGBTs

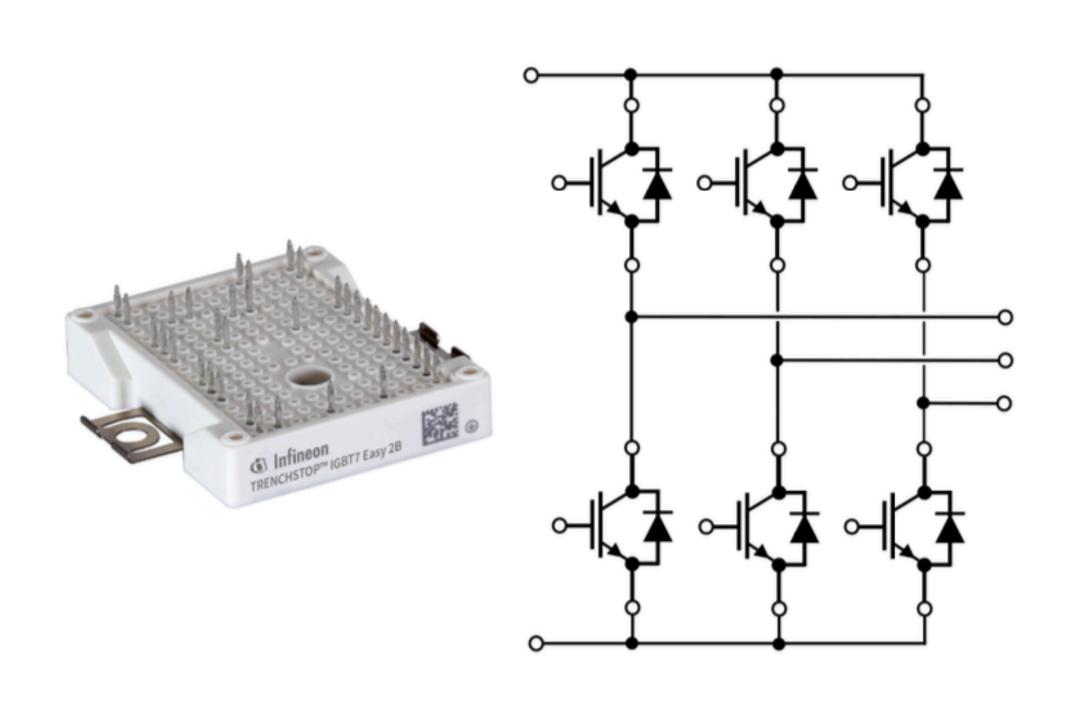

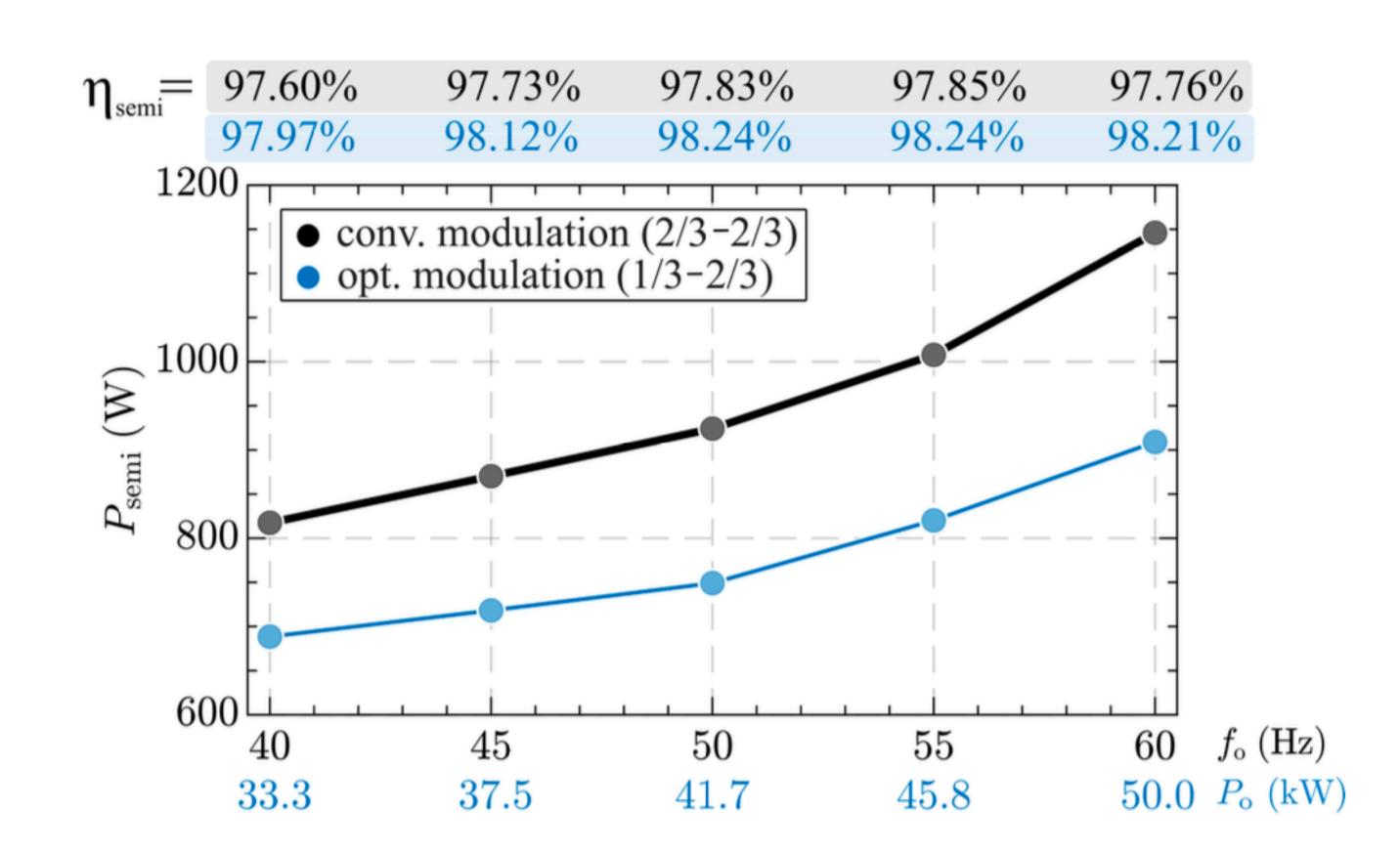

Again, 99% was not feasible...




# Prototype

Specifications and parameters:

$$P = 11 \, \mathrm{kW} \, ; V_{\mathrm{grid}} = 380 \, \mathrm{V} \, ; f_{\mathrm{grid}} = 50 \, \mathrm{Hz} \, ; f_o \in \{0..60\} \, \mathrm{Hz}$$

Description	Value
VSR-I semi.	C3M0016120K (1200 V, 16 mΩ)
VSR-I DM ind.	140 μH (2×KoolMu-60 E40/20, 22 turns)
CM ind.	1.35  mH (2×VAC 40/25/15, 3×6 turns)
DM ind.	6.8 μH (WE-7443640680B [21])
VSR DM cap. DC-link cap. VSI DM cap. CM cap.	3.0 μF 2×5.6 μF 2.2 μF 112 nF
	VSR-I semi.  VSR-I DM ind.  CM ind.  DM ind.  VSR DM cap.  DC-link cap.  VSI DM cap.

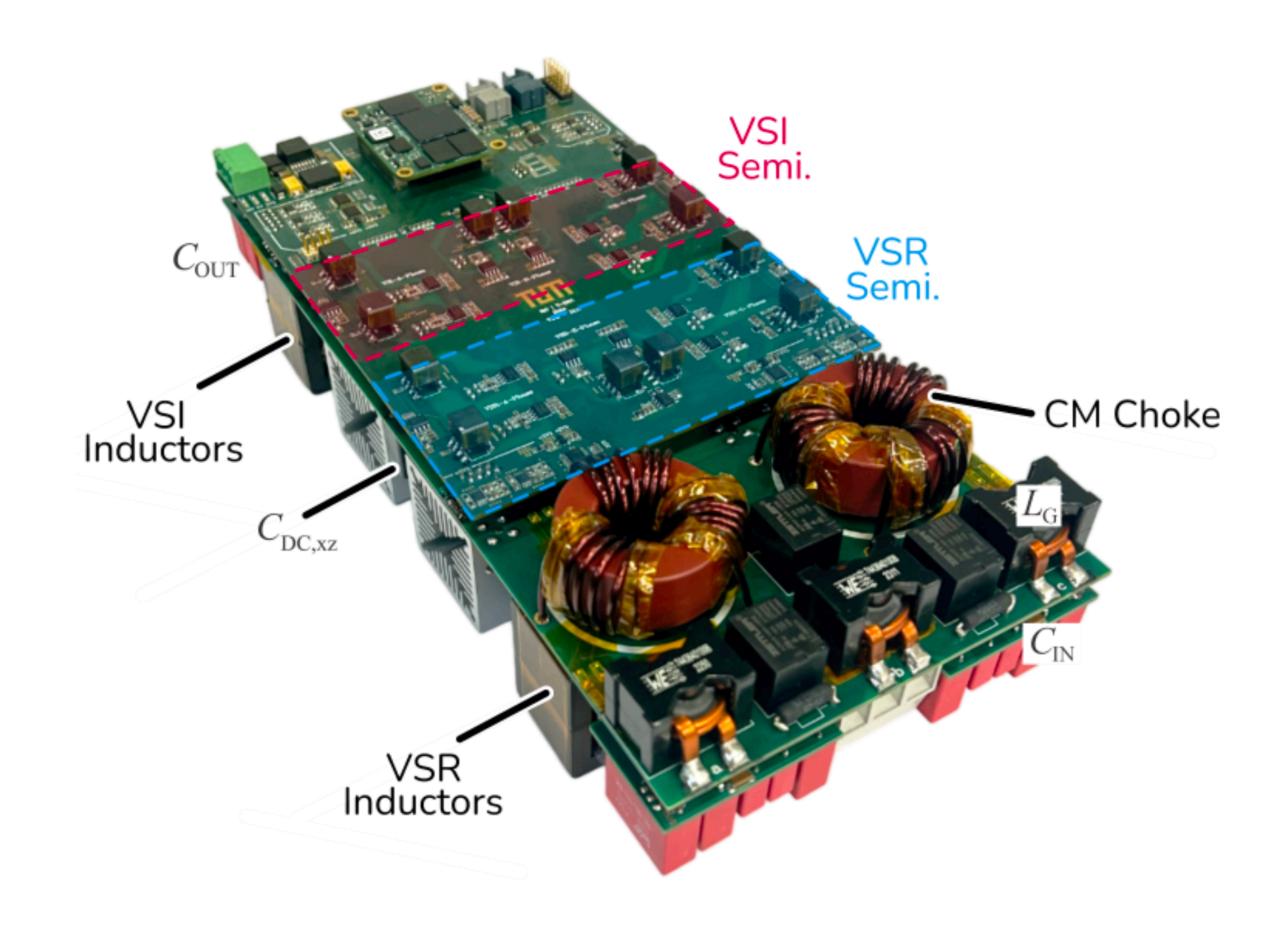


Dimensions:  $280 \times 132 \times 63 \text{ mm}^3$ 

Power density:  $\rho \approx 4.7 \, \text{kW/dm}^3$ 



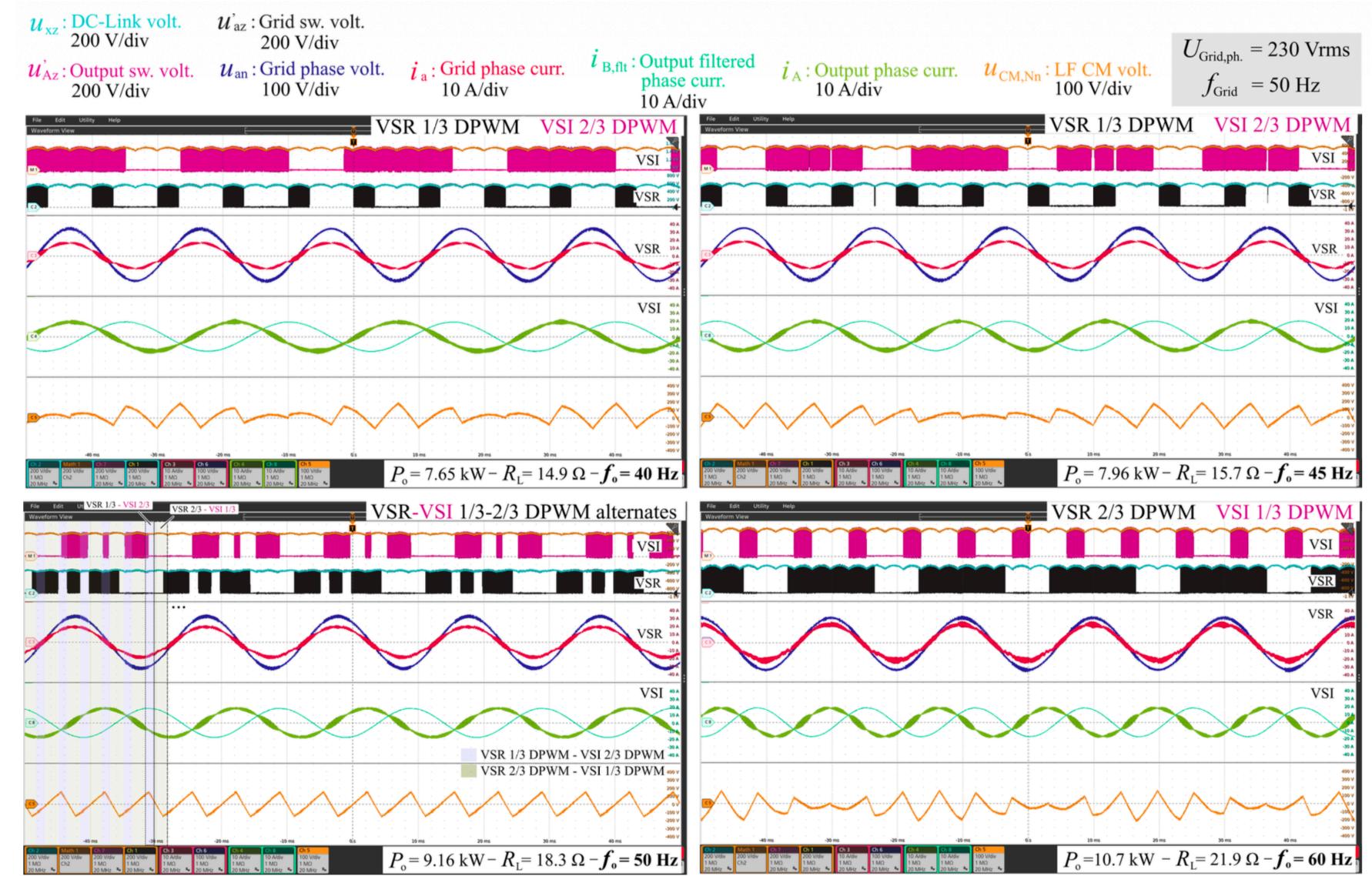
### Experimental waveforms - different steady state conditions





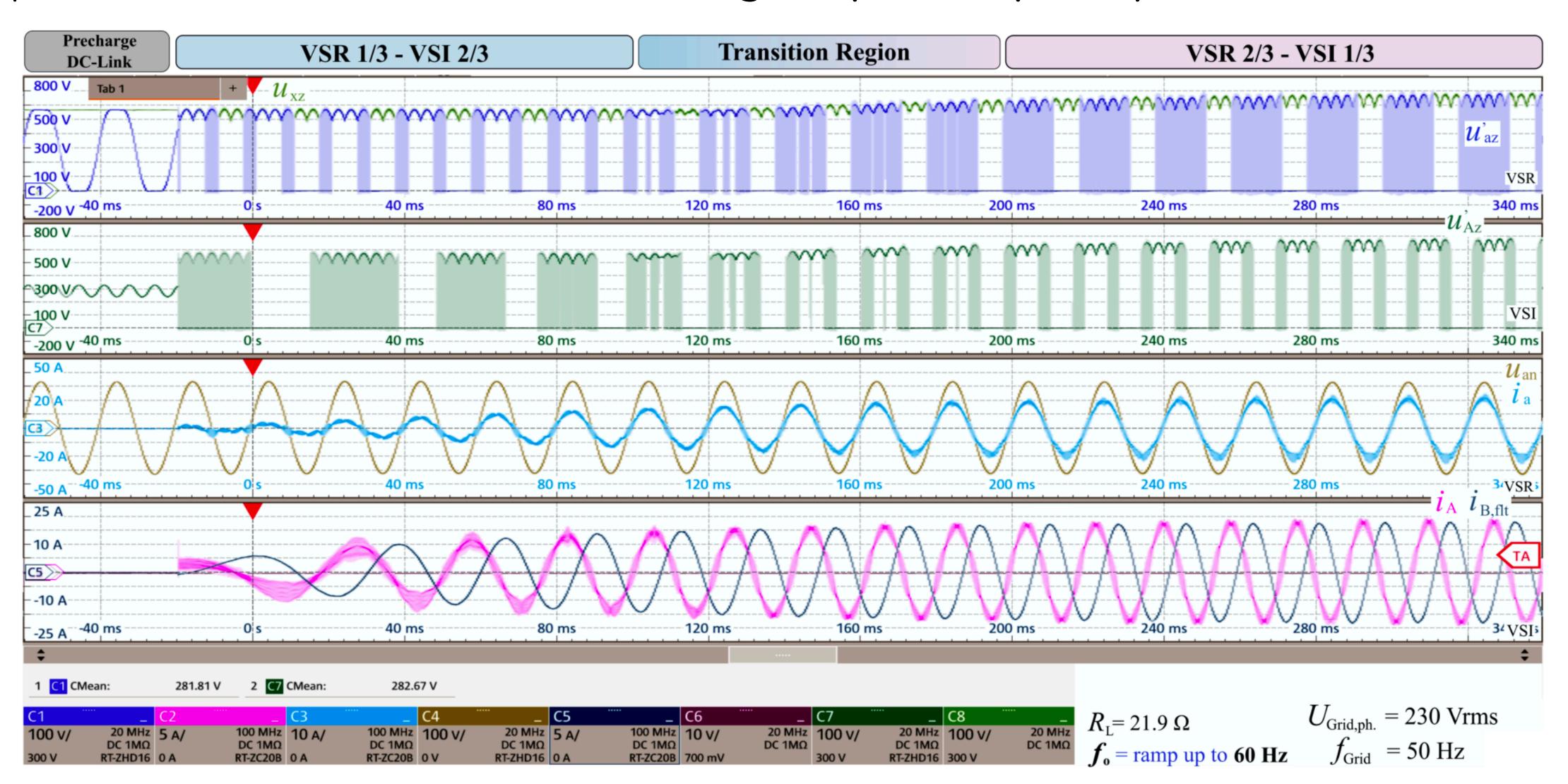
#### Experimental waveforms - increasing output frequency






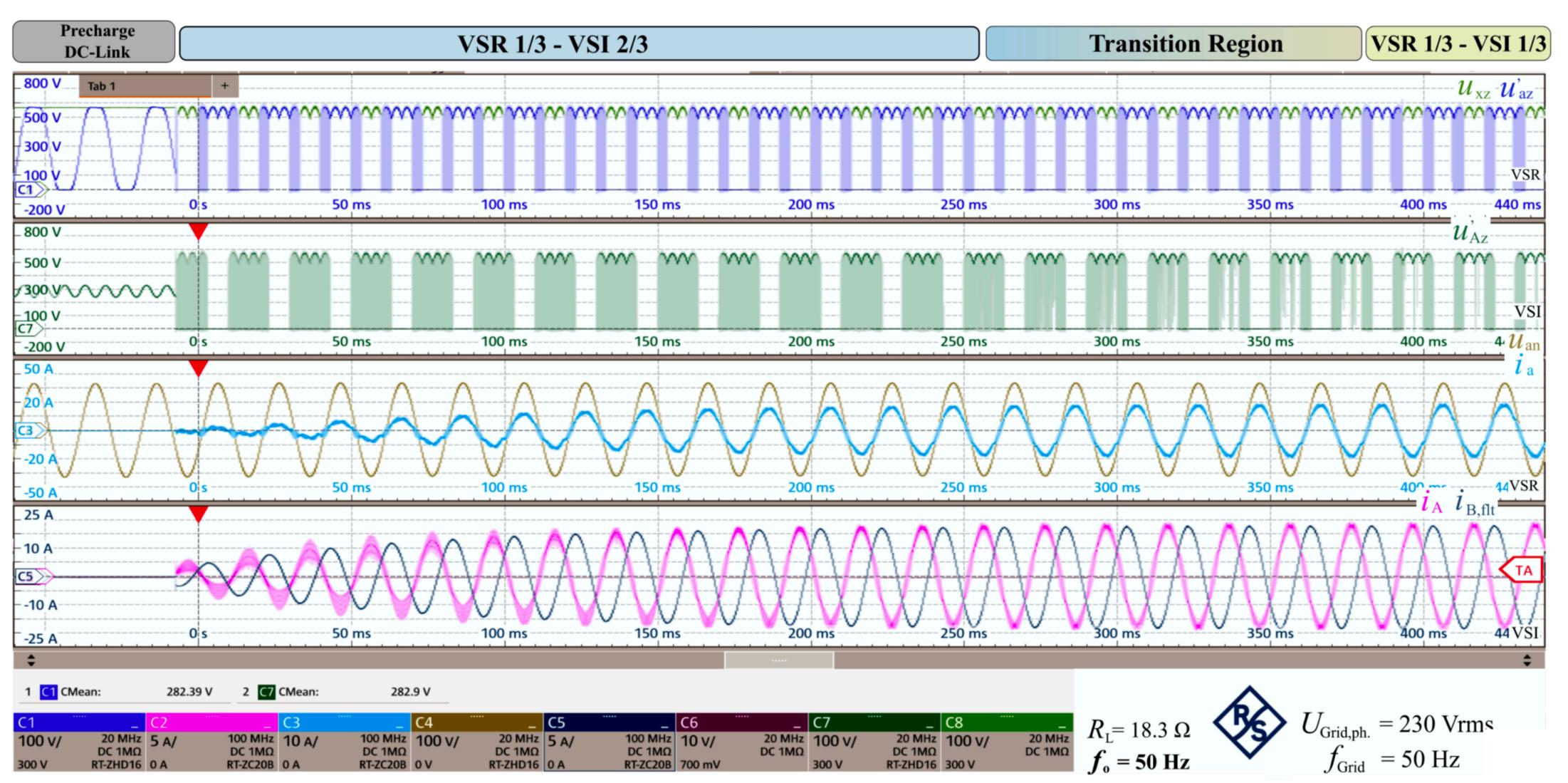
### Experimental waveforms - output frequency = input frequency






### Loss analysis

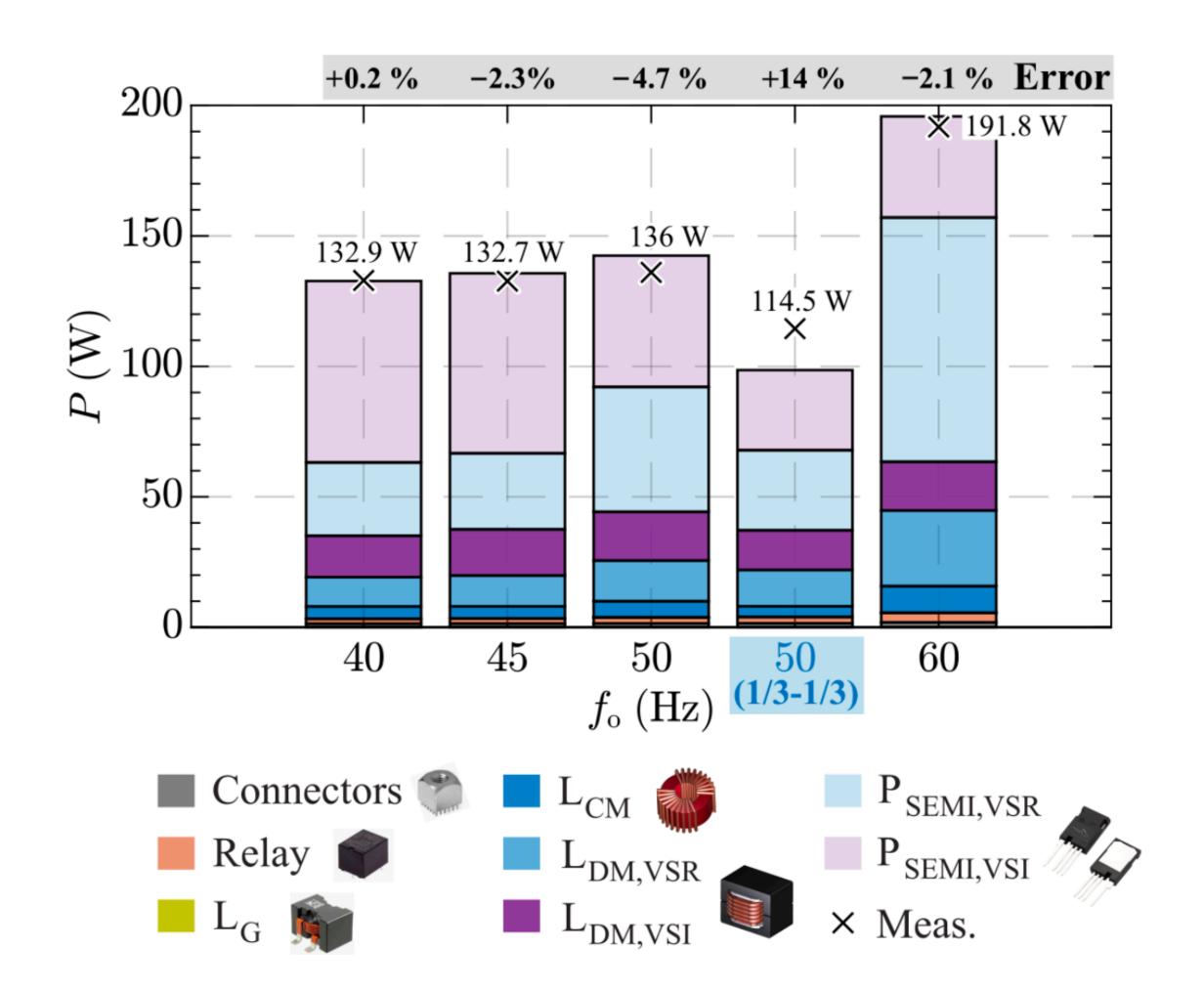

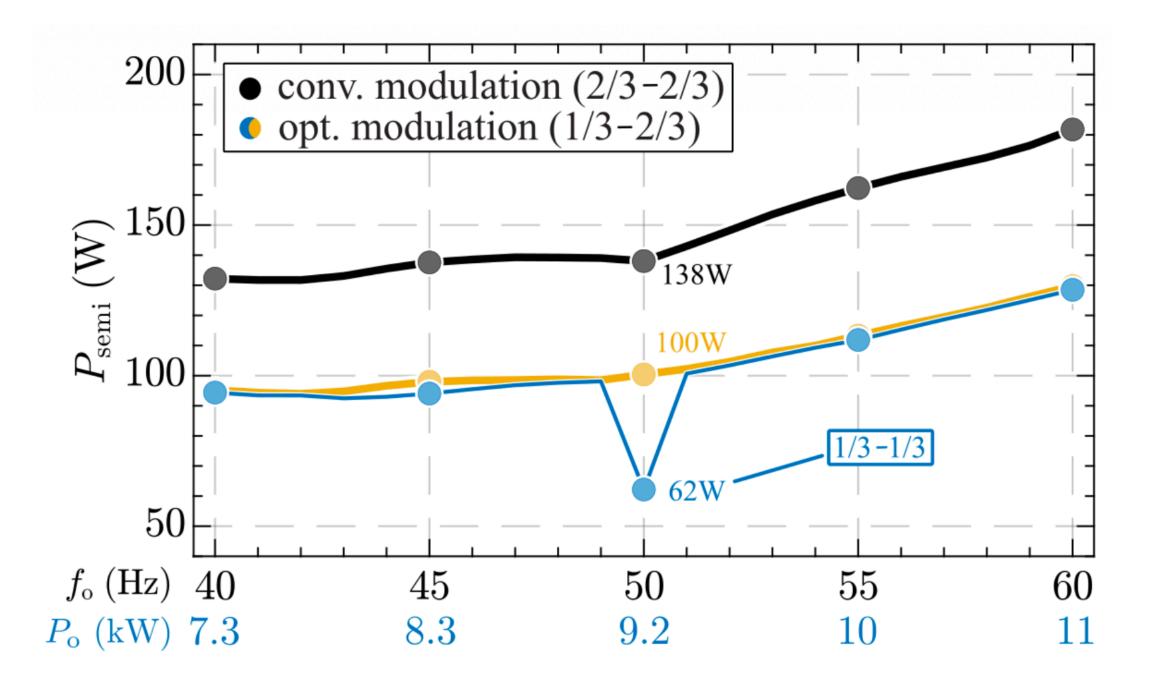




# Measured efficiency values

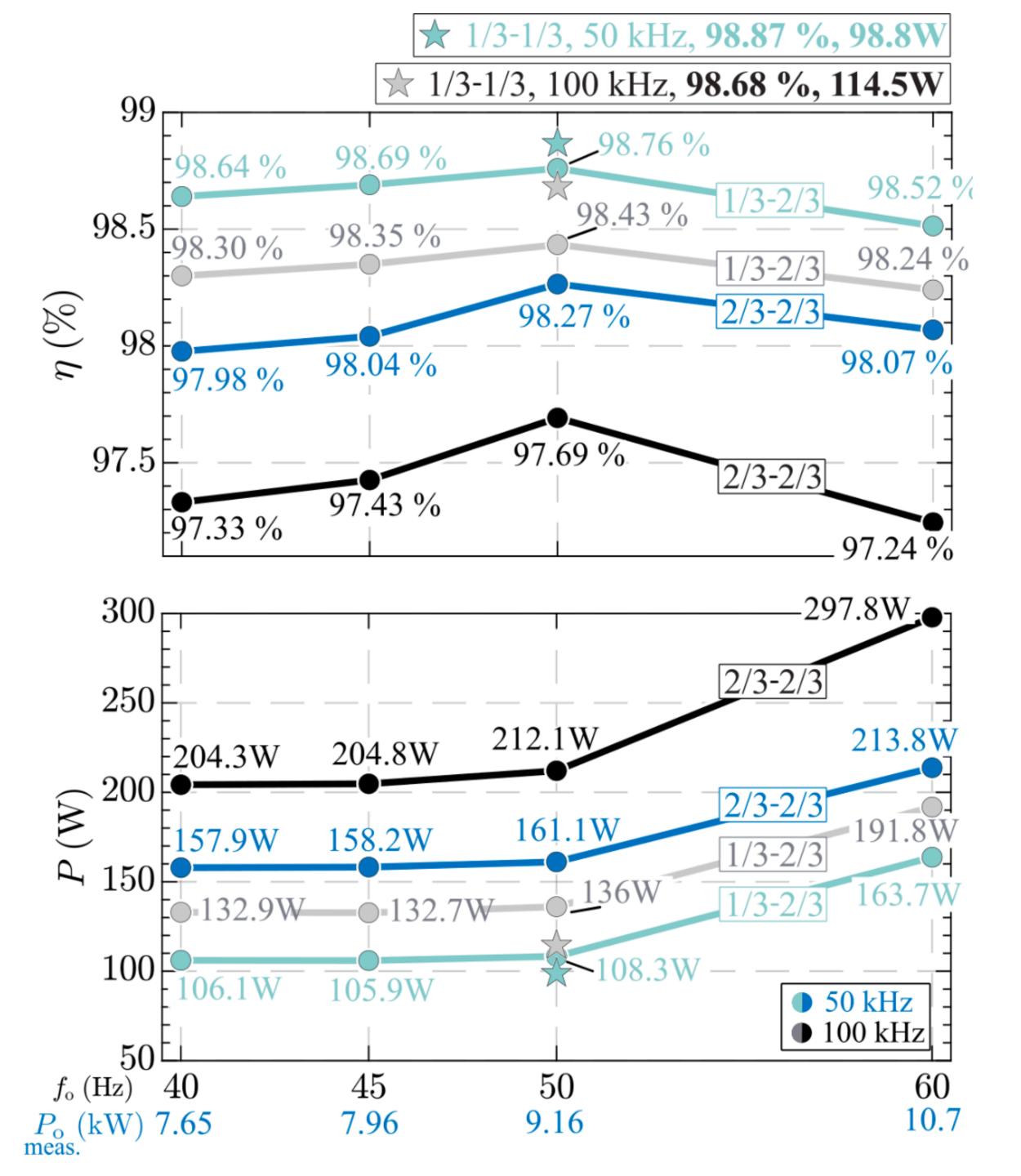


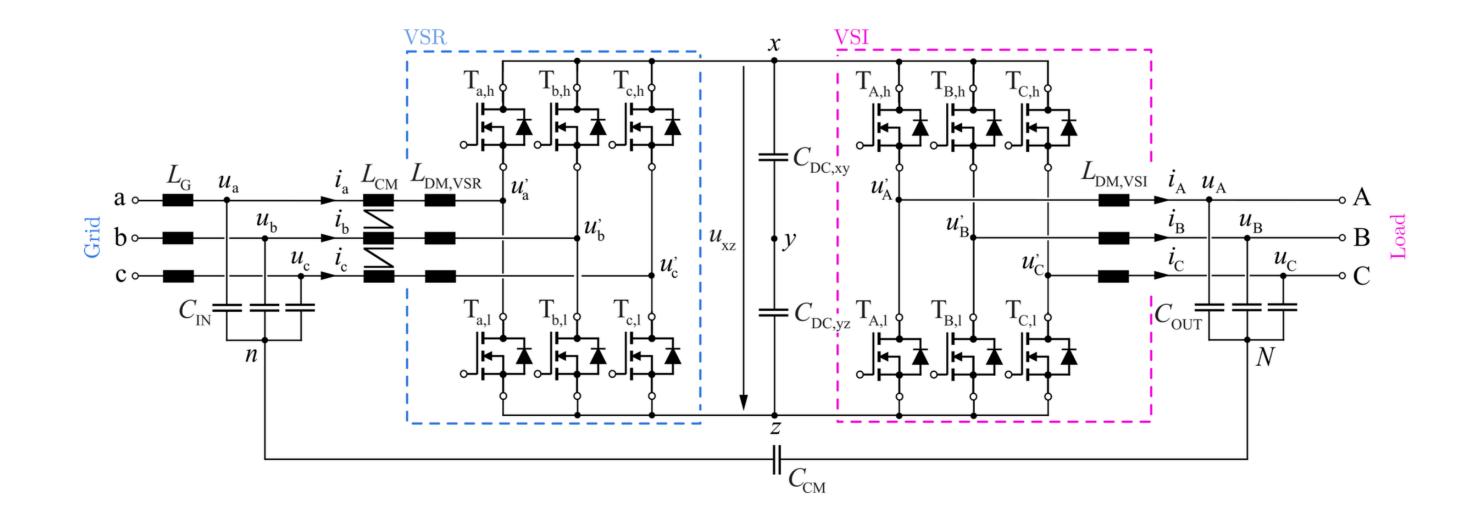
### Critical evaluation of the three-leg operated VSC-B2B concept



Industry standard topology, can be operated with different switching frequencies and without a filter at the motor side if needed, switching losses are very low, conduction losses are nearly unchanged


Did not achieve 99%




# Final thoughts


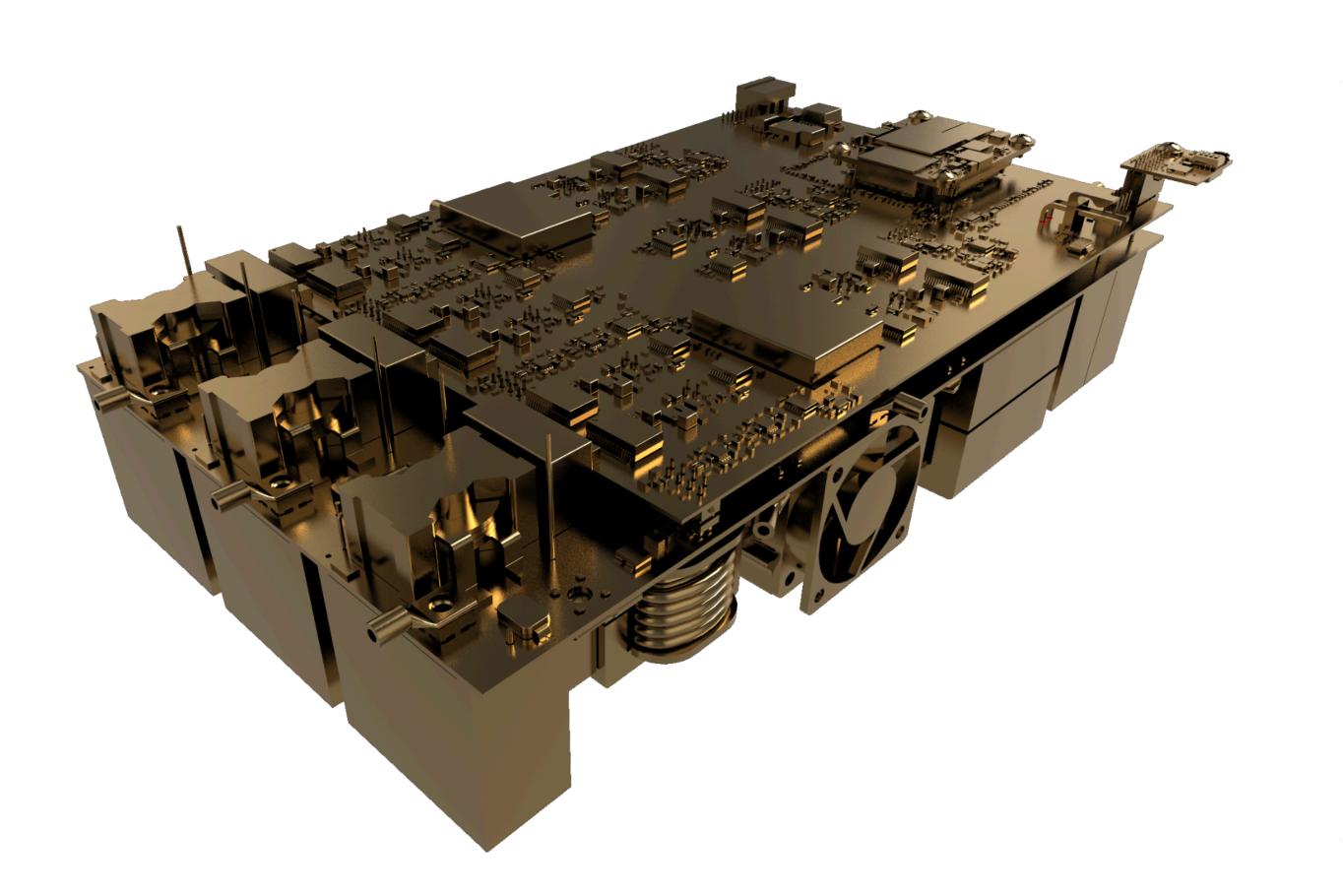
# We still want to get there... stay tuned!



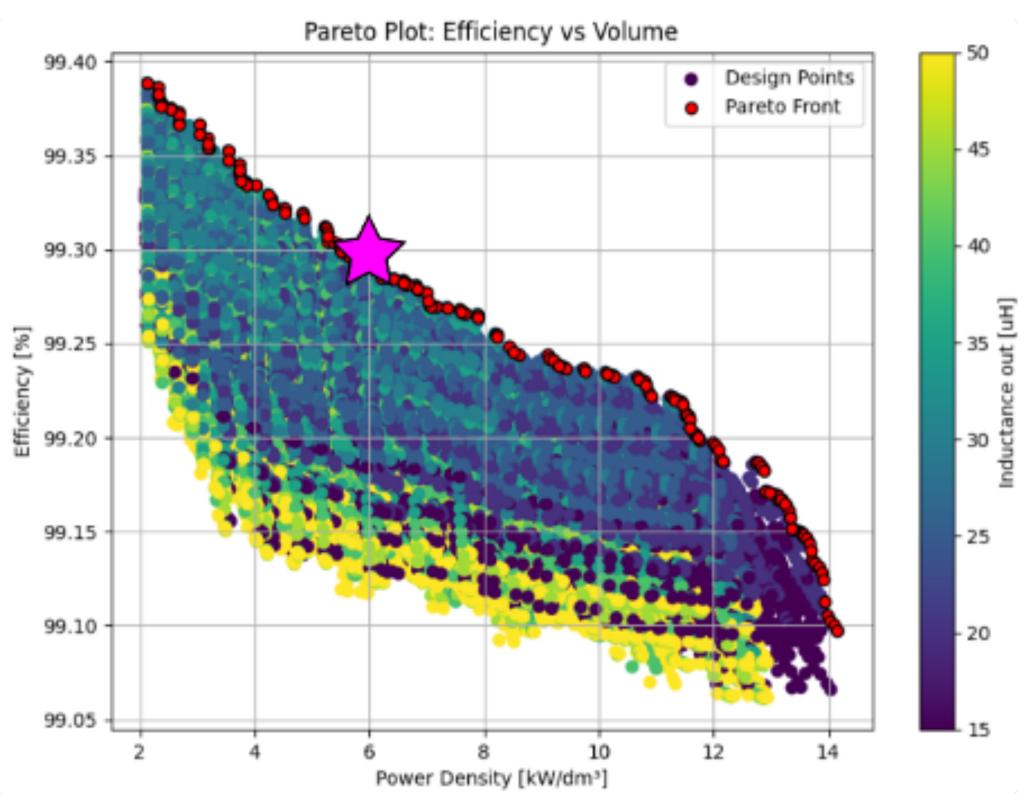



#### References

The slides without references are from these two publications:

[1] C. Leontaris, G. J. M. de Sousa and M. L. Heldwein, "Three-Stage/-Phase Voltage/Current DC-link AC-AC Converter with Synergetic Control," PCIM Europe 2025, 2025, pp. 1321-1330.

doi: https://doi.org/10.30420/566541172

[2] C. Leontaris, G. J. M. de Sousa and M. L. Heldwein, "Three-Leg Operation of Back-to-Back Converters," in IEEE Transactions on Power Electronics.

doi: https://doi.org/10.1109/TPEL.2025.3624327

